

6. First-Order LTI Systems

A. First-Order LTI systems

B. First-Order Filter: RC Circuit

Linear time-invariant systems, or briefly called LTI systems, are the most important systems in engineering even though they are ideal, not real.

A. First-Order LTI Systems

The simplest dynamic system is a first-order LTI system shown in Figure 6-1. Mathematically, it is expressed by a state equation and an output equation, given as below:

$$\dot{x}(t) = ax(t) + bu(t), \quad x(0) = x_0 \quad (6-1)$$

$$y(t) = cx(t) + du(t) \quad (6-2)$$

where $x(t)$ is the state variable representing the system intrinsic feature and $x(0) = x_0$ is its initial state at the initial time $t=0$. Besides, the system is excited by the external input $u(t)$ to generate the output response $y(t)$ accordingly.

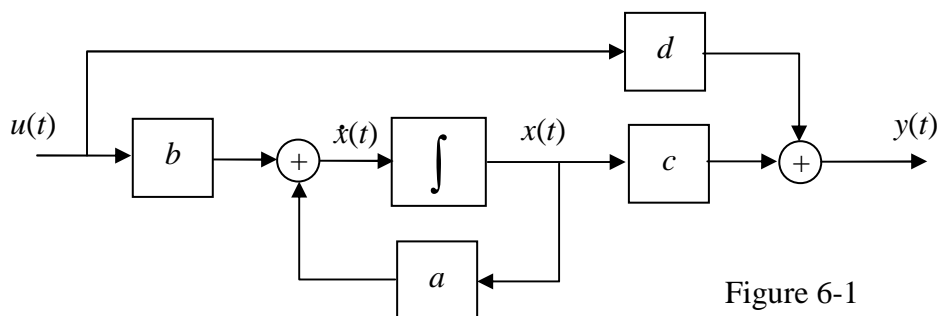


Figure 6-1

From the state equation (1), the system state $x(t)$ for $t \geq 0$, starting from the initial time $t=0$, can be obtained as

$$x(t) = e^{at} x_0 + \int_0^t e^{a(t-\tau)} bu(\tau) d\tau \quad (6-3)$$

and then the output equals to

$$y(t) = ce^{at} x_0 + c \int_0^t e^{a(t-\tau)} bu(\tau) d\tau + du(t) \quad (6-4)$$

which is measurable.

In addition to the model described by (1) and (2), an LTI system could be expressed by a differential equation without the state variable $x(t)$. First, let's calculate the following equation:

$$\begin{aligned}
 \dot{y}(t) - ay(t) &= c\dot{x}(t) + d\dot{u}(t) - a(cx(t) + du(t)) \\
 &= c(\dot{x}(t) - ax(t)) + d\dot{u}(t) - adu(t) \\
 &= cbu(t) + d\dot{u}(t) - adu(t) \\
 &= d\dot{u}(t) + (cb - ad)u(t)
 \end{aligned}
 \tag{6-5}$$

where the term $\dot{x}(t) - ax(t)$ is replaced by $bu(t)$ according to (6-1). Clearly, the system in Figure 6-1 can be changed into a first-order differential equation, called the input-output equation and expressed by

$$\dot{y}(t) + a_0y(t) = b_1\dot{u}(t) + b_0u(t), \quad y(0) = y_0
 \tag{6-6}$$

where $a_0 = -a$, $b_1 = d$, $b_0 = cb - ad$ and $y_0 = cx_0 + du(0)$. It is known that if $b_1 = d \neq 0$ then (6-6) is a proper system and if $b_1 = d = 0$ then it is a strictly proper system, given as

$$\dot{y}(t) + a_0y(t) = b_0u(t), \quad y(0) = y_0
 \tag{6-7}$$

Figure 6-2 shows the block diagram of (6-7) correspondingly.

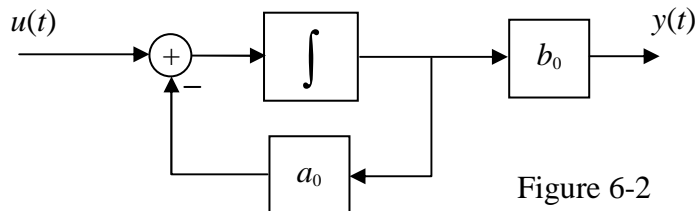


Figure 6-2

Obviously, the state equation and output equation of a first-order strictly proper LTI system is described as

$$\dot{x}(t) = ax(t) + bu(t), \quad x(0) = x_0
 \tag{6-8}$$

$$y(t) = cx(t)
 \tag{6-9}$$

and the block diagram is shown in Figure 6-3. Since most of the systems in engineering are strictly proper, we will focus on this kind of systems from now on.

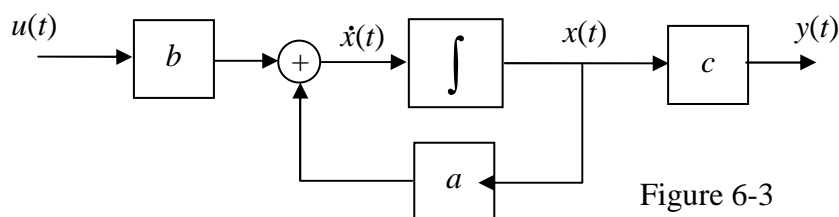


Figure 6-3

B. First-Order Filter: RC Circuit

In engineering, we often face problems related to signal processing, which usually requires a system, called filter, to extract desired signals from the input $u(t)$. Figure-4 shows the simplest low-pass filter implemented by an RC circuit, which only allows signals of low frequency to pass through.

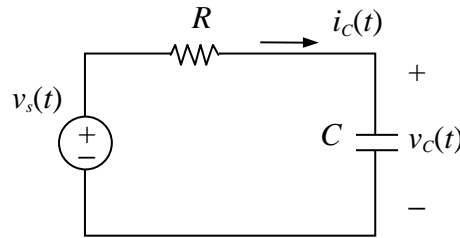


Figure 6-4

Now, let's derive the state equation by choosing the capacitor voltage $v_c(t)$ as the state variable due to its continuity in time domain. According to the Kirchoff's voltage law, we have

$$R i_c(t) + v_c(t) = v_s(t), \quad v_c(0) = v_{c0} \quad (6-10)$$

where $v_c(0) = v_{c0}$ is the initial voltage of the capacitor. The current through a capacitor is related to the voltage across it as below:

$$i_c(t) = C \dot{v}_c(t) \quad (6-11)$$

By substituting (6-11) into (6-10), we have

$$\dot{v}_c(t) = -\frac{1}{RC} v_c(t) + \frac{1}{RC} v_s(t), \quad v_c(0) = v_{c0} \quad (6-12)$$

Let the state and input be $x(t) = v_c(t)$ and $u(t) = v_s(t)$, then (6-12) is rewritten as

$$\dot{x}(t) = ax(t) + bu(t), \quad x(0) = x_0 = v_{c0} \quad (6-13)$$

where $a = -\frac{1}{RC}$ and $b = \frac{1}{RC}$. To be used as a low-pass filter, the capacitor voltage is selected as the output, i.e.,

$$y(t) = v_c(t) = x(t) \quad (6-14)$$

which is equal to the state variable. Hence, from (6-13) we can write its input-output equation of the RC circuit as below:

$$\dot{y}(t) + a_0 y(t) = b_0 u(t), \quad y(0) = y_0 = v_{c0} \quad (6-15)$$

where $a_0 = -\frac{1}{RC}$ and $b_0 = \frac{1}{RC}$. From (6-3), we have

$$\begin{aligned}
 y(t) = x(t) &= e^{-a_0 t} v_{C0} + \int_0^t e^{-a_0(t-\tau)} b_0 u(\tau) d\tau \\
 &= e^{-\frac{1}{RC}t} v_{C0} + \frac{1}{RC} \int_0^t e^{-\frac{1}{RC}(t-\tau)} u(\tau) d\tau
 \end{aligned}
 \tag{6-16}$$

where the function $e^{-\frac{1}{RC}t}$ is shown in Figure 6-5 and $T=RC$ is called the time constant. Obviously, if the time t increases by one time constant T , then the function decreases in a ratio of $e^{-1}=0.3679$. Moreover, the larger the time constant T is, the slower the function decreases. Note that $e^{-\frac{1}{RC}t} \rightarrow 0$ as $t \rightarrow \infty$. Therefore, when the time increases, the output (6-16) will be gradually approximated as below:

$$y(t) = x(t) \approx \frac{1}{RC} \int_0^t e^{-\frac{1}{RC}(t-\tau)} u(\tau) d\tau
 \tag{6-17}$$

which depends on the input $u(t)$ only. As a result, the initial condition $y_0=v_{C0}$ is usually neglected in filter design. Next, let's check the frequency response of the RC circuit by the use of sinusoidal input $u(t)=\cos \omega t$.

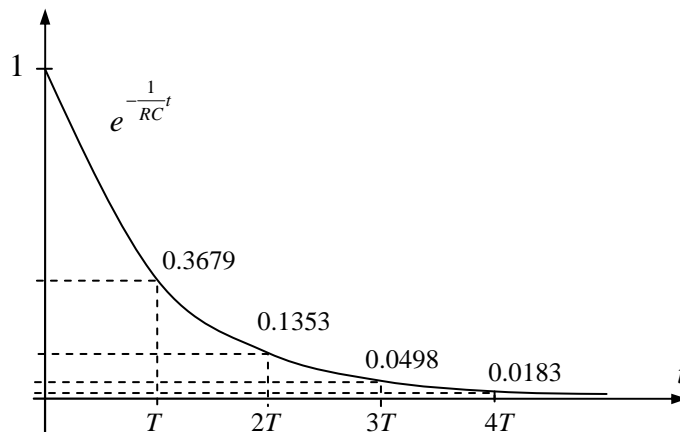


Figure 6-5

One important tool of frequency response is the Laplace transform. Let $U(s)$ and $Y(s)$ be the Laplace transform of $u(t)$ and $y(t)$, then (6-15) can be transformed as

$$sY(s) + a_0 Y(s) = b_0 U(s)
 \tag{6-18}$$

i.e.,

$$Y(s) = \frac{b_0}{s + a_0} U(s) = H(s)U(s)
 \tag{6-19}$$

where $H(s) = \frac{b_0}{s + a_0}$ is called the transfer function. If s is replaced by $j\omega$, then

$$H(s)\Big|_{s=j\omega} = H(j\omega) = |H(j\omega)|e^{-j\angle H(j\omega)} \quad (6-20)$$

where the magnitude of $H(j\omega)$ is

$$|H(j\omega)| = \left| \frac{b_0}{j\omega + a_0} \right| = \left| \frac{1}{j\omega RC + 1} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad (6-21)$$

and the phase is

$$\angle H(j\omega) = -\tan^{-1}(\omega RC) \quad (6-22)$$

It is well known that if the input is $u(t) = \cos \omega t$, then its output is

$$y(t) = |H(j\omega)| \cos(\omega t + \angle H(j\omega)) \quad (6-23)$$

which implies the output possesses the same frequency ω as the input signal, but its magnitude and phase are changed by $|H(j\omega)|$ and $\angle H(j\omega)$, shown in Figure 6-6.

From (6-21), $|H(j\omega)|$ is decreased as the frequency ω is increased. Besides, when

$\omega = \omega_c = \frac{1}{RC}$, we have

$$|H(j\omega_c)| = \frac{1}{\sqrt{1 + (\omega_c RC)^2}} = \frac{1}{\sqrt{2}} \quad (6-24)$$

$$\angle H(j\omega_c) = -\tan^{-1}(\omega_c RC) = -45^\circ \quad (6-25)$$

and then

$$y(t) = |H(j\omega_c)| \cos(\omega t + \angle H(j\omega_c)) = \frac{1}{\sqrt{2}} \cos(\omega t - 45^\circ) \quad (6-26)$$

which implies the signal's power, in a form concerning $y^2(t)$, at $\omega = \omega_c$ is reduced to one half. Hence, $\omega = \omega_c$ is called the half power frequency or the cutoff frequency.

To sum up, an input $u(t) = \cos \omega t$ with lower frequency ω will generate an output with larger magnitude $|H(j\omega)|$. In other words, the filter $H(s) = \frac{b_0}{s + a_0}$ acts as a low-pass

filter since it allows input signals of lower frequency to pass through easier.

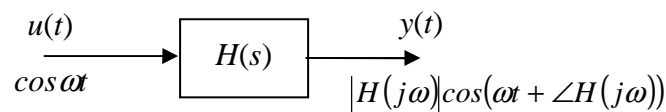


Figure 6-6

Let's take a numerical example to demonstrate the feature of the RC filter in

Figure 6-4, where $R=1k\Omega$, $C=10\mu F$ and the initial capacitor voltage is 1V. From (6-12), we write the input-output equation as below:

$$\dot{v}_C(t) = -100v_C(t) + 100v_s(t), \quad v_C(0)=1 \quad (6-26)$$

What are the output responses for $u(t)=\cos\omega t$, where $\omega=1, 10, 100$ and 1000 ? The numerical answer is obtained by MATLAB and given as below:


```
=====
Create m-file: RC1.m
function dy=RC1(t,y)
dy=-100*y+100*cos(t);

Create m-file: RC2.m
function dy=RC2(t,y)
dy=-100*y+100*cos(10*t);


Create m-file: RC3.m
function dy=RC3(t,y)
dy=-100*y+100*cos(100*t);

Create m-file: RC4.m
function dy=RC4(t,y)
dy=-100*y+100*cos(1000*t);
```
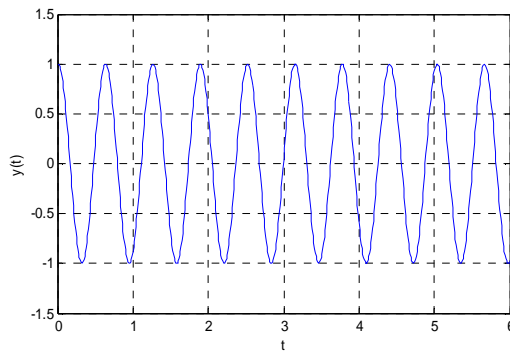
```
>> % key in the following instructions
>> [t,y]=ode23(@RC1,[0:0.01:6],1.0)
>> plot(t,y); xlabel('t'); ylabel('y(t)')
```



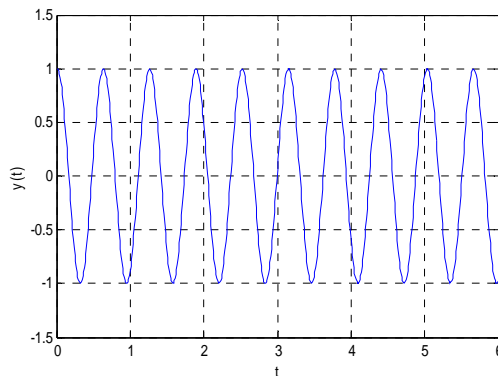
```
>> % key in the following instructions
>> [t,y]=ode23(@RC2,[0:0.01:6],1)
>> plot(t,y); xlabel('t'); ylabel('y(t)')
```




```
>> % key in the following instructions
```
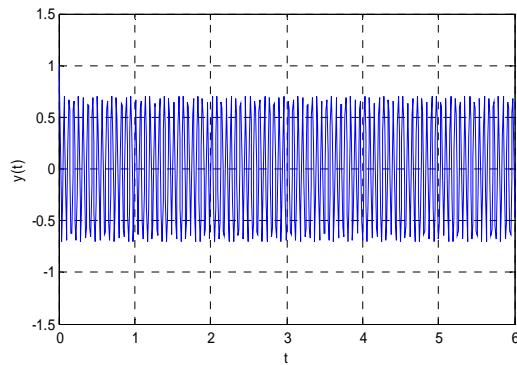
```
>> [t,y]=ode23(@RC3,[0:0.01:6],1)
>> plot(t,y); xlabel('t'); ylabel('y(t)')
```


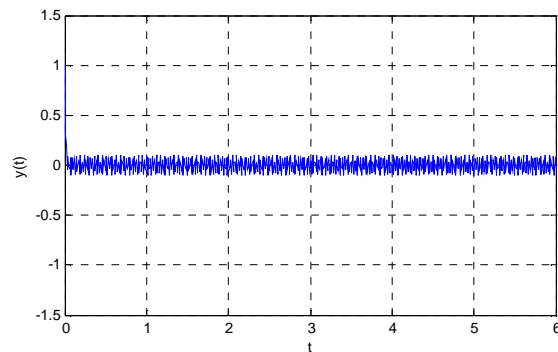
```
>> % key in the following instructions
>> [t,y]=ode23(@RC4,[0:0.01:6],1)
>> plot(t,y); xlabel('t'); ylabel('y(t)')
```



=====

The numerical result shows that the RC circuit indeed act as a low-pass filter since the magnitude of output is decreased as the input frequency ω is increased.

Problems

- P.6-1 If the RC filter in Figure 6-4 contains $R=16k\Omega$, $C=40\mu F$ and neglect the initial capacitor voltage. What is the cutoff frequency ω_c and what are the output responses for $u(t)=\cos\omega t$ for $\omega=0.1\omega_c$, ω_c , $10\omega_c$ and $100\omega_c$?
- P.6-2 Replace the capacitor in Figure 6-4 by an inductor L . If $R=16k\Omega$, $L=10mH$ and neglect the initial condition, then what is the cutoff frequency ω_c and what are the output responses for $u(t)=\cos\omega t$ for $\omega=0.1\omega_c$, ω_c , $10\omega_c$ and $100\omega_c$?