

9. Second-Order Filter Design

In engineering, a filter is often used to acquire or reject signals of special frequency domain. There are three fundamental types of filters, called low-pass, high-pass and band-pass filters. Let's employ a second order LTI system for filter design, which is expressed by the following input-output equation

$$\ddot{y}(t) + a_1 \dot{y}(t) + a_0 y(t) = b_2 \ddot{u}(t) + b_1 \dot{u}(t) + b_0 u(t) \quad (1)$$

where $a_1 > 0$ and $a_0 > 0$. Taking The Laplace transform, we have the transfer function as

$$H(s) = \frac{Y(s)}{U(s)} = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0} \quad (2)$$

where $U(s)$ and $Y(s)$ are the Laplace transforms of the input $u(t)$ and output $y(t)$.

Assign s_1 and s_2 , located on the left-half complex plane due to $a_1 > 0$ and $a_0 > 0$, as the roots of the characteristic equation, then

$$s^2 + a_1 s + a_0 = (s - s_1)(s - s_2) = 0 \quad (3)$$

Since both s_1 and s_2 possess negative real part, the system (1) is stable and the effect caused by the initial conditions will vanish as $t \rightarrow \infty$. Therefore, it is not necessary to consider the initial conditions in the filter design.

Commonly, there are three fundamental filters concerning the second-order LTI system (1), named low-pass, high-pass and band-pass filters. The low-pass filter is of the form

$$\ddot{y}_{LP}(t) + a_1 \dot{y}_{LP}(t) + a_0 y_{LP}(t) = b_0 u(t) \quad (4)$$

where $b_0 = k_0 a_0$ and $k_0 > 0$ is the gain. The resulted transfer function is

$$H_{LP}(s) = \frac{Y_{LP}(s)}{U(s)} = k_0 \frac{a_0}{s^2 + a_1 s + a_0} \quad (5)$$

Let $s = j\omega$, then

$$H_{LP}(j\omega) = \frac{Y_{LP}(j\omega)}{U(j\omega)} = k_0 \frac{a_0}{(j\omega)^2 + a_1(j\omega) + a_0} \quad (6)$$

which implies

$$H_{LP}(j\omega) \approx k_0 \angle 0^\circ \quad \text{as } \omega \rightarrow 0 \quad (7)$$

$$H_{LP}(j\omega) \approx 0 \angle -180^\circ \quad \text{as } \omega \rightarrow \infty \quad (8)$$

Clearly, if the input is a sinusoidal signal given as

$$u(t) = A \cos(\omega t + \theta) \quad (9)$$

with magnitude A and phase θ , then its output is

$$y_{LP}(t) = A |H_{LP}(j\omega)| \cos(\omega t + \theta + \angle H_{LP}(j\omega)) \quad (10)$$

with magnitude changed by the gain $|H_{LP}(j\omega)|$ and phase shifted by $\angle H_{LP}(j\omega)$.

Moreover, from (7) and (8) we have

$$y_{LP}(t) \approx A k_0 \cos(\omega t + \theta) \quad \text{as } \omega \rightarrow 0 \quad (11)$$

$$y_{LP}(t) \approx 0 \cdot \cos(\omega t + \theta - 180^\circ) \quad \text{as } \omega \rightarrow \infty \quad (12)$$

i.e., the low-pass filter rejects inputs of high frequency and allows low-frequency inputs to pass through.

In a certain cases, if we need a system to receive high-frequency inputs and reject those of low frequency, then the following high-pass filter can reach the goal:

$$\ddot{y}_{HP}(t) + a_1 \dot{y}_{HP}(t) + a_0 y_{HP}(t) = b_2 \ddot{u}(t) \quad (13)$$

where $b_2 = k_2 > 0$ is the gain. The transfer function is

$$H_{HP}(s) = \frac{Y_{HP}(s)}{U(s)} = k_2 \frac{s^2}{s^2 + a_1 s + a_0} \quad (14)$$

Hence,

$$H_{HP}(j\omega) = \frac{Y_{HP}(j\omega)}{U(j\omega)} = k_2 \frac{(j\omega)^2}{(j\omega)^2 + a_1(j\omega) + a_0} \quad (15)$$

which implies

$$H_{HP}(j\omega) \approx 0 \angle 180^\circ \quad \text{as } \omega \rightarrow 0 \quad (16)$$

$$H_{HP}(j\omega) \approx k_2 \angle 0^\circ \quad \text{as } \omega \rightarrow \infty \quad (17)$$

The sinusoidal input (9) will generate the following output

$$y_{HP}(t) = A |H_{HP}(j\omega)| \cos(\omega t + \theta + \angle H_{HP}(j\omega)) \quad (18)$$

Similarly, we have

$$y_{HP}(t) \approx 0 \cdot \cos(\omega t + \theta + 180^\circ) \quad \text{as } \omega \rightarrow 0 \quad (19)$$

$$y_{HP}(t) \approx A k_2 \cos(\omega t + \theta) \quad \text{as } \omega \rightarrow \infty \quad (20)$$

i.e., the high-pass filter (13) rejects low-frequency inputs, but allows high-frequency inputs to pass through.

If both the low-frequency and high-frequency inputs are unwanted, then a

band-pass filter is required to achieve the objective, constructed as the following form:

$$\ddot{y}_{BP}(t) + a_1 \dot{y}_{BP}(t) + a_0 y_{BP}(t) = b_1 \dot{u}(t) \quad (21)$$

where $b_1 = k_1 a_1$ and $k_1 > 0$ is the gain. The transfer function is

$$H_{BP}(s) = \frac{Y_{BP}(s)}{U(s)} = k_1 \frac{a_1 s}{s^2 + a_1 s + a_0} \quad (22)$$

Therefore,

$$H_{BP}(j\omega) = \frac{Y_{BP}(j\omega)}{U(j\omega)} = k_1 \frac{a_1(j\omega)}{(j\omega)^2 + a_1(j\omega) + a_0} \quad (23)$$

which implies

$$H_{BP}(j\omega) \approx 0 \angle 90^\circ \quad \text{as } \omega \rightarrow 0 \quad (24)$$

$$H_{BP}(j\omega) = k_1 \angle 0^\circ \quad \text{at } \omega = \sqrt{a_0} \quad (25)$$

$$H_{BP}(j\omega) \approx 0 \angle -90^\circ \quad \text{as } \omega \rightarrow \infty \quad (26)$$

With the use of sinusoidal input (9), the output is

$$y_{BP}(t) = A |H_{BP}(j\omega)| \cos(\omega t + \theta + \angle H_{BP}(j\omega)) \quad (27)$$

which leads to

$$y_{BP}(t) \approx 0 \cdot \cos(\omega t + \theta + 90^\circ) \quad \text{as } \omega \rightarrow 0 \quad (28)$$

$$y_{BP}(t) \approx A k_1 \cos(\omega t + \theta) \quad \text{at } \omega = \sqrt{a_0} \quad (29)$$

$$y_{BP}(t) \approx 0 \cdot \cos(\omega t + \theta - 90^\circ) \quad \text{as } \omega \rightarrow \infty \quad (30)$$

Clearly, the band-pass filter rejects both the low-frequency and high-frequency inputs.

To implement the above 2nd order filters, we adopt a basic system with the state equation described as below:

$$\dot{x}_1(t) = x_2(t) \quad (31)$$

$$\dot{x}_2(t) = -a_0 x_1(t) - a_1 x_2(t) + u(t) \quad (32)$$

If the output is $y_{LP}(t) = b_0 x_1(t)$ where $b_0 = k_0 a_0$, then the input-output equation can be obtained as

$$\ddot{y}_{LP}(t) + a_1 \dot{y}_{LP}(t) + a_0 y_{LP}(t) = b_0 u(t) \quad (33)$$

Clearly, it is a low-pass filter with the same expression as (4).

If the output is chosen as $y_{HP}(t) = b_2 \dot{x}_2(t) = k_2 (u(t) - a_0 x_1(t) - a_1 x_2(t))$, where $b_2 = k_2$, then the input-output equation can be obtained as

$$\ddot{y}_{HP}(t) + a_1 \dot{y}_{HP}(t) + a_0 y_{HP}(t) = b_2 \ddot{u}(t) \quad (34)$$

Clearly, it is a high-pass filter with the same expression as (13).

If the output is chosen as $y_{BP}(t) = b_1 x_2(t)$ where $b_1 = k_1 a_1$, then the input-output equation can be obtained as

$$\ddot{y}_{BP}(t) + a_1 \dot{y}_{BP}(t) + a_0 y_{BP}(t) = b_1 \ddot{u}(t) \quad (35)$$

Clearly, it is a band-pass filter with the same expression as (21). Figure-1 shows the basic system described by (31) and (32) and the outputs $y_{LP}(t)$, $y_{HP}(t)$ and $y_{BP}(t)$ for low-pass, high-pass and band-pass filters.

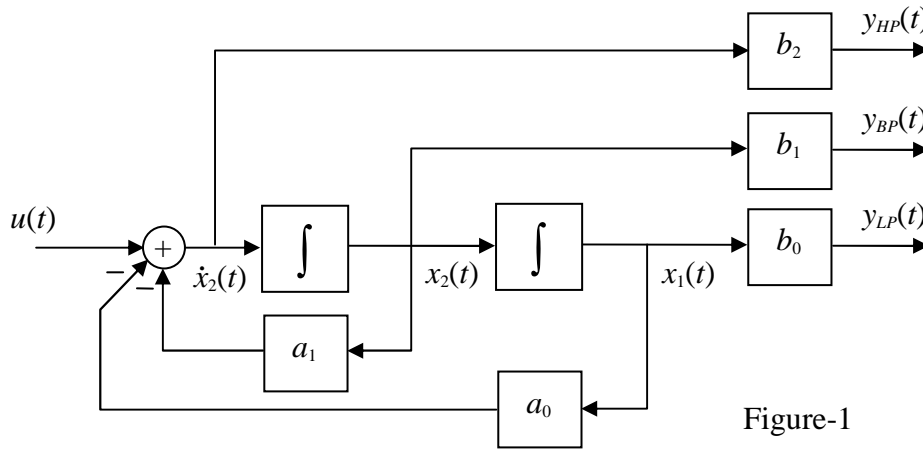


Figure-1

For numerical demonstration, we choose $s_1 = -10$ and $s_2 = -100$ for the filters discussed below. The resulted transfer function is

$$H(s) = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + 110s + 1000} = \frac{b_2 s^2 + b_1 s + b_0}{(s + 10)(s + 100)} \quad (36)$$

Let the coefficients be $b_2 = 0$, $b_1 = 0$ and $b_0 = 1000$, then (36) is a low-pass filter of the following form

$$H(j\omega) = \frac{1000}{(j\omega + 10)(j\omega + 100)} = \frac{1}{\left(1 + j\frac{\omega}{10}\right)\left(1 + j\frac{\omega}{100}\right)} \quad (37)$$

Clearly, the magnitude $|H(j\omega)|$ decreases monotonically as ω increases. Besides, the maximum magnitude is $|H(j\omega)| = 1$ at $\omega = 0$ and $|H(j\omega)| \rightarrow 0$, as $\omega \rightarrow \infty$.

If the coefficients are $b_2 = 1$, $b_1 = 0$ and $b_0 = 0$, then (36) is a high-pass filter of the

following form

$$H(j\omega) = \frac{(j\omega)^2}{(j\omega+10)(j\omega+100)} = \frac{1}{\left(1 - j\frac{10}{\omega}\right)\left(1 - j\frac{100}{\omega}\right)} \quad (38)$$

where the maximum magnitude $|H(j\omega)|=1$ exists at $\omega \rightarrow \infty$. Besides, the magnitude $|H(j\omega)|$ increases monotonically as ω increases and $|H(j\omega)| \rightarrow 0$, as $\omega \rightarrow 0$.

If the coefficients are $b_2=0$, $b_1=110$ and $b_0=0$, then (36) is a band-pass filter of the following form

$$\begin{aligned} H(j\omega) &= \frac{110j\omega}{(j\omega)^2 + 110j\omega + 1000} \\ &= \frac{1}{1 + j\frac{\sqrt{1000}}{110}\left(\frac{\omega}{\sqrt{1000}} - \frac{\sqrt{1000}}{\omega}\right)} \end{aligned} \quad (39)$$

where the maximum magnitude $|H(j\omega)|=1$ at $\omega = \sqrt{1000}$. For $\omega < \sqrt{1000}$, the magnitude $|H(j\omega)|$ increases monotonically as ω increases. For $\omega > \sqrt{1000}$, the magnitude $|H(j\omega)|$ decreases monotonically as ω increases.

The Bode plots of these three filters can be obtained by the use of MATLAB, which are shown as below:

```
=====
>>% Create transfer function
>>numlp=[0 0 1000]; numhp=[1 0 0]; numbp=[0 110 0]; den=[1 110 1000];
>>lpf=tf(numlp,den)

Transfer function:
      1000
-----
s^2 + 110 s + 1000

>>hpf=tf(numhp,den)

Transfer function:
      s^2
-----
s^2 + 110 s + 1000


>>bpf=tf(numbp,den)

Transfer function:
```

```

110s
-----
s^2 + 110 s + 1000

>>bode(lpf,hpf,bpf);grid
    
```

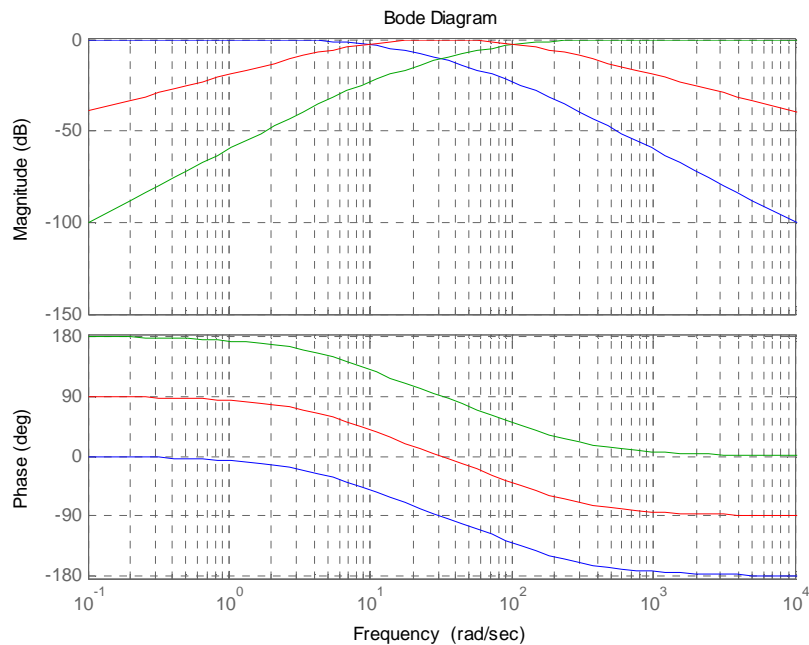

To show the property of these filters, let the input be a signal composed of three frequencies, expressed as

$$u(t) = \cos(t) + \cos(\sqrt{1000}t) + \cos(1000t) \quad (40)$$


where $\omega=1$ rad/sec is the low-frequency signal, $\omega=1000$ rad/sec is the high-frequency signal and $\omega=\sqrt{1000}$ is of the middle frequency. The outputs $y_{LP}(t)$, $y_{HP}(t)$ and $y_{BP}(t)$ are obtained by the use of MABLAB.

```


=====
Create m-file: second.m
function dx=second(t,x)
dx=zeros(2,1);
dx(1)=x(2);
dx(2)=-1000*x(1)-110*x(2)+cos(t)+cos(sqrt(1000)*t)+cos(1000*t);

>> % key in the following instructions
>> [t,x]=ode45(@second,[0:0.001:8],[0 0])
>> for k=1:8001
    tk=0.001*(k-1);
    ylp(k)=1000*x(k,1);
    ybp(k)=110*x(k,2);
    
```

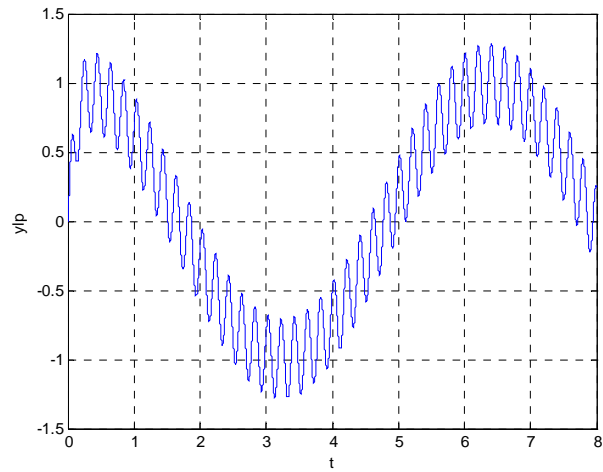
```
u(k)=cos(tk)+ cos(sqrt(1000)*tk)+cos(1000*tk) ;  
yhp(k)=u(k)-ylp(k)-ybp(k) ;  
end  
>> plot(t,ylp(:)); xlabel('t'); ylabel('ylp'); grid
```


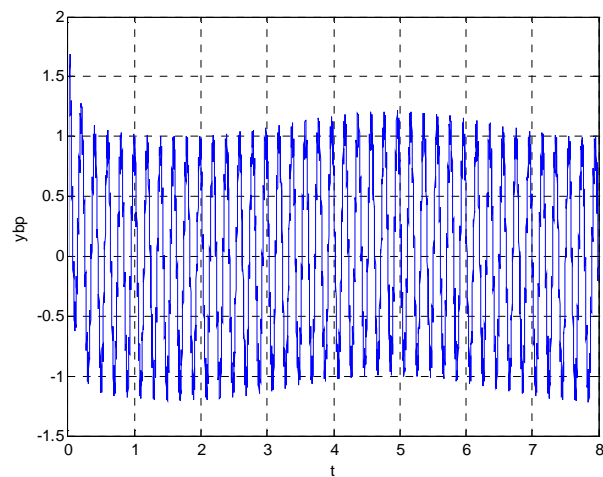
```
>> plot(t,ybp(:)); xlabel('t'); ylabel('ybp'); grid
```


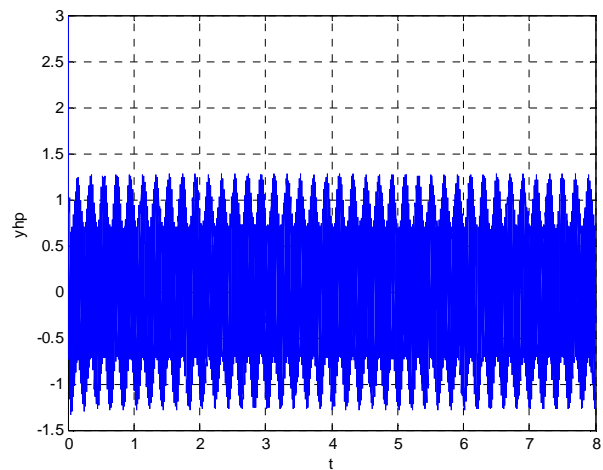
```
>> plot(t,yhp(:)); xlabel('t'); ylabel('yhp'); grid
```



=====

P.1 Consider the following filter with transfer function as below:

$$H(s) = \frac{100s + 1000}{s^2 + 100s + 5000}$$

Draw the Bode plot and determine the frequency ω_1 at which the magnitude $|H(j\omega_1)|$ is maximal. If the input is $u(t) = \cos(10\omega_1 t)$, what is the output $y(t)$?

10. Implementation of Second-Order Filters

In general, a filter can be implemented by electrical elements, such as resistors, capacitors and inductors. For example, an RLC circuit in Figure-1 is constructed to realize a low-pass filter where $v_s(t)$ is the input voltage and $v_L(t)$ is the output voltage to the payload resistance R_L . Its input-output equation is described as

$$\ddot{v}_L(t) + \left(\frac{R}{L} + \frac{1}{R_L L} \right) \dot{v}_L(t) + \frac{R_L + R}{R_L LC} v_L(t) = \frac{1}{LC} v_s(t) \quad (1)$$

and the transfer function is

$$H(s) = \frac{V_L(s)}{V_s(s)} = k_0 \frac{a_0}{s^2 + a_1 s + a_0} \quad (2)$$

where $a_1 = \frac{R}{L} + \frac{1}{R_L L}$, $a_0 = \frac{R_L + R}{R_L LC}$ and $k_0 = \frac{R_L}{R_L + R}$. Although a low-pass filter

can be easily implemented by an RLC circuit, there exists a serious problem concerning about the payload effect, i.e., the transfer function varies as the payload R_L changes. To avoid such undesired problem, a circuit including operational amplifiers, or Op-Amp in short, is often adopted as a substitute.

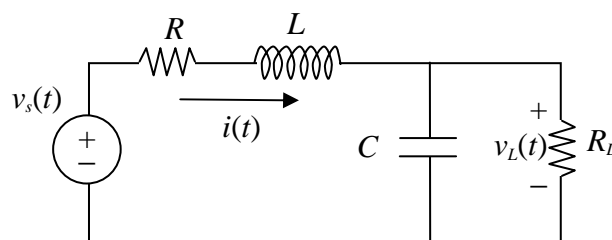


Figure-1

Let's employ Figure-2 as an example of a low-pass filter which is implemented by a circuit with an ideal Op-Amp. First, let's derive its transfer function. Since the current and voltage input to the Op-Amp are negligible, the node voltage $v_2(t) \approx 0$ is often considered to connect a virtual ground and both the currents passing through R_2 and C_2 are the same and denoted as $i(t)$. Therefore, we have

$$\frac{V_1(s)}{R_2} = -V_L(s)(sC_2) \quad (3)$$

where $V_1(s)$ and $V_L(s)$ are the Laplace transforms of $v_1(t)$ and $v_L(t)$. Moreover, based on the Kirchoff's current law we obtain

$$\frac{V_1(s) - V_s(s)}{R_1} + V_1(s)(sC_1) + \frac{V_1(s)}{R_2} + \frac{V_1(s) - V_L(s)}{R_3} = 0 \quad (4)$$

where $V_s(s)$ are the Laplace transforms of $v_s(t)$. Substituting (3) into (4) leads to

$$\left(s^2 R_2 C_1 C_2 + s R_2 C_2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + \frac{1}{R_3} \right) V_L(s) = -\frac{V_s(s)}{R_1} \quad (5)$$

which implies the transfer function is

$$H(s) = \frac{V_L(s)}{V_s(s)} = k_0 \frac{a_0}{s^2 + a_1 s + a_0} \quad (6)$$

where $a_1 = \frac{1}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$, $a_0 = \frac{1}{R_3 R_2 C_1 C_2}$ and $k_0 = -\frac{R_3}{R_1}$. As a consequence,

$H(s)$ is not affected by the payload resistance, but the gain k_0 is negative different from the case in (2). To change the numerical sign, an extra Op-Amp circuit is attached in

Figure-3, which is then changed into a low-pass filter with a positive gain $k_0 = \frac{R_3}{R_1}$

in (6).

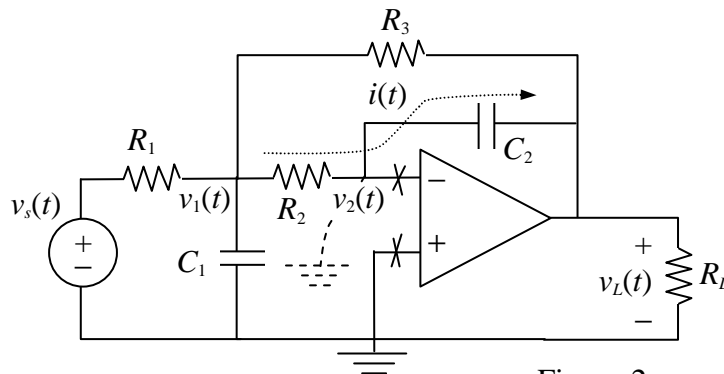


Figure-2

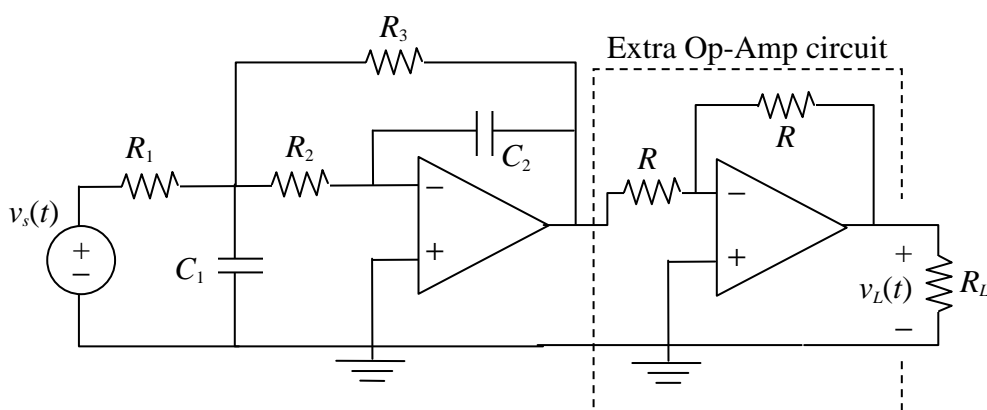


Figure-3

Next, let's first focus on the implementation of the 2nd order filter with transfer function expressed by

$$H(s) = \frac{1}{s^2 + a_1s + a_0} \quad (7)$$

where $a_1 > 0$ and $a_0 > 0$. Mathematically, it can be realized by the following state equation

$$\dot{x}_1(t) = x_2(t) \quad (8)$$

$$\dot{x}_2(t) = -a_0x_1(t) - a_1x_2(t) \quad (9)$$

and the output equation is

$$y(t) = x_1(t) \quad (10)$$

From (8), we have

$$x_1(t) = \int_0^t x_2(\tau) d\tau \quad (11)$$

which implies an integrator is needed. In practice, the integrator is constructed by the Op-Amp circuit shown in Figure-4, described as

$$x_1(t) = -\int_0^t x_2(\tau) d\tau \quad (12)$$

which is different from (11). In order to simplify the implementation, we purposely change the state equation (8) and (9) into

$$\dot{x}_1(t) = -x_2(t) \quad (13)$$

$$-\dot{x}_2(t) = -a_0x_1(t) + a_1x_2(t) + u(t) \quad (14)$$

and take the same output $y(t) = x_1(t)$ in (10). Correspondingly, Figure-5 shows its block diagram.

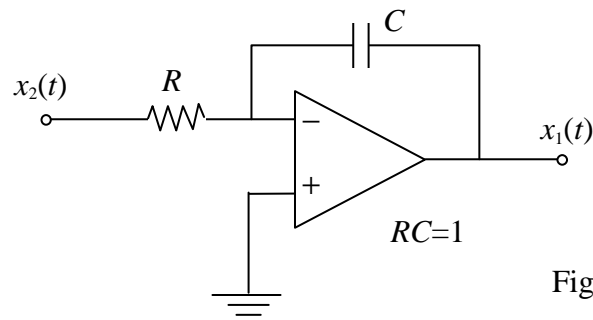


Figure-4

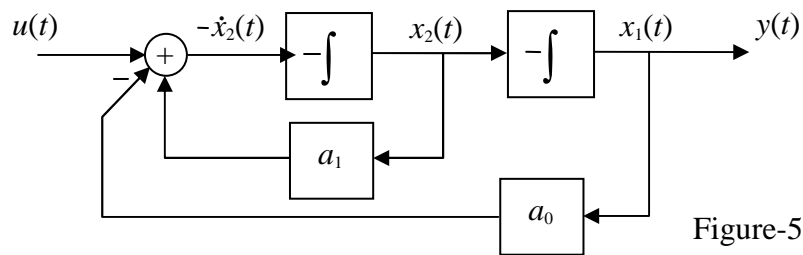


Figure-5

Viewing from Figure-5, it is clear that we still need to implement the inverter and adder, respectively shown in Figure-6 and Figure-7. Further rearranging (14) yields

$$-\dot{x}_2(t) = -[a_0 x_1(t) + (-[a_1 x_2(t) + u(t)])] \quad (15)$$

Figure-8 shows the block diagram correspondingly. Hence, the filter (7) can be implemented by the circuit with Op-Amps shown in Figure-9.

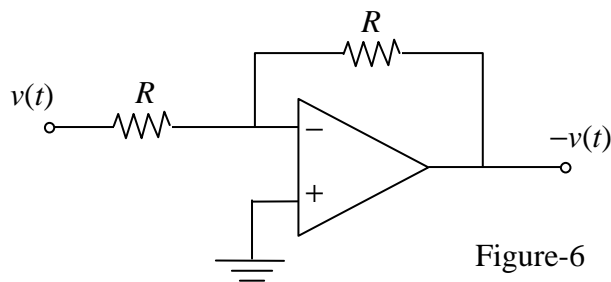


Figure-6

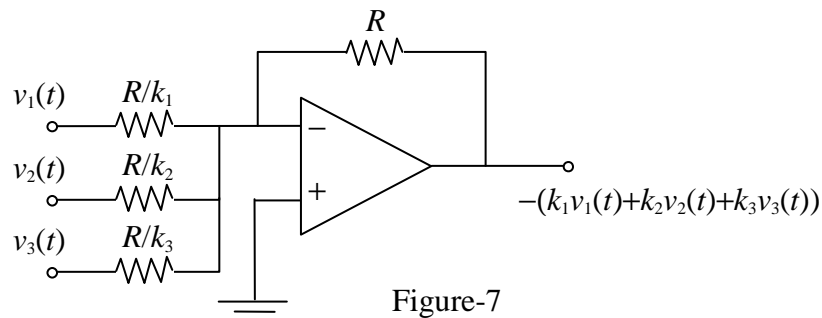


Figure-7

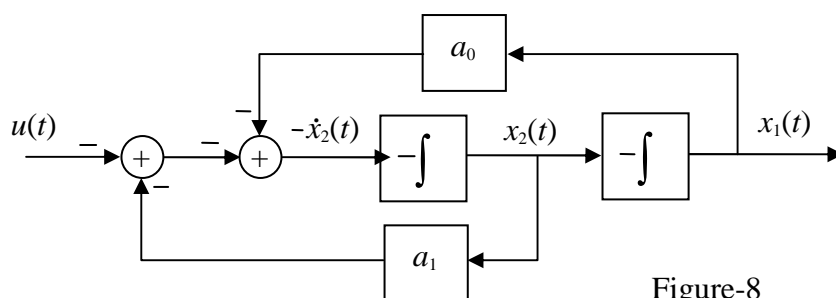


Figure-8

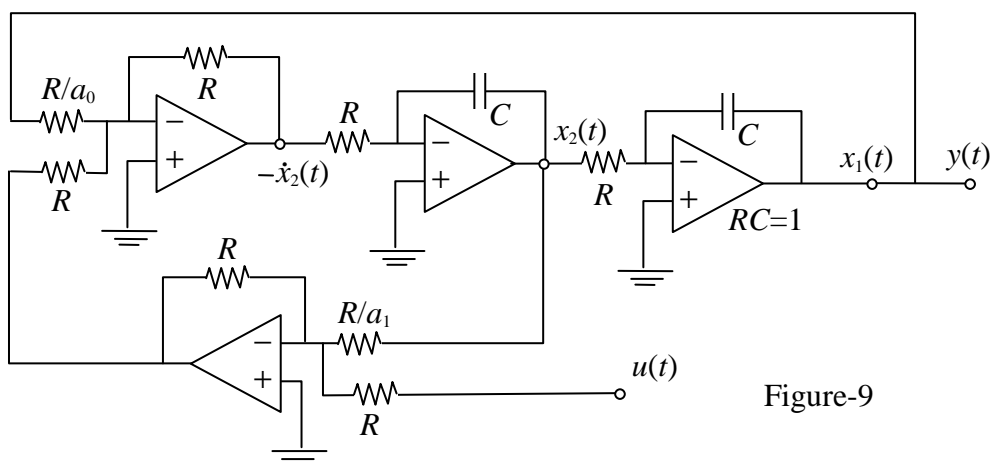


Figure-9

Based on Figure-9, we can implement the low-pass filter, band-pass filter and high-pass filter, respectively expressed as below:

$$H(s) = k_0 \frac{a_0}{s^2 + a_1s + a_0} \quad (16)$$

$$H(s) = k_1 \frac{a_1s}{s^2 + a_1s + a_0} \quad (17)$$

$$H(s) = k_2 \frac{s^2}{s^2 + a_1s + a_0} \quad (18)$$

Here, we will leave them as homework to draw their circuits with Op-Amps.

P.1 Implement the low-pass filter (16), band-pass filter (17) and high-pass filter (18) by the use of circuits with Op-Amps.