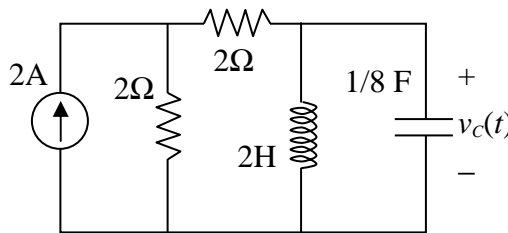


To solve the following circuits, you can use all the methods you learned in this course.

1. (15%) Consider the circuit on the right, where the initial capacitor voltage is $v_C(0) = 1$ V and the initial inductor current is $i_L(0) = -1$ A. What is the capacitor voltage $v_C(t)$ for $t \geq 0$?



Sol:

The circuit can be transformed into Norton equivalent circuit on the right.


Based on KCL, we have

$$\frac{v_C(t)}{4} + i_L(t) + \frac{1}{8} \dot{v}_C(t) = 1$$

Differentiating it yields

$$\frac{\dot{v}_C(t)}{4} + \frac{di_L(t)}{dt} + \frac{1}{8} \ddot{v}_C(t) = 0$$

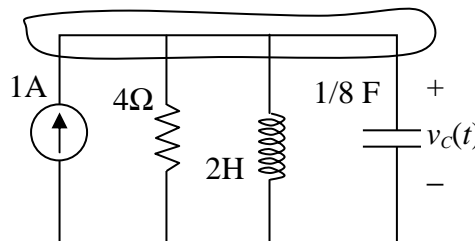where $\frac{di_L(t)}{dt} = \frac{1}{2} \dot{v}_L(t) = \frac{1}{2} \dot{v}_C(t)$.



Hence, $\ddot{v}_C(t) + 2\dot{v}_C(t) + 4v_C(t) = 0$ whose characteristic equation is $\lambda^2 + 2\lambda + 4 = 0$.


Then, the eigenvalues are $\lambda = -1 \pm j\sqrt{3}$. Therefore, $v_C(t) = e^{-t}(A_1 \cos \sqrt{3}t + A_2 \sin \sqrt{3}t)$

and $\dot{v}_C(t) = -e^{-t}(A_1 \cos \sqrt{3}t + A_2 \sin \sqrt{3}t) + e^{-t}\sqrt{3}(-A_1 \sin \sqrt{3}t + A_2 \cos \sqrt{3}t)$.

Since, $v_C(0) = 1 = A_1$ and $\dot{v}_C(0) = 8 - (2v_C(0) + 8i_L(0)) = 14 = -A_1 + \sqrt{3}A_2$, we have

$A_1 = 1$ and $A_2 = 5\sqrt{3}$, i.e., $v_C(t) = e^{-t}(\cos \sqrt{3}t + 5\sqrt{3} \sin \sqrt{3}t)$ V

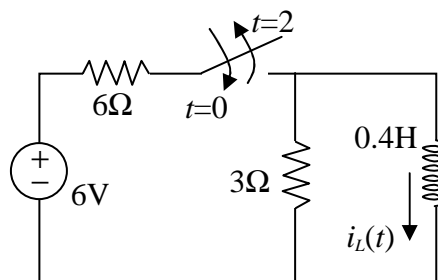
2. (15%) Consider the RL circuit on the right, whose switch has been opened for a long time before $t=0$. If the switch is closed at $t=0$ and then opened again at $t=2$, please solve $i_L(t)$ for $0 < t < \infty$?



Sol:

At $t=0$, we have $i_L(0)=0$.

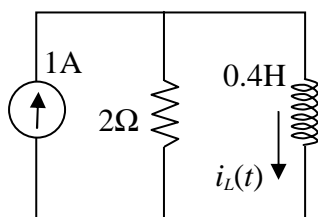For $0 < t < 2$, the Norton equivalent circuit is shown below and described by




$$\frac{0.4}{2} \frac{di_L(t)}{dt} + i_L(t) = 1$$

i.e., $\frac{di_L(t)}{dt} + 5i_L(t) = 5$.

We have $i_L(t) = -e^{-5t} + 1$.

At $t=2$, we have $i_L(2) = -e^{-10} + 1$.

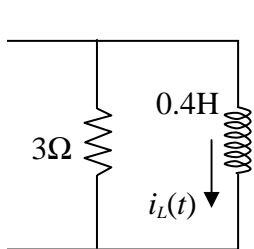For $t > 2$, the Norton equivalent circuit is shown below and described by



$$\frac{0.4}{3} \frac{di_L(t)}{dt} + i_L(t) = 0$$

i.e., $\frac{di_L(t)}{dt} + 7.5i_L(t) = 0$.

We have $i_L(t) = (1 - e^{-10})e^{-5(t-2)}$.

Hence, the inductor current is

$$i_L(t) = \begin{cases} -e^{-5t} + 1 & 0 < t \leq 2 \\ (1 - e^{-10})e^{-5(t-2)} & 2 < t < \infty \end{cases}$$

3. (10%) Find the Laplace transforms $H_i(s)$ of the following functions $h_i(t)$:

$$h_1(t) = e^{-2t}(\sin 3t - 2), \quad h_2(t) = t^2 \cdot \sin 3t$$

Sol:

$$H_1(s) = \frac{3}{(s+2)^2 + 9} - \frac{2}{s+2} = \frac{3(s+2) - 2(s^2 + 4s + 13)}{(s^2 + 4s + 13)(s+2)} = \frac{-2s^2 - 5s - 20}{s^3 + 6s^2 + 21s + 26}$$

$$H_2(s) = \frac{d^2}{ds^2} \left(\frac{3}{s^2 + 9} \right) = \frac{18s^2 - 54}{(s^2 + 9)^3}$$

4. (10%) Find the functions $h_i(t)$ and $h_i(\infty)$ from the following Laplace transforms $H_i(s)$:

$$H_1(s) = \frac{3}{s(s^2 + 2s + 2)}, \quad H_2(s) = \frac{s-1}{(s+1)(s^2 + 4s + 4)}$$

Sol:

$$H_1(s) = \frac{3}{s(s^2 + 2s + 2)} = \frac{1.5}{s} - \frac{1.5(s+1) + 1.5}{(s+1)^2 + 1}$$

$\rightarrow h_1(t) = 1.5 - 1.5e^{-t}(\cos t + \sin t)$ and $h_1(\infty) = 1.5$

$$H_2(s) = \frac{s-1}{(s+1)(s^2 + 4s + 4)} = \frac{-2}{s+1} + \frac{2}{s+2} + \frac{3}{(s+2)^2}$$


$\rightarrow h_2(t) = -2e^{-t} + 2e^{-2t} + 3te^{-2t}$ and $h_2(\infty) = 0$.

5. (15%) Given the circuit on the right, the initial

inductor current is $i_L(0) = 2A$ and the

voltage source is $v_s(t) = 5\sin 3t$ V.

What is the voltage $v_2(t)$?

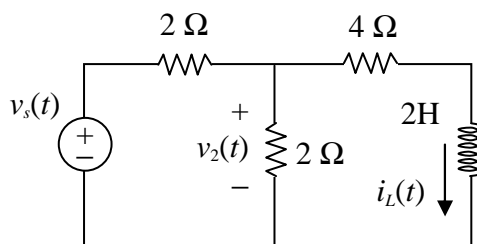


Sol:

The circuit in s-form is on the right.

$$\text{KCL} \textcircled{1}: \frac{V_1 - V_2}{4} + \frac{V_1}{2s} + \frac{2}{s} = 0$$
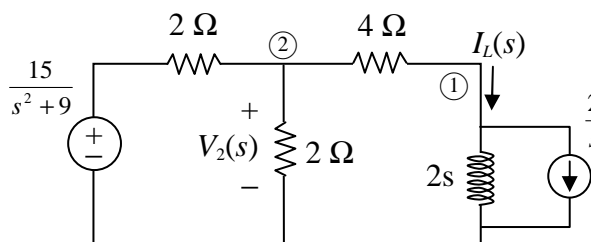
$$\text{KCL} \textcircled{2}: \frac{V_2 - \frac{15}{s^2 + 9}}{2} + \frac{V_2}{2} + \frac{V_2 - V_1}{4} = 0$$



Hence, $V_2(s) = \frac{-2s^2 + 7.5s - 3}{(s^2 + 9)(s + 2.5)} = \frac{-2.246}{s + 2.5} + \frac{0.246s + 3 \times 2.295}{s^2 + 9}$

i.e., $v_2(t) = -2.246e^{-2.5t} + 0.246\cos 3t + 2.295\sin 3t$

6. (15%) The dynamic equation of a circuit can be described as $V_L(s) = H(s)I_s(s)$, where $I_s(s)$ and $V_L(s)$ are the Laplace transforms of input $i_s(t)$ and output $v_L(t)$. Let the transfer function $H(s) = \frac{2s + 1}{s^2 + 5s + 3}$ and the input $i_s(t) = 4\cos(\omega t - 20^\circ)$ A with $\omega = 3$ rad.

(A) What is I_s , the phasor of $i_s(t)$?

(B) If $H(j\omega) = |H(j\omega)|e^{j\theta}$, what are $|H(j\omega)|$ and θ ?

(C) What is the output $v_L(t)$ as $t \rightarrow \infty$?

Sol:

(A) $I_s = 4\angle(-20^\circ) = 4\cos 20^\circ - j4\sin 20^\circ = 3.7588 - j1.3681$

(B) $H(j3) = \frac{j6 + 1}{-9 + j15 + 3} = \frac{1 + j6}{-6 + j15} = 0.3218 - j0.1954 = 0.3765\angle(-31.26^\circ)$

(C) $V_L = 0.3765\angle(-31.26^\circ) \times 4\angle(-20^\circ) = 1.5060\angle(-51.26^\circ)$


Hence, $v_L(t) = 1.5060\cos(3t - 51.26^\circ)$

7. (20%) Consider the circuit on the right with

$\tilde{V}_s = 5\angle 30^\circ$. If $Z = R + jX$, determine the

maximum power P_{max} transferred to the Z .

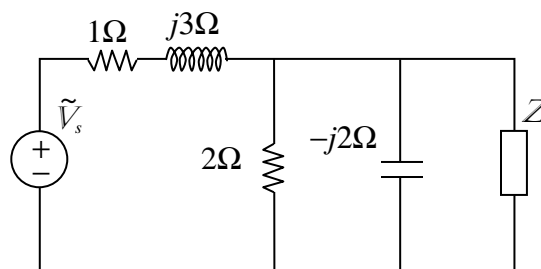If $Z = R$, what is the maximum power P_{max} transferred to R ?



Sol:

The Thevenin equivalent circuit is on the right.

If $Z = 1.5 + j0.5$, the maximum power is

$$P_{max} = \frac{\tilde{V}_T^2}{4R_T} = \frac{0.25^2}{4 \times 1.5} = 0.0104 \text{ W}$$

If $Z = R = \sqrt{1.5^2 + 0.5^2} = 1.5811$,

the maximum power is

$$P_{max} = \frac{\tilde{V}_T^2}{2(R + R_T)} = \frac{0.25^2}{2(1.5811 + 1.5)} = 0.0101 \text{ W}$$

