


1. (10%) Assume a current  $i(t)=10\text{mA}$  passes through a long electrical line, whose cross area is  $a = 7\mu\text{m}^2$ . Let the density be  $n = 6.3 \times 10^{28}$  particles/ $\text{m}^3$  and the charge of each particle be  $q = 1.6 \times 10^{-19}\text{C}$ . What is the average velocity of the particles moving along the electrical line?

Sol: Since  $i = \frac{Q}{T} = \frac{Lanq}{L/v} = anqv$ , we have the average velocity

$$v = \frac{i}{anq} = \frac{0.01}{7 \times 10^{-6} \times 6.3 \times 10^{28} \times 1.6 \times 10^{-19}} = \frac{1}{70.56 \times 10^5} = 1.42 \times 10^{-7} \text{ m/sec}$$


2. (5%) In Fig-1, select a tree and show the cut surfaces  $S_i, i=1,2,\dots$

Sol:

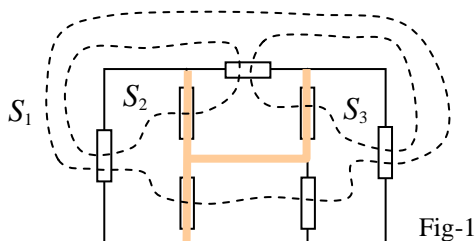


3. (15%) In Fig-2, find the equivalent resistance  $R_{eq}$ .

Sol:

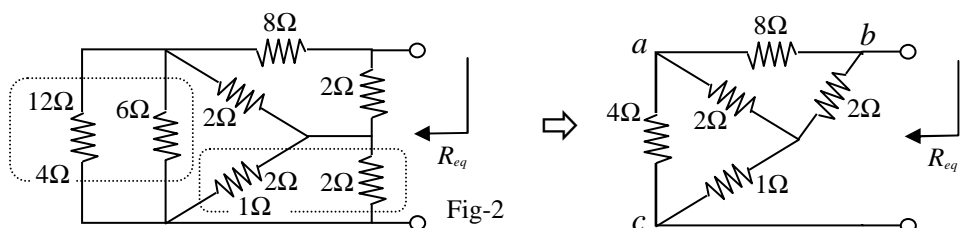

Y- $\Delta$  transform:
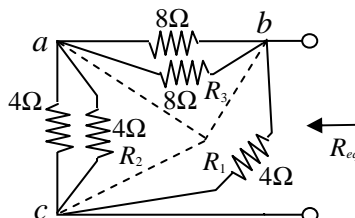
$$\begin{aligned} R_1 R_a &= R_2 R_b = R_3 R_c = R_a R_b + R_b R_c + R_c R_a \\ \Rightarrow 2R_1 &= 2R_2 = R_3 = 4 + 2 + 2 = 8 \\ \Rightarrow R_1 &= 4, R_2 = 4, R_3 = 8 \end{aligned}$$



$$R_{eq} = 4 // ((4 // 4) + (8 // 8)) = 4 // (2 + 4) = 4 // 6 = 24 / (4 + 6) = 2.4 \Omega$$


4. (15%) In Fig-3, write the nodal voltage equation  $Fv=Gu$ .

Sol:

$$\begin{aligned} \text{KCL} \textcircled{1}: \quad v_1 + 4(v_1 - v_2) + (v_1 - v_4) &= -I \\ \Rightarrow 6v_1 - 4v_2 - v_4 &= -I \end{aligned}$$

$$\text{KVL} \textcircled{2} \textcircled{3}: \quad v_2 - v_3 = v(t)$$
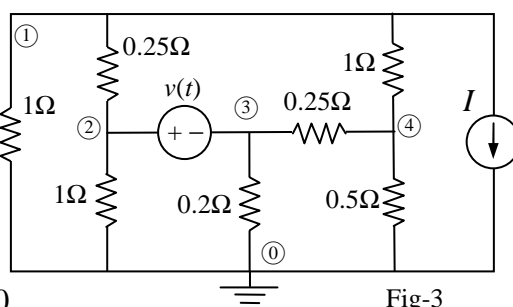
$$\begin{aligned} \text{KCL} \textcircled{2} \textcircled{3}: \quad 4(v_2 - v_1) + 4(v_3 - v_4) + v_2 + 5v_3 &= 0 \\ \Rightarrow -4v_1 + 5v_2 + 9v_3 - 4v_4 &= 0 \end{aligned}$$



KCL④:  $(v_4 - v_1) + 4(v_4 - v_3) + 2v_4 = 0 \Rightarrow -v_1 - 4v_3 + 7v_4 = 0$

The nodal voltage equation is

$$\underbrace{\begin{bmatrix} 6 & -4 & 0 & -1 \\ 0 & 1 & -1 & 0 \\ -4 & 5 & 9 & -4 \\ -1 & 0 & -4 & 7 \end{bmatrix}}_{\mathbf{F}} \cdot \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} -1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \end{bmatrix}}_{\mathbf{G}} \cdot \underbrace{\begin{bmatrix} I \\ v(t) \end{bmatrix}}_{\mathbf{u}}$$


5. (15%) In Fig-4, solve  $i$  through the resistor  $2\Omega$  based on the mesh analysis.

Sol:

KCL①②:  $i_1 - i_2 = -3v_x = -3i_2 \Rightarrow i_1 = -2i_2$

KVL①②:  $2i_1 + i_2 + 2(i_2 - i_3) = 0$   
 $\Rightarrow 2i_1 + 3i_2 - 2i_3 = 0 \Rightarrow i_2 = -2i_3$

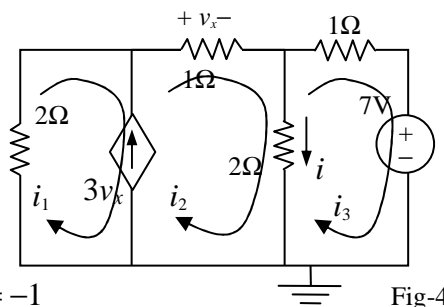
KVL③:  $2(i_3 - i_2) + i_3 = -7$   
 $\Rightarrow 3i_3 - 2i_2 = -7 \Rightarrow 7i_3 = -7 \Rightarrow i_3 = -1$



Hence,  $i = i_2 - i_3 = -2i_3 - i_3 = -3i_3 = 3 \text{ A}$

6. (15%) In Fig-5, write the Thevenin equivalent circuit through  $R_L$ . What is the resistance  $R_L$  that can receive the maximum power? What is the maximum power?

Sol:

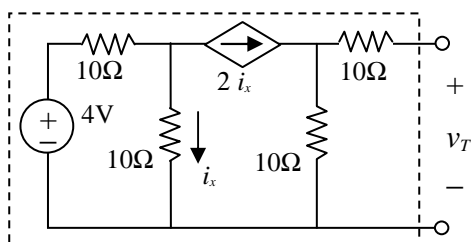



$4 = 10(i_x + 2i_x) + 10i_x \Rightarrow i_x = 0.1$

$v_T = 10 \times 2i_x = 2 \text{ V}$

From the circuit on the right,

we have  $i_x + i_x + 2i_x = 0 \Rightarrow i_x = 0$

Hence,  $R_T = 10 + 10 = 20 \Omega$

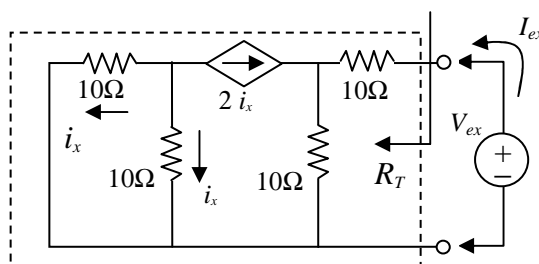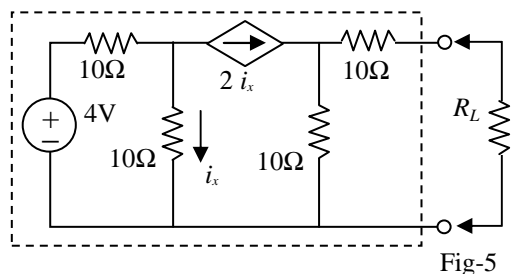


The Thevenin equivalent circuit is shown on the right.

If  $R_L = 20\Omega$ , it can receive the maximum power.

The voltage across  $R_L$  is  $v_L = \frac{20}{20 + 20} \times 2 = 1 \text{ V}$

and the current is  $i_L = \frac{2}{20 + 20} = 0.05 \text{ A}$

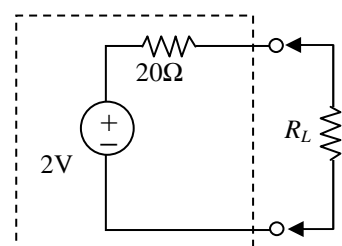Therefore, the maximum power is  $p_{L,max} = v_L i_L = 1 \times 0.05 = 0.05 \text{ W}$



7. (10%) In Fig-6, consider a voltage source  $v(t)=2u(t)-3u(t-1)+2u(t-4)-u(t-5)$  and apply it to a resistor  $R=4\Omega$ . What is the average power dissipated by  $R$  for  $0 < t < 6$ ?

Sol:

The curve of  $v(t)$  is shown on the right.

The power is  $p(t) = \frac{v^2(t)}{R}$  and

the average power is

$$P_{av} = \frac{1}{6} \int_0^6 \frac{v^2(t)}{4} dt$$

$$= \frac{1}{6} \left( \int_0^1 \frac{2^2}{4} dt + \int_1^4 \frac{(-1)^2}{4} dt + \int_4^5 \frac{1^2}{4} dt \right) = \frac{1}{6} \left( 1 + \frac{3}{4} + \frac{1}{4} \right) = \frac{1}{3} \text{ W}$$

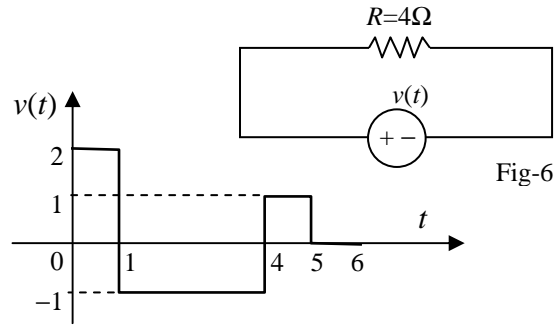


Fig-6

8. (15%) In Fig-7, a constant voltage source  $v(t)=5\text{V}$  is connected to a series  $RC$  circuit with  $R=40\text{k}\Omega$  and  $C=5\mu\text{F}$ . If the initial voltage across the capacitor is  $v_C(0)=1\text{V}$ , then what is the current  $i_R(t)$  for  $t > 0$ ?

Sol:

The system equation is

$$\dot{v}_C(t) = \frac{1}{C} i_C(t) = \frac{5 - v_C(t)}{RC} = 25 - 5v_C(t)$$

$$\Rightarrow \dot{v}_C(t) + 5v_C(t) = 25$$

Hence,  $\Rightarrow v_C(t) = -4e^{-5t} + 5$

We have  $i_R(t) = \frac{5 - v_C(t)}{40 \times 10^3} = 0.1 \times e^{-5t} \text{ mA}$

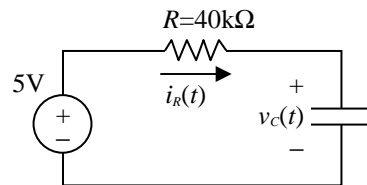


Fig-7