

NCTU Summer Course <Electrical Circuits> Quiz-01

\_\_\_\_\_大學\_\_\_\_\_系 學號\_\_\_\_\_ 姓名\_\_\_\_\_

1. (25%) In addition to the fundamental SI units m, kg, sec and A, some derived units are also used in electrical engineering. For example, J(joule) is the unit of energy  $E$ , W(watt) is the unit of power  $P$ , H(henry) is the unit of inductance  $L$  and  $\Omega$ (Ohm) is the unit of resistance  $R$ . It is known that the power dissipated in a resistor is  $P = RI^2$  and the energy stored in an inductor is  $E = LI^2/2$  where  $I$  is the current. Show the expression of J, W, H and  $\Omega$  in terms of m, kg, sec and A.

Sol:

$$J \equiv \text{kg}\cdot\text{m}^2/\text{s}^2$$

$$W \equiv \text{kg}\cdot\text{m}^2/\text{s}^3$$

$$H \equiv \text{kg}\cdot\text{m}^2/\text{s}^2/\text{A}^2$$

$$\Omega \equiv \text{kg}\cdot\text{m}^2/\text{s}^3/\text{A}^2$$

2. (25%) Let  $f(t) = \int_0^2 (2x^2 + 3)dx$ ,  $g(t) = \int_0^t (2y^2 + 3)dy$  and  $h(t) = \int_0^t (2tz + 3)dz$ .

Calculate  $\frac{df(t)}{dt}$ ,  $\frac{dg(t)}{dt}$  and  $\frac{dh(t)}{dt}$ .

Sol:

$$f(t) = \int_0^2 (2x^2 + 3)dx = \text{constant} \Rightarrow \frac{df(t)}{dt} = 0$$


$$g(t) = \int_0^t (2y^2 + 3)dy \Rightarrow \frac{dg(t)}{dt} = 2t^2 + 3$$

$$h(t) = \int_0^t (2tz + 3)dz = t^3 + 3t \Rightarrow \frac{dh(t)}{dt} = 3t^2 + 3$$

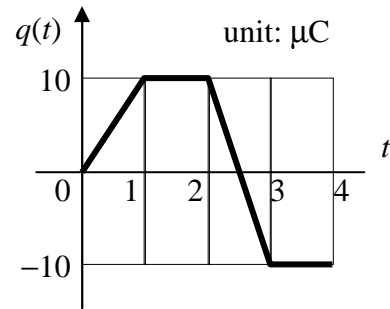3. (25%) Consider an electrical element whose voltage  $v(t)=\alpha q(t)$  where  $\alpha=2000\text{V/C}$  and  $q(t)$  is the stored charge as shown in the figure on the right. Let the current through the element be


$$i(t) = \frac{dq(t)}{dt} \text{ in passive sign. What is the}$$

average power for  $t \in [0, 4]\text{sec}$  ?



Sol:
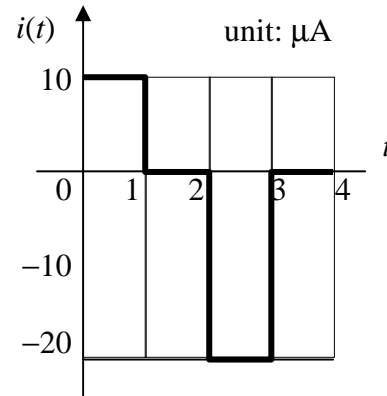
$$\begin{aligned} P &= \frac{1}{4} \int_0^4 p(t) dt = \frac{1}{4} \int_0^4 v(t) i(t) dt \\ &= 500 \int_0^4 q(t) i(t) dt \\ &= 5 \times 10^{-10} \left( \int_0^1 (10t \cdot 10) dt + \int_2^3 (-20(t-2.5)) \cdot (-20) dt \right) \\ &= 5 \times 10^{-8} (0.5 + 0) = 2.5 \times 10^{-8} \text{ W} \end{aligned}$$



4. (25%) Assume a long conductor with cross area  $a = 9 \times 10^{-6} \text{ m}^2$  is uniformly distributed with electrical particles whose density is  $n = 5 \times 10^{28} \text{ particles/m}^3$ . Let the charge of each particle be  $q = 3.2 \times 10^{-19} \text{ C}$ . If a current  $i(t)=0.2\text{A}$  through the conductor is measured, what is the velocity of the electrical particles?

Sol:

$$I = \frac{\Delta Q}{\Delta t} = \frac{\Delta Q/L}{\Delta t/L} = \frac{\Delta Q \cdot v}{L} = \frac{aLnq \cdot v}{L} = anqv$$

Hence,


$$v = \frac{I}{anq} = \frac{0.2}{9 \times 10^{-6} \times 5 \times 10^{28} \times 3.2 \times 10^{-19}} = \frac{1}{9 \times 10^4 \times 8} = 1.39 \times 10^{-6} \text{ m/s}$$

大學 \_\_\_\_\_ 系 學號 \_\_\_\_\_ 姓名 \_\_\_\_\_


1. (25%) In the following circuit,  
 (A) select a tree and show the cut surfaces  $S_i, i=1,2,\dots,$   
 (B) select a different tree and show the link loops,  $i=1,2,\dots$

Sol:


(A)

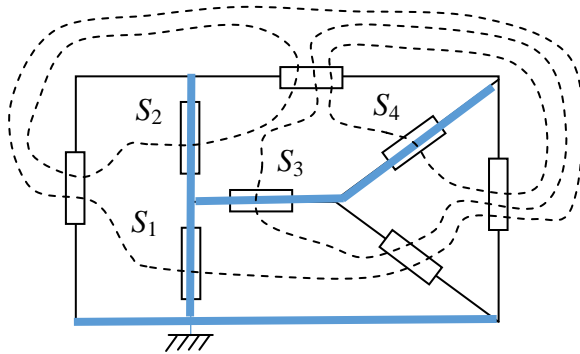

(B)

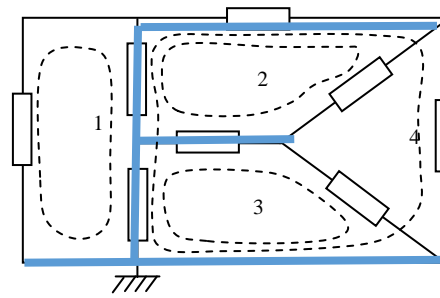

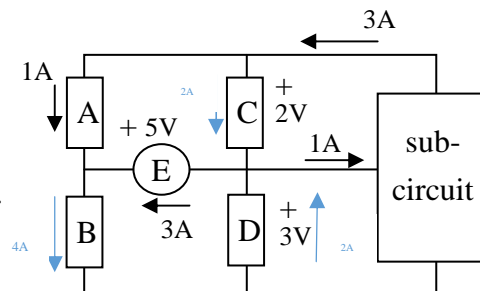2. (25%) A circuit is depicted on the right, which contains five elements and one sub-circuit. Determine the power absorbed by each element. Is the sub-circuit a power provider or a power absorber?



Sol:

$$V_A = V_E - V_C = -(5-2) = -3V$$

$$P_A = -3 \times 1 = -3W$$

$$V_B = -(-V_E + V_D) = 8V$$

$$P_B = 8 \times 4 = 32W$$

$$P_C = 2 \times 2 = 4W$$

$$P_D = -2 \times 3 = -6W$$

$$V_E = -3 \times 5 = -15W$$


$$P_A + P_B + P_C + P_D + P_E + P_{sub} = 0$$

$$P_{sub} = -12W$$


(power provider)

3. (25%) There are four dependent sources, voltage-controlled voltage source (VCVS), voltage-controlled current source (VCCS), current-controlled voltage source (CCVS), and current-controlled current source (CCCS). Please write their component symbols and control equations.


Sol:

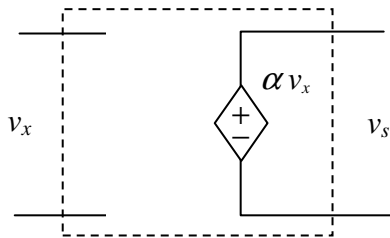


(a) VCVS

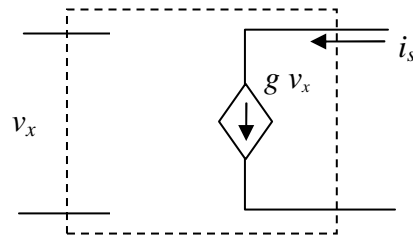

(b) VCCS

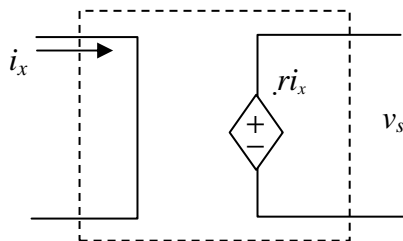

(c) CCVS

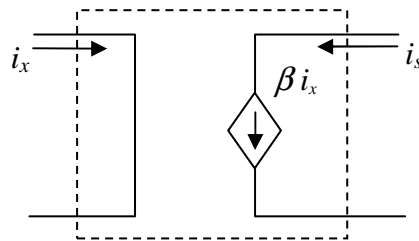

(d) CCCS

4. (25%) A circuit is shown on the right.

Find the current  $i_x$  and voltage  $v_x$ .


Sol:

$$2v_x = i_x + 4$$

$$5i_x + (-7V) - v_x = 0$$

$$v_x = 3V$$


$$i_x = 2A$$

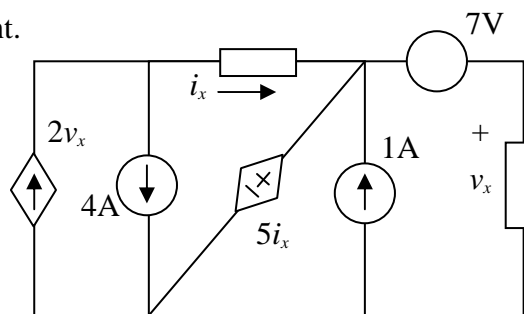

\_\_\_\_\_ 大學 \_\_\_\_\_ 系 學號 \_\_\_\_\_ 姓名 \_\_\_\_\_

1. (25%) In the following circuit, Find the equivalent resistances  $R_1$  and  $R_2$ .

Sol:

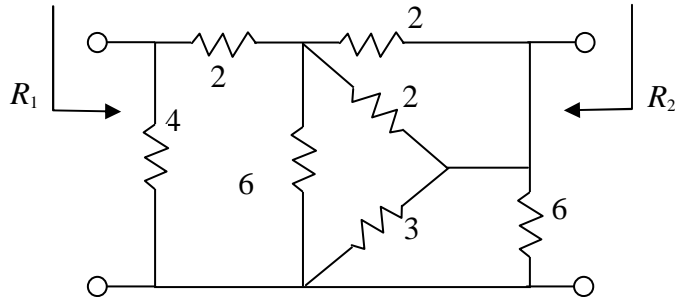

$$R_1: (((6 // 3) + (2 // 2)) // 6) + 2 // 4 = 2$$

$$R_2: ((4 + 2) // 6) // ((2 // 2) + 3) // 6 = 4/3$$


2. (25%) A voltage source  $v(t) = 3\cos 3t + 2e^{-2t}$  V is applied to a capacitor with  $C = 47\mu\text{F}$  parallel to a resistor  $R = 2\text{k}\Omega$ . What is the current  $i(t)$  generated by the voltage source?

Sol:

$$i(t) = i_C(t) + i_R(t)$$

$$i_R(t) = \frac{3\cos 3t + 2e^{-2t}}{2000} \text{ A}$$
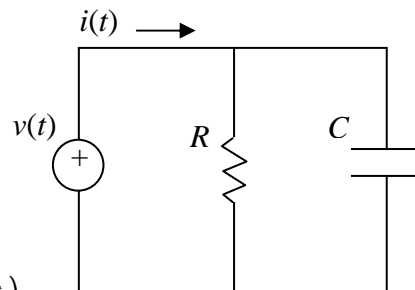
$$i_C(t) = C \frac{dv(t)}{dt} = 47 \times 10^{-6} (-9\sin 3t - 4e^{-2t})$$




Hence,

$$i(t) = \frac{3\cos 3t + 2e^{-2t}}{2000} + 47 \times 10^{-6} (-9\sin 3t - 4e^{-2t})$$

$$= 1.5 \cos 3t - 0.423 \sin 3t + 0.812e^{-2t} \text{ mA}$$

3. (25%) The current  $i(t)$  through a capacitor with  $C=50\mu\text{F}$  is shown in the following figure. If the capacitor has no charge at the initial time, i.e.,  $q_c(0)=0\text{ C}$ , draw the voltage  $v(t)$  of the capacitor.

Sol:

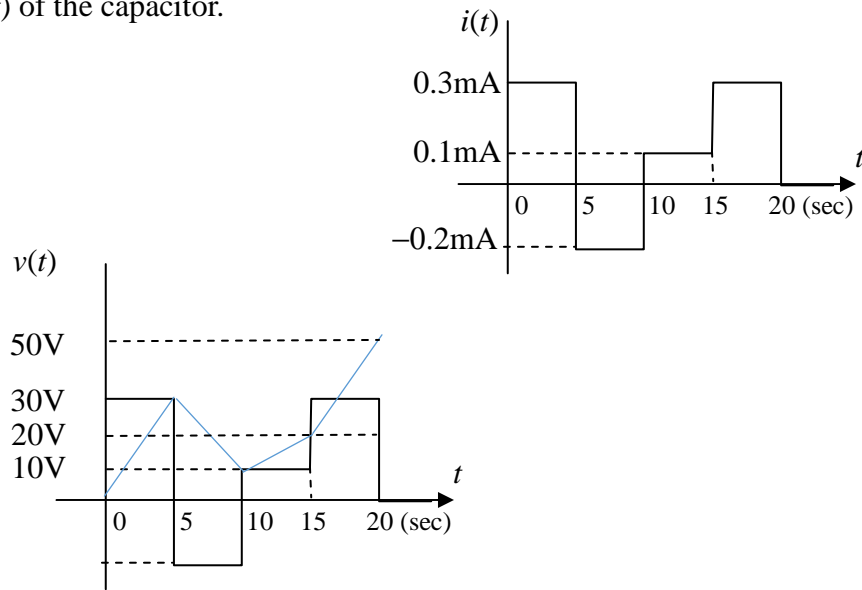

4. (25%) A circuit is shown on the right. Find the current  $i_x$  and voltage  $v_x$ .



Sol:

$$5i_x = 2i_x + (1 + i_x)2$$

$$i_x = 2\text{ A}$$

$$v = 5i_x - 2i_x = 10 - 4 = 6\text{ V}$$

$$v_x = \frac{1}{6}v = 1\text{ V}$$

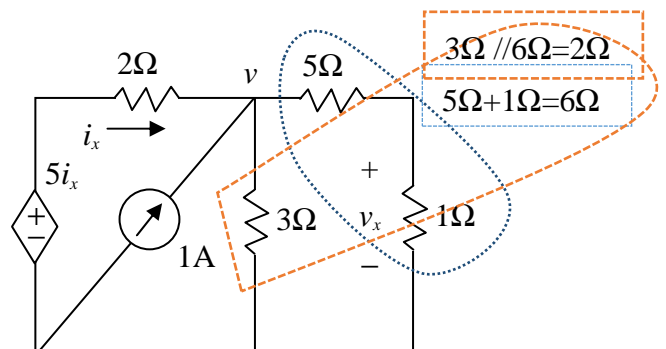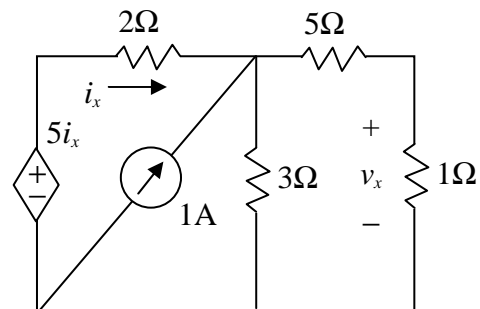

大學 \_\_\_\_\_ 系 學號 \_\_\_\_\_ 姓名 \_\_\_\_\_

1. (30%) The voltage source is  $v(t)=0.6 \sin 2t$  and there is no initial energy stored in the circuit. Find the equivalent inductance  $L_{eq}$  through A and B and the total energy  $w(t)$  stored in all the inductors at time  $t$ .

Sol:

$$L_{eq} = 2\text{mH}$$

$$v(t) = 0.6 \sin 2t$$

$$i_L(t) = \frac{1}{L_{eq}} \int_0^t v(\tau) d\tau$$


$$= \frac{10^3}{2} \int_0^t 0.6 \sin 2\tau d\tau$$

$$= -\frac{10^3}{2} 0.3 \cos 2\tau \Big|_0^t$$

$$= -0.15(\cos 2t - 1) \text{ kA}$$


$$w(t) = \frac{1}{2} L_{eq} i_L^2(t)$$

$$= 22.5(\cos 2t - 1)^2$$

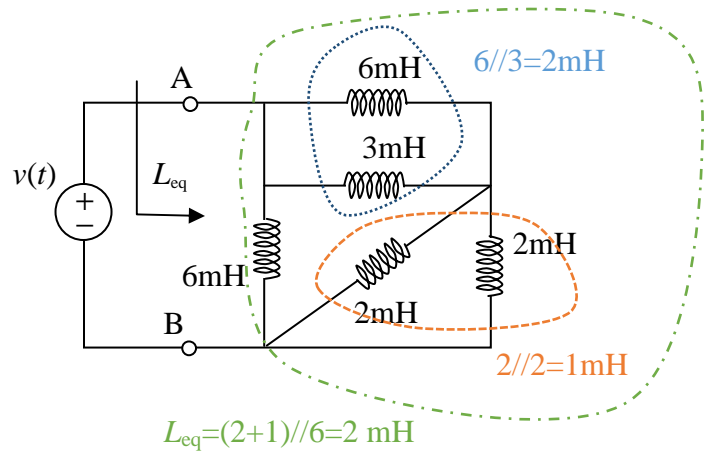

2. (30%) Based on nodal analysis, determine the current  $i(t)$ .

Sol:

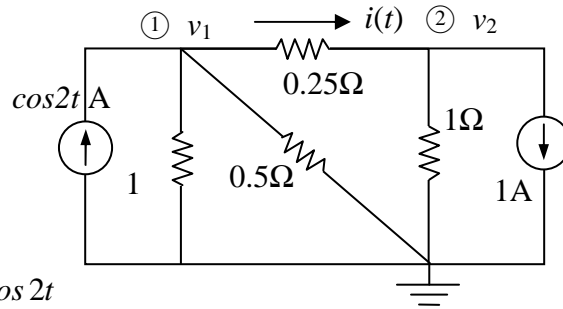

$$KCL \text{①: } 4(v_1 - v_2) + 1 \cdot v_1 + 2 \cdot v_1 = \cos 2t$$

$$\Rightarrow 7v_1 - 4v_2 = \cos 2t$$

$$KCL \text{②: } 4(v_2 - v_1) + 1 \cdot v_2 = -1$$

$$\Rightarrow -4v_1 + 5v_2 = -1$$


$$\text{Hence, } v_1 = \frac{-4 + 5 \cos 2t}{19}, \quad v_2 = \frac{-7 + 4 \cos 2t}{19}$$

$$\Rightarrow i(t) = 4(v_1 - v_2) = \frac{12 + 4 \cos 2t}{19} \text{ A}$$

3. (40%) Based on nodal analysis, write the nodal voltage equation

$$\mathbf{Fv}=\mathbf{Gu}.$$

Sol:

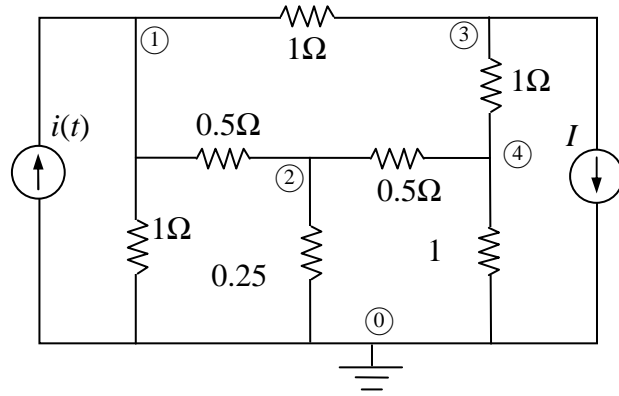

$$KCL①: 1 \cdot (v_1 - v_3) + 1 \cdot v_1 + 2 \cdot (v_1 - v_2) = i(t)$$

$$\Leftrightarrow 4v_1 - 2v_2 - v_3 = i(t)$$

$$KCL②: 2 \cdot (v_2 - v_1) + 4 \cdot v_2 + 2 \cdot (v_2 - v_4) = 0$$

$$\Leftrightarrow -2v_1 + 8v_2 - 2v_4 = 0$$

$$KCL③: 1 \cdot (v_3 - v_1) + 1 \cdot (v_3 - v_4) = -I$$

$$\Leftrightarrow -v_1 + 2v_3 - v_4 = -I$$

$$KCL④: 1 \cdot (v_4 - v_3) + 1 \cdot v_4 + 2 \cdot (v_4 - v_2) = 0$$

$$\Leftrightarrow -2v_2 - v_3 + 4v_4 = 0$$

Hence, we have

$$\underbrace{\begin{bmatrix} 4 & -2 & -1 & 0 \\ -2 & 8 & 0 & -2 \\ -1 & 0 & 2 & -1 \\ 0 & -2 & -1 & 4 \end{bmatrix}}_{\mathbf{F}} \cdot \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & -1 \\ 0 & 0 \end{bmatrix}}_{\mathbf{G}} \cdot \underbrace{\begin{bmatrix} i(t) \\ I \end{bmatrix}}_{\mathbf{u}}$$



\_\_\_\_\_大學 \_\_\_\_\_系 學號\_\_\_\_\_ 姓名\_\_\_\_\_

1. (50%) Based on the nodal analysis, solve the voltage  $v$  across the resistor  $1\Omega$ .

Sol:

KVL①:  $v_1 = 3$

KCL②:  $4(v_2 - v_1) + 2v_2 + 1 \cdot (v_2 - v_3) = -1$

$\Rightarrow -4v_1 + 7v_2 - v_3 = -1$

KCL③:  $v_3 = 2(2v_2) = 4v_2$


We have

$-12 + 7v_2 - 4v_2 = -1$

$\Rightarrow v_2 = \frac{11}{3}$

and then

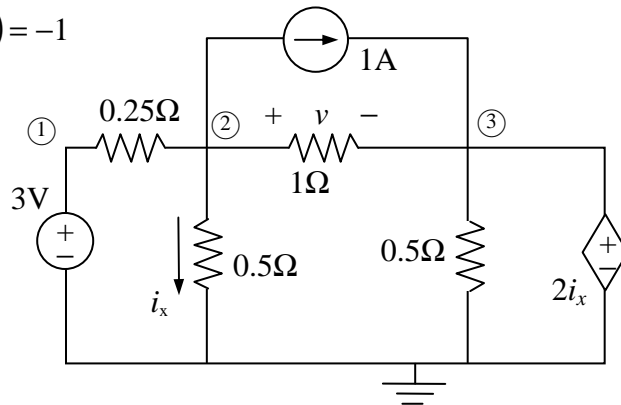$\Rightarrow v = v_2 - v_3 = -3v_2 = -11 \text{ V}$



2. (50%) Based on the mesh analysis, solve the current  $i$  through the resistor  $1\Omega$ .

Sol:

KCL①②:  $i_2 - i_1 = 1$

KVL①②:  $5i_1 + 2i_1 + 3i_2 + 1 \cdot (i_2 - i_3) = 0$

$\Rightarrow 7i_1 + 4i_2 - i_3 = 0$

KVL③:  $3(-5i_1) + 1 \cdot (i_3 - i_2) = 0$

$\Rightarrow -15i_1 - i_2 + i_3 = 0$


We have

$i_2 - i_1 = 1$

$-8i_1 + 3i_2 = 0$

which leads to  $i_1 = 0.6$ ,  $i_2 = 1.6$ , and  $i_3 = 10.6$ .

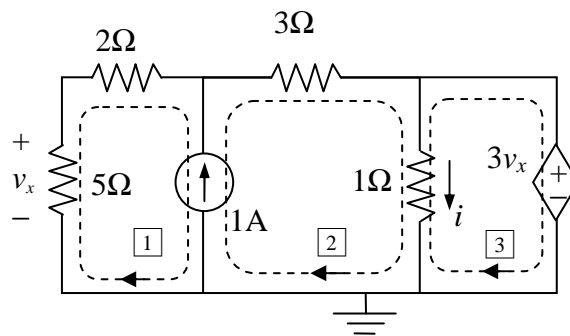Therefore,  $i = i_2 - i_3 = 9 \text{ A}$



大學 \_\_\_\_\_ 系 學號 \_\_\_\_\_ 姓名 \_\_\_\_\_

1. (50%) Draw the Norton equivalent circuit referring to the load resistance  $R_L$ .


Sol:

(I) Short  $R_L$  to find short current  $i_N$

Since the output is short,

We have  $i_x = 0$ .

Then,  $i_N = 15 / (3 + 3) = 2.5$  A

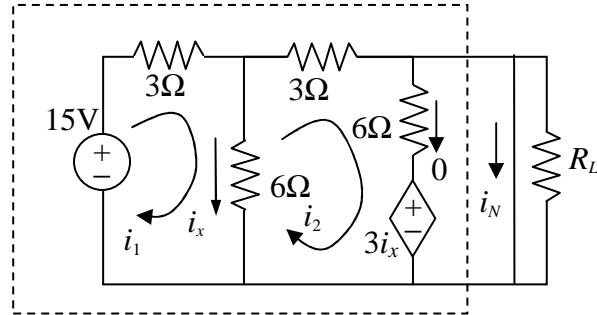


(II) Take away source and add an extra source

$$V_{ex} = 3 \cdot 3i_x + 6i_x = 6(I_{ex} - 3i_x) + 3i_x$$


We have  $i_x = \frac{V_{ex}}{15}$  and

$$V_{ex} = 6 \left( I_{ex} - \frac{V_{ex}}{5} \right) + \frac{V_{ex}}{5} = 6I_{ex} - V_{ex}$$
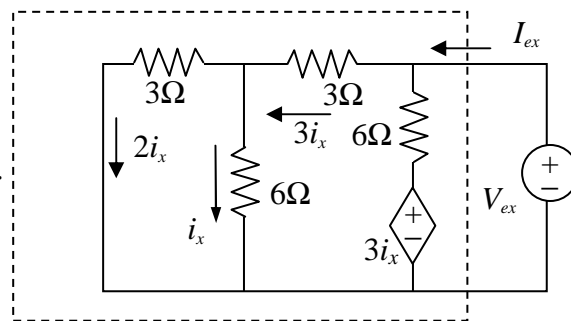
$$\text{Hence, } R_N = \frac{V_{ex}}{I_{ex}} = 3 \Omega$$



The Norton's equivalent circuit is

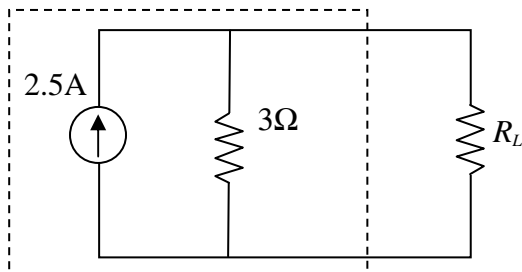

2. (50%) What is the maximum power can be transferred to the load resistance  $R_L$ .


Sol:

(I) Take away  $R_L$  to find open voltage  $v_T$

$$\text{Since } (2+1)(3-i_x) + 2i_x = 5i_x,$$

we have  $i_x = 1.5$  and
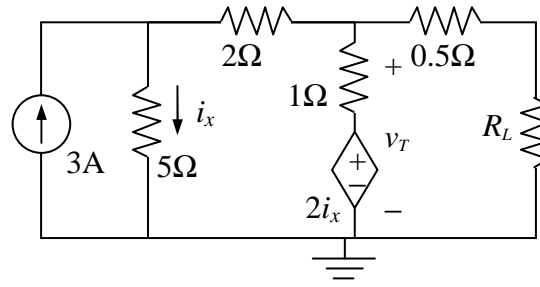
$$v_T = (3-i_x) + 2i_x = 4.5 \text{ V.}$$




(II) Take away source and add an extra source


$$V_{ex} = 0.5I_{ex} + 7i_x = 0.5I_{ex} + (I_{ex} - i_x) + 2i_x$$

We have  $i_x = 0.1V_{ex} = I_{ex} / 6$
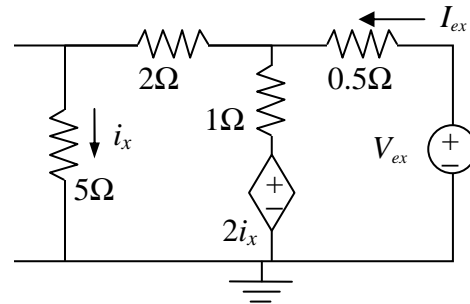
$$\text{and thus } R_T = \frac{V_{ex}}{I_{ex}} = \frac{5}{3}.$$



The Thevenin's equivalent circuit is

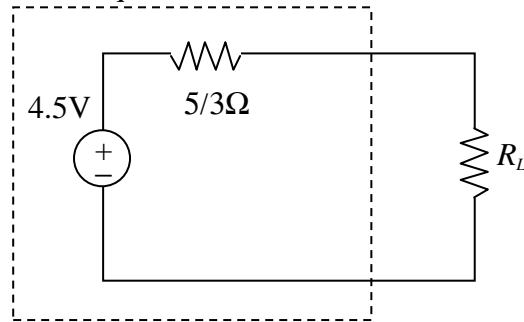

Choose  $R_L = 5/3 \Omega$ , then the maximum power is  $P_{max} = \frac{4.5}{2} \cdot \frac{4.5}{5/3 + 5/3} = 3.0375 \text{ W}$

\_\_\_\_\_大學 \_\_\_\_\_系 學號\_\_\_\_\_ 姓名\_\_\_\_\_

1. (50%) Consider a system described by the following ODE:

$$2\dot{y}(t) + 3y(t) = 12, \quad y(0.5) = 1$$

Find  $y(t)$ , for  $t \geq 0.5$ . What is the time constant of this system?

Sol:


$$y(t) = -3e^{-1.5(t-0.5)} + 4$$

Time constant is 0.667 sec.

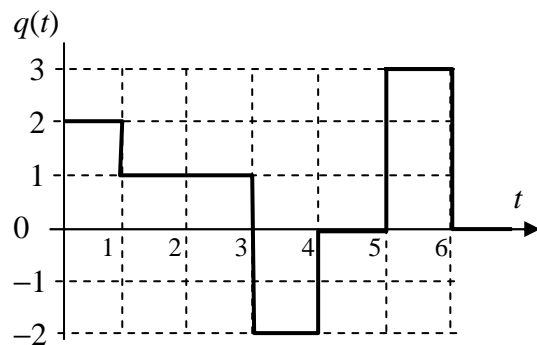2. (50%) A piecewise continuous function  $q(t)$  is depicted below. Express  $q(t)$  by the combination of step functions  $u(t-\alpha)$  where  $\alpha$  is an integer.

Sol:

$$q(t) = 2u(t) - u(t-1) - 3u(t-3) + 2u(t-4) + 3u(t-5) - 3u(t-6)$$



\_\_\_\_\_大學 \_\_\_\_\_系 學號\_\_\_\_\_ 姓名\_\_\_\_\_


1. (50%) Consider the  $RL$  circuit shown below, where the initial inductor current is  $i_L(0) = 1 \text{ A}$ . What is the inductor current  $i_L(t)$  for  $t \geq 0$ ?

Sol:

$$R/L = 0.6/5\text{m} = 120$$

$$i_L(0) = 1 \text{ A}, \quad i_L(\infty) = 5 \text{ A}$$

$$i_L(t) = -4e^{-120t} + 5 \text{ A}$$

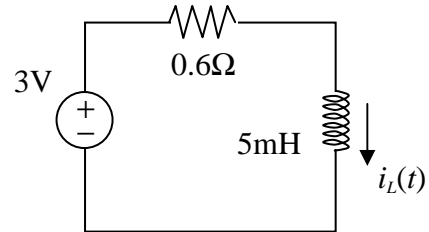

2. (50%) Consider the circuit shown below, where the initial capacitor voltage is  $v_C(0) = 1 \text{ V}$ . What is the capacitor voltage  $v_C(t)$  for  $t \geq 0$ ?

Sol:

$$v_T = 4 \text{ V}$$

$$R_T = 4 \text{ k}\Omega$$

$$1/R_T C = 5$$

$$v_C(0) = 1 \text{ V}, \quad v_C(\infty) = 4 \text{ V}$$

$$v_C(t) = -3e^{-5t} + 4 \text{ V}$$

