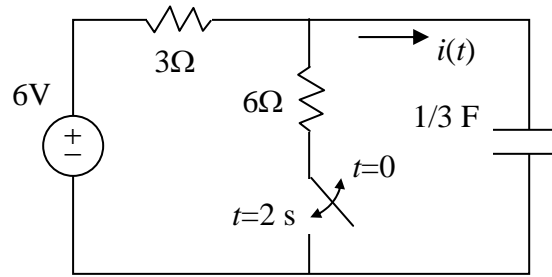


1. The switch has been closed for a long time. If the switch is opened at $t=0$ and is closed again at $t=2$ sec, determine $i(t)$ for $t>0$.



Sol:

Let the voltage across the capacitor is $v_C(t)$. Since the switch has been closed for a long time, we

have $\frac{1}{3} \frac{dv_C}{dt} + \frac{v_C - 6}{3} + \frac{v_C}{6} = 0$, where $\frac{dv_C}{dt}(0^-) = 0$ and then $v_C(0^-) = 4$ V.

For $2 > t > 0$, the switch is opened and then $\frac{1}{3} \frac{dv_C}{dt} + \frac{v_C - 6}{3} = 0 \Rightarrow \frac{dv_C}{dt} + v_C = 6$.

This leads to $v_C(t) = Ae^{-t} + 6$ and $v_C(0^+) = v_C(0^-) = 4 \Rightarrow A + 6 = 4 \Rightarrow A = -2$.

Hence, $v_C(t) = -2e^{-t} + 6$ and $i(t) = \frac{1}{3} \dot{v}_C(t) = \frac{2}{3}e^{-t}$ for $2 > t > 0$.

For $t > 2$, the switch is closed again and then $\frac{1}{3} \frac{dv_C}{dt} + \frac{v_C - 6}{3} + \frac{v_C}{6} = 0$, where $v_C(2^-) = -2e^{-2} + 6$.


We have $\frac{dv_C}{dt} + \frac{3v_C}{2} = 6$ and then $v_C(t) = Be^{-\frac{3}{2}t} + 4$.

Hence, $v_C(2^+) = v_C(2^-) = -2e^{-2} + 6 \Rightarrow Be^{-3} + 4 = -2e^{-2} + 6 \Rightarrow B = -2e + 2e^3$.

This results in $v_C(t) = (-2e + 2e^3)e^{-\frac{3}{2}t} + 4 = 34.73e^{-\frac{3}{2}t} + 4$ and $i(t) = \frac{1}{3} \dot{v}_C(t) = -17.37e^{-\frac{3}{2}t}$.

The total solution for $t > 0$ is
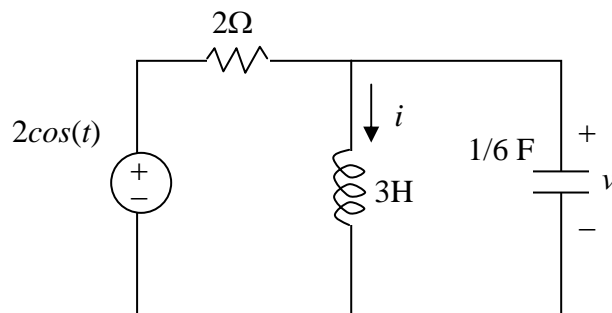
$$i(t) = \begin{cases} \frac{2}{3}e^{-t}, & 2 > t > 0 \\ -17.37e^{-\frac{3}{2}t}, & t > 2 \end{cases}$$



2. Determine $v(t)$ for $t \rightarrow \infty$.

Sol:

The component equations are $\frac{1}{6} \frac{dv}{dt} = i_C = \frac{2\cos(t) - v}{2} - i$ and $3 \frac{di}{dt} = v_L = v$, i.e.,

$$\dot{v} = -3v - 6i + 6\cos(t) \quad \text{and} \quad \frac{di}{dt} = \frac{1}{3}v.$$

Hence, the system equation is derived as

$$\ddot{v} = -3\dot{v} - 6\frac{di}{dt} - 6\sin(t) = -3\dot{v} - 2v - 6\sin(t) \Rightarrow \ddot{v} + 3\dot{v} + 2v = -6\sin(t).$$

First, calculate $\left. \frac{1}{D^2 + 3D + 2} \right|_{D=j} = \left. \frac{1}{1 + j3} \right| = \frac{1}{\sqrt{10}} \angle \theta$, where $\cos \theta = \frac{1}{\sqrt{10}}$ and $\sin \theta = -\frac{3}{\sqrt{10}}$.

Hence,

$$v(t) = -6 \cdot \left(\frac{1}{\sqrt{10}} \right) \sin(t + \theta) = -\frac{6}{\sqrt{10}} (\sin(t)\cos\theta + \cos(t)\sin\theta) = -\frac{6}{10}\sin(t) + \frac{18}{10}\cos(t).$$


3. If $i(0^-)=1, v(0^-)=2$, determine $v(t)$ for $t>0$.

Sol:

The component equations are

$$\frac{1}{4}\dot{v} = -i \Rightarrow \dot{v}(0^+) = -4i(0^+) = -4i(0^-) = -4$$

$$2\frac{di}{dt} = v - 6i$$

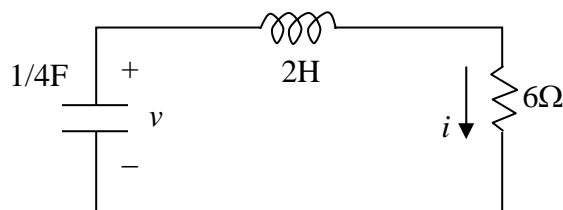

The system equation is derived as $\ddot{v} = -4\frac{di}{dt} = -2v + 12i = -2v - 3\dot{v} \Rightarrow \ddot{v} + 3\dot{v} + 2v = 0$,

i.e., $\ddot{v} + 3\dot{v} + 2v = 0$, $v(0^+) = v(0^-) = 2$ and $\dot{v}(0^+) = -4$.

The eigenfunction is $s^2 + 3s + 2 = 0 \Rightarrow s = -1, -2$, and then

$$v(t) = Ae^{-t} + Be^{-2t}, \quad v(0^+) = A + B = 2$$

$$\dot{v}(t) = -Ae^{-t} - 2Be^{-2t}, \quad \dot{v}(0^+) = -A - 2B = -4.$$

Hence, $A = 0$ and $B = 2$, i.e., $v(t) = 2e^{-2t}, t>0$.


4. If $v_1(0^-)=0, v_2(0^-)=10$, determine $i(t)$ for $t>0$.

Sol:

The component equations are

$$\frac{1}{8}\dot{v}_1 = i_{C1} = \frac{v_2 - v_1}{4} \Rightarrow \dot{v}_1 = 2v_2 - 2v_1$$
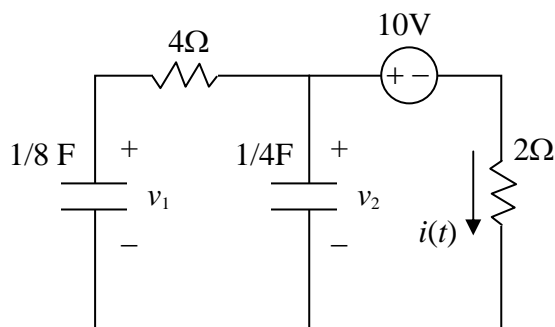
$$\frac{1}{4}\dot{v}_2 = i_{C2} = -i_{C1} - i = -\frac{v_1 - v_2}{4} - \frac{v_2 - 10}{2} = \frac{v_1}{4} - \frac{3v_2}{4} + 5 \Rightarrow \dot{v}_2 = v_1 - 3v_2 + 20$$



The system equation is derived as

$$\ddot{v}_2 = \dot{v}_1 - 3\dot{v}_2 = 2v_2 - 2v_1 - 3\dot{v}_2 = 2v_2 - 2(\dot{v}_2 + 3v_2 - 20) - 3\dot{v}_2 = -5\dot{v}_2 - 4v_2 + 40$$

We have

$$\ddot{v}_2 + 5\dot{v}_2 + 4v_2 = 40.$$

where $v_2(0^+) = v_2(0^-) = 10$ and $\dot{v}_2(0^+) = v_1(0^+) - 3v_2(0^+) + 20 = v_1(0^-) - 3v_2(0^-) + 20 = -10$

The particular solution is $v_{2p}=10$. The eigenfunction is $s^2 + 5s + 4 = 0 \Rightarrow s = -1, -4$, and then


$$v_2(t) = Ae^{-t} + Be^{-4t} + 10, \quad v_2(0^+) = A + B + 10 = 10$$

$$\dot{v}_2(t) = -Ae^{-t} - 4Be^{-4t}, \quad \dot{v}_2(0^+) = -A - 4B = -10.$$

Hence, $A = -\frac{10}{3}$ and $B = \frac{10}{3}$, which results in $v_2(t) = -\frac{10}{3}e^{-t} + \frac{10}{3}e^{-4t} + 10, t > 0$.

The solution is $i(t) = \frac{v_2(t) - 10}{2} = -\frac{5}{3}e^{-t} + \frac{5}{3}e^{-4t}, t > 0$.

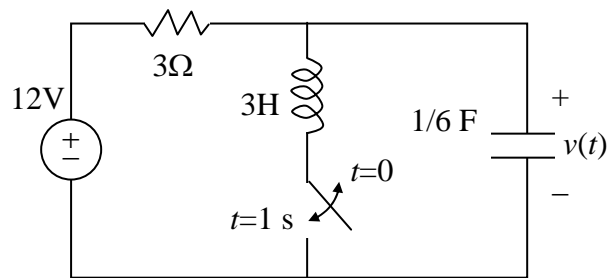5. The switch has been closed for a long time. If the switch is opened at $t=0$ and is closed again at $t=1$ sec, determine $v(t)$ for $t > 0$.



Sol:

Let the current through the inductor is $i_L(t)$. Since the switch has been closed for a long time, we

have constant $i_L(t)$ at $t=0^-$, i.e., $v(0^-) = L \left. \frac{di_L(t)}{dt} \right|_{t=0^-} = 0$.

For $1 > t > 0$, the switch is opened and then $\frac{1}{6} \frac{dv}{dt} + \frac{v-12}{3} = 0 \Rightarrow \dot{v} + 2v = 24$.

This leads to $v(t) = Ae^{-2t} + 12$ and $v(0^+) = v(0^-) = 0 \Rightarrow A + 12 = 0 \Rightarrow A = -12$.

Hence, $v(t) = -12e^{-2t} + 12$ for $1 > t > 0$ and $v(1^-) = -12e^{-2} + 12 = 10.376 = v(1^+)$.

For $t > 1$, with the switch closed again, we have a second-order circuit.

The component equations are $\frac{1}{6} \frac{dv}{dt} = i_C = \frac{12-v}{3} - i_L$ and $3 \frac{di_L}{dt} = v_L = v$, i.e.,

$$\dot{v} = -2v - 6i_L + 24 \quad \text{and} \quad \frac{di_L}{dt} = \frac{1}{3}v.$$

The initial conditions are $i_L(1^+) = 0$ and $\dot{v}(1^+) = -2v(1^+) - 6i_L(1^+) + 24 = -2(10.376) + 24 = 3.248$.

Hence, the system equation is derived as

$$\ddot{v} = -2\dot{v} - 6\frac{di_L}{dt} = -2\dot{v} - 2v \Rightarrow \ddot{v} + 2\dot{v} + 2v = 0.$$

The eigenfunction is $s^2 + 2s + 2 = 0 \Rightarrow s = -1 \pm j$, and then

$$v(t) = e^{-t}(A\cos(t) + B\sin(t)),$$

$$v(1^+) = e^{-1}(A\cos(1) + B\sin(1)) = 10.376 \Rightarrow 0.540A + 0.841B = 28.205$$

$$\dot{v}(t) = -e^{-t}(A\cos(t) + B\sin(t)) + e^{-t}(-A\sin(t) + B\cos(t)),$$

$$\dot{v}(1^+) = e^{-1}(-A[\cos(1) + \sin(1)] + B[\cos(1) - \sin(1)]) = 3.248 \Rightarrow 1.382A + 0.301B = -8.829$$

Hence, $A = -15.933$ and $B = 43.779$, i.e., $v(t) = e^{-t}(-15.933\cos(t) + 43.779\sin(t))$, $t > 1$.

The total solution is $v(t) = -12e^{-2t} + 12$

$$v(t) = \begin{cases} -12e^{-2t} + 12, & 1 > t > 0 \\ e^{-t}(-15.933\cos(t) + 43.779\sin(t)), & t > 1 \end{cases}$$