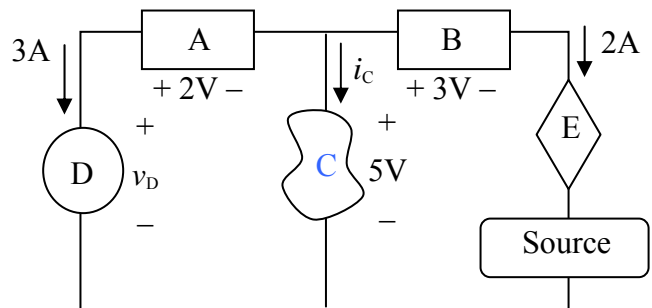


1. There are four fundamental *SI* units, m, kg, s, and A. Based on these fundamental units, some derived units are often used in electrical circuit analysis, such as C(coulomb), Ω (ohm), H(henry), and F(farad). Please write the SI units of C, Ω , H, and F.

Solution:

$$C := A \cdot s, \quad \Omega := \frac{\text{kg} \cdot \text{m}^2}{\text{s}^3 \cdot \text{A}^2}, \quad H := \frac{\text{kg} \cdot \text{m}^2}{\text{s}^2 \cdot \text{A}^2}, \quad F := \frac{\text{s}^4 \cdot \text{A}^2}{\text{kg} \cdot \text{m}^2}$$

2. What is the absorbed power p_A of device A?
 What is the absorbed power p_B of device B?
 What is the current i_C through device C?
 What is the voltage drop v_D along device D?
 If the power provided by the source is 10W,
 what is the absorbed power p_E of device E?




Solution:

$$p_A = (-3) \cdot 2 = -6\text{W}, \quad p_B = 2 \cdot 3 = 6\text{W}, \quad i_C = (-3) + (-2) = -5\text{A}, \quad v_D = 2 + 5 = 7\text{V}.$$

$$\text{Since } p_C = (-5) \cdot 5 = -25\text{W} \text{ and } p_D = 3 \cdot 7 = 21\text{W},$$

$$\text{we have } p_E = 10 - (p_A + p_B + p_C + p_D) = 10 - (-6 + 6 - 25 + 21) = 14\text{W}$$

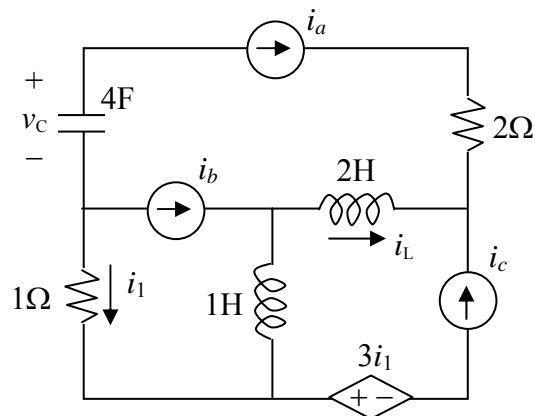3. Determine v_C , i_L , and the power absorbed by the dependent source. The independent sources in amperes for $t \geq 0$ are $i_a = e^{-2t}$, $i_b = -3e^{-4t}$, and $i_c = 5e^{-t}$. The initial capacitance voltage is $v_C(0) = 1\text{V}$.



Solution:

$$v_C = v_C(0) + \frac{1}{C} \int_0^t i_C(\tau) d\tau = 1 + \frac{1}{4} \int_0^t (-i_a(\tau)) d\tau$$

$$= 1 + \frac{1}{4} \int_0^t (-e^{-2\tau}) d\tau = 1 + \frac{1}{8} e^{-2\tau} \Big|_0^t = 1 + \frac{1}{8} e^{-2t} - \frac{1}{8} = \frac{7}{8} + \frac{1}{8} e^{-2t}$$

$$i_L = L \frac{di_L}{dt} = 2 \cdot \frac{d(-i_a - i_c)}{dt} = 2 \cdot \frac{d(-e^{-2t} - 5e^{-t})}{dt} = 4e^{-2t} + 10e^{-t}$$


$$\text{The voltage drop across the dependent source is } v = 3i_1 = -3(i_a + i_b) = -3e^{-2t} + 9e^{-4t}.$$

$$\text{The current through it is } i = i_c = 5e^{-t}.$$

$$\text{So, the power absorbed is } vi = (-3e^{-2t} + 9e^{-4t}) \cdot (5e^{-t}) = -15e^{-3t} + 45e^{-5t} \text{ W}$$

4. For the circuit on the right, $R_1=15\Omega$, $R_2=10\Omega$, and $R_3=10\Omega$.

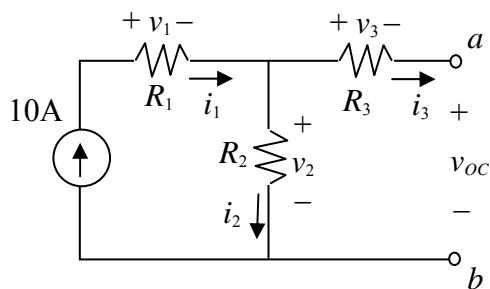- (a) Determine current i_1 and the open-circuit voltage v_{OC} . Also calculate the power absorbed by R_2 and R_3 .
- (b) Short-circuit terminals a and b , then calculate current i_1 , voltage v_2 , and the short-circuit current i_{ab} .



Solution:

(a) For the open circuit, $i_3=0$ and $i_1=i_2$.

Hence, $i_1=i_2=10A$, $v_{OC}=v_2=R_2i_2=10\cdot 10=100V$.

The power absorbed by R_2 is $v_2i_2=100\cdot 10=1000W$

The power absorbed by R_3 is $v_3i_3=0W$.

(b) For the short circuit, current i_1 does not change, that is, $i_1=10A$ and $i_2+i_3=10$.


Because $R_2=R_3$, we have $i_2=i_3$ and thus, $i_2=i_3=5A$.

The voltage drop $v_2=R_2i_2=10\cdot 5=50V$.

The short-circuit current $i_{ab}=i_3=5A$.


5. Find the equivalent resistance when connections to the network shown on the right are made to the terminals specified.

- (a) a and b (b) b and c .

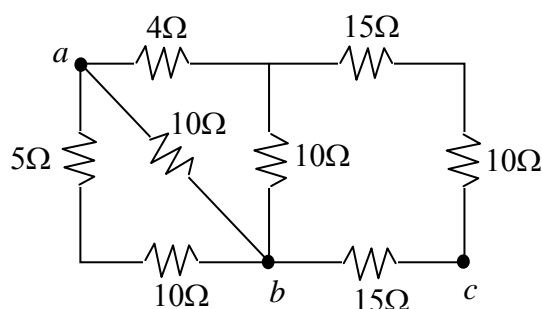


Solution:

(a) a and b

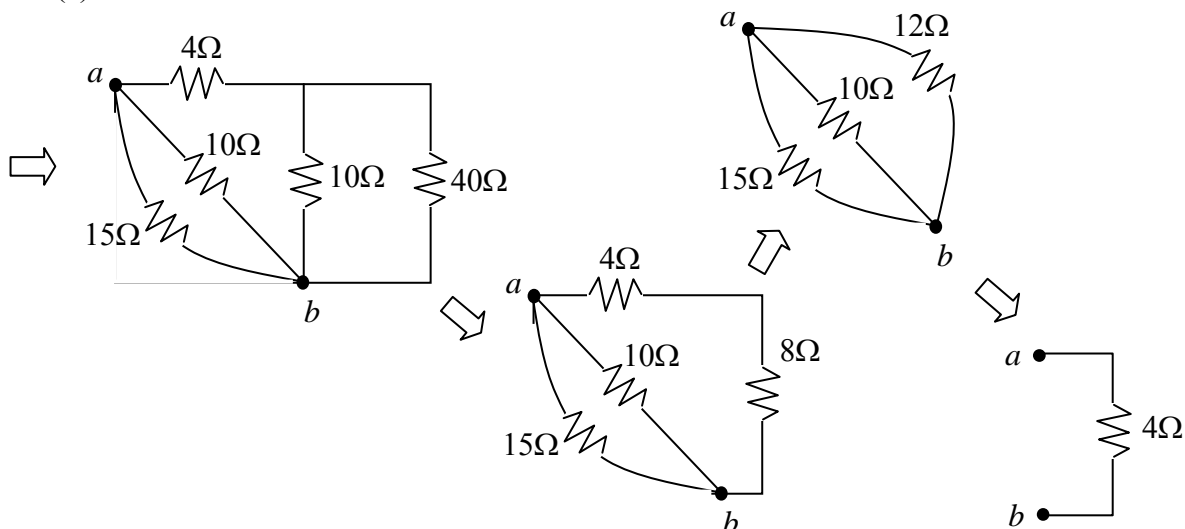

(b) *b* and *c*

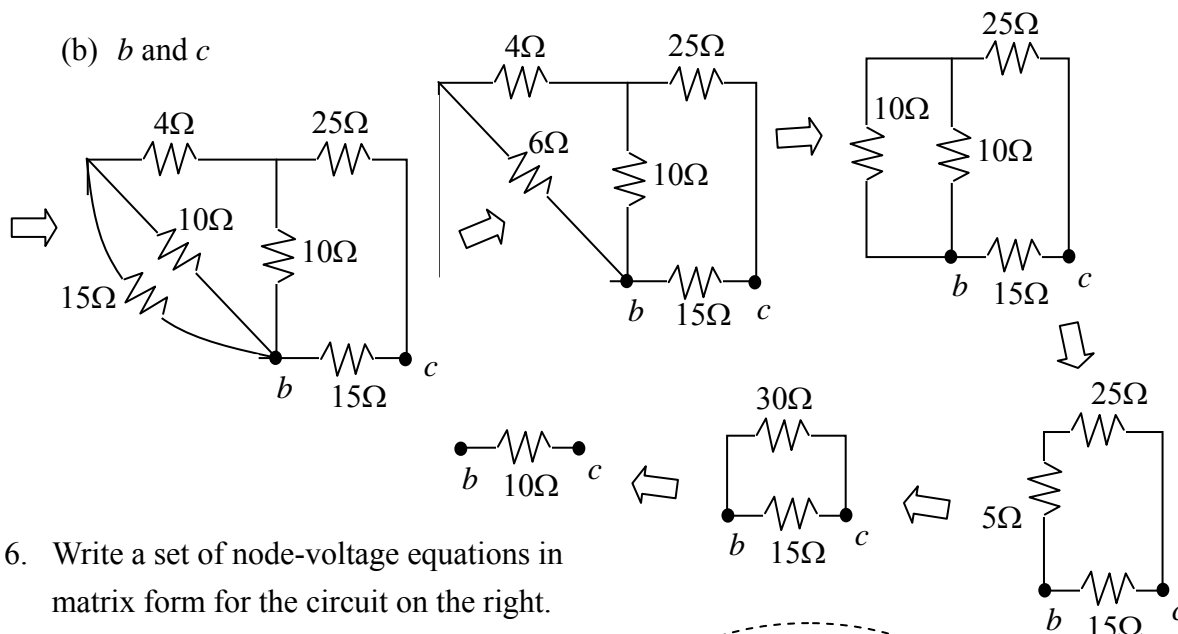


6. Write a set of node-voltage equations in matrix form for the circuit on the right. Determine current i_x .

Solution:

Group v_1 and v_2 as the supernode.

$$\text{KVL: } v_1 - v_2 = 4i_y = 2v_1 \Rightarrow v_1 + v_2 = 0$$
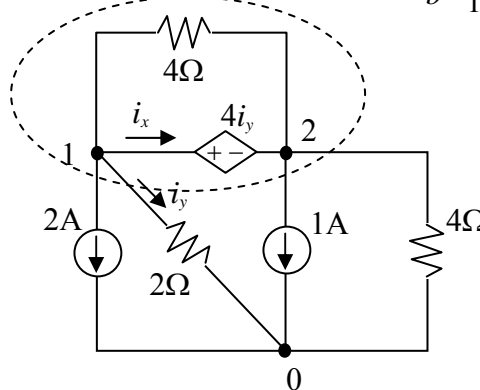
$$\text{KCL: } 2 + \frac{v_1}{2} + 1 + \frac{v_2}{4} = 0 \Rightarrow 2v_1 + v_2 = -12$$



In matrix form, we obtain $\begin{bmatrix} 1 & 1 \\ 2 & 1 \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -12 \end{bmatrix}$ and thus, $v_1 = -12\text{V}$ and $v_2 = 12\text{V}$.

$$\text{Hence, } i_x = -2 - \frac{v_1}{2} - \frac{v_2}{4} = -2 + 6 + 6 = 10\text{A}.$$


7. Write a set of mesh-current equations in matrix form for the circuit on the right. Determine voltage v_x .

Solution:

Group i_1 and i_2 as the supermesh.

$$\text{KCL: } i_2 - i_1 = 5 \Rightarrow i_1 - i_2 = -5$$

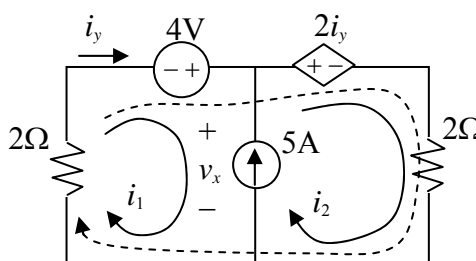
$$\text{KVL: } -4 + 2i_y + 2i_2 + 2i_1 = 0 \Rightarrow -4 + 2i_1 + 2i_2 + 2i_1 = 0 \Rightarrow 2i_1 + i_2 = 2$$



In matrix form, we obtain $\begin{bmatrix} 1 & -1 \\ 2 & 1 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -5 \\ 2 \end{bmatrix}$. The solution is $i_1 = -1\text{A}$ and $i_2 = 4\text{A}$.

$$\text{Hence, } v_x = 4 - 2i_1 = 4 + 2 = 6\text{V}.$$

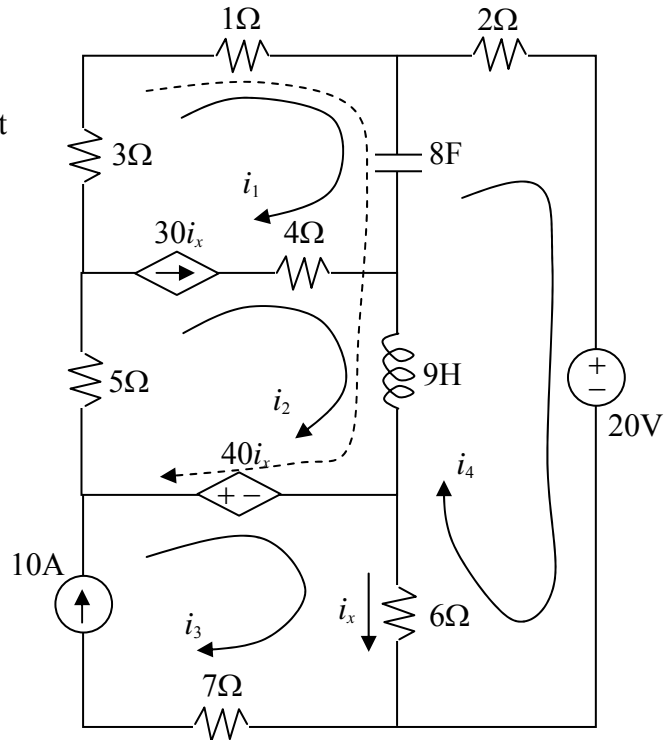8. For the circuit on the right, please define suitable mesh currents and then write a set of mesh-current equations in matrix form.



Solution:

The mesh currents are shown in the figure.

(1) KCL: $i_3 = 10$

(2) Group i_1 and i_2 as the supermesh

$$\text{KCL: } i_2 - i_1 = 30i_x = 30(i_3 - i_4)$$

$$\Rightarrow i_1 - i_2 + 30i_3 - 30i_4 = 0$$

$$\text{KVL: } -40i_x + 5i_2 + 3i_1 + i_1 + \frac{1}{8} \int_{-\infty}^t (i_1 - i_4) d\tau + 9 \frac{d(i_2 - i_4)}{dt} = 0$$

$$\Rightarrow 4i_1 + \frac{1}{8} \int_{-\infty}^t i_1 d\tau + 5i_2 + 9 \frac{di_2}{dt} - 40i_3 + 40i_4 - \frac{1}{8} \int_{-\infty}^t i_4 d\tau - 9 \frac{di_4}{dt} = 0$$

(3) KVL: $20 + 6(i_4 - i_3) + 9 \frac{d(i_4 - i_2)}{dt} + \frac{1}{8} \int_{-\infty}^t (i_4 - i_1) d\tau + 2i_4 = 0$

$$\Rightarrow -\frac{1}{8} \int_{-\infty}^t i_1 d\tau - 9 \frac{di_2}{dt} - 6i_3 + 8i_4 + 9 \frac{di_4}{dt} + \frac{1}{8} \int_{-\infty}^t i_4 d\tau = -20$$

In matrix form, we have

$$\begin{bmatrix} 1 & -1 & 30 & -30 \\ 4 + \frac{1}{8} \int_{-\infty}^t d\tau & 5 + 9 \frac{d}{dt} & -40 & 40 - \frac{1}{8} \int_{-\infty}^t d\tau - 9 \frac{d}{dt} \\ 0 & 0 & 1 & 0 \\ -\frac{1}{8} \int_{-\infty}^t d\tau & -9 \frac{d}{dt} & -6 & 8 + 9 \frac{d}{dt} + \frac{1}{8} \int_{-\infty}^t d\tau \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 10 \\ -20 \end{bmatrix}$$