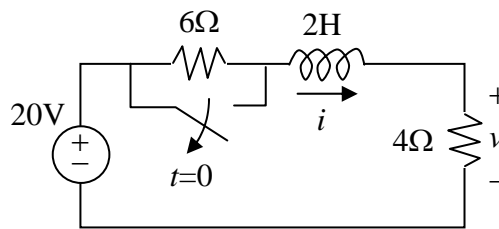


1. The switch has been closed for a long time and is opened at  $t=0$ . Solve for  $v(t)$  for  $t>0$ .



**Solution:**

The component equation is  $v_L = 2 \frac{di}{dt}$ .

The system equation is  $20 = Ri + v_L = Ri + 2 \frac{di}{dt} \Rightarrow \frac{di}{dt} + \frac{R}{2} i = 10$ .

For  $t < 0$ , we have  $R=4\Omega$  and then  $\frac{di}{dt} + 2i = 10$ . Since the switch has been closed for a long time, it implies  $i(0^-)$  is a constant and then  $2i(0^-) = 10 \Rightarrow i(0^-) = 5 \text{ A}$ .


For  $t > 0$ , we have  $R=4+6=10\Omega$  and then  $\frac{di}{dt} + 5i = 10$ .

The current is solved as  $i(t) = Ae^{-5t} + 2$ .

From the initial condition  $i(0^+) = i(0^-) = 5$ , we obtain  $A=3$ , i.e.,  $i(t) = 3e^{-5t} + 2$ , for  $t > 0$ .

This results in  $v(t) = 4i(t) = 12e^{-5t} + 8$ , for  $t > 0$ .

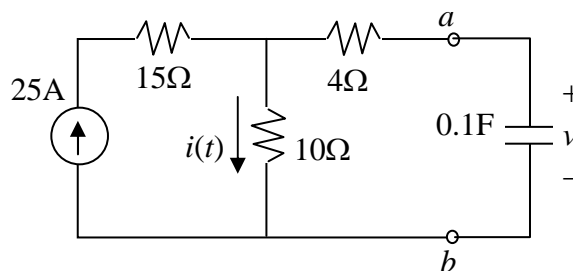2. Find the Thevenin equivalent circuit for the circuit to the left of terminals  $a$  and  $b$ . If  $v(0^-) = 2 \text{ V}$ , what is  $i(t)$  for  $t > 0$ ?



**Solution:**

The Thevenin equivalent resistance is

$$R_{Th} = 4 + 10 = 14 \Omega.$$

The open-circuit voltage is  $v_{OC} = 10 \cdot 25 = 250 \text{ V}$ .

Hence, the Thevenin circuit is shown on the right.


The component equation is  $i_C = 0.1 \frac{dv}{dt}$ .

The system equation is  $250 = 14i_C + v = 1.4 \frac{dv}{dt} + v \Rightarrow \frac{dv}{dt} + \frac{5}{7}v = \frac{1250}{7}$ .

For  $t > 0$ , we have  $v(t) = Ae^{-\frac{5}{7}t} + 250$ .

From the initial condition  $v(0^-) = 2$ , we obtain  $A = -248$ , i.e.,  $v(t) = -248e^{-\frac{5}{7}t} + 250$ , for  $t > 0$ .

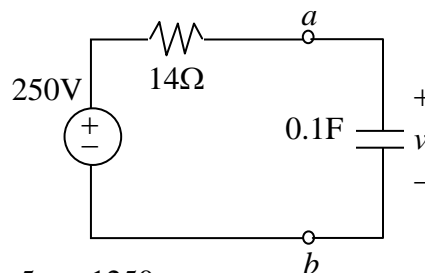This results in  $i(t) = 25 - i_C(t) = 25 - 0.1 \cdot \left( \frac{1240}{7} e^{-\frac{5}{7}t} \right) = 25 - \frac{124}{7} e^{-\frac{5}{7}t}$ , for  $t > 0$ .



3. Use superposition to determine current  $i_x$  in the circuit on the right.

**Solution:**

(1)  $i_{x1}$

$$-i_{x1} + \frac{30 - 6i_{x1}}{3} + \frac{30 - 6i_{x1} - 2i_{x1}}{2} = 0$$

$$\Rightarrow i_{x1} = \frac{25}{7}$$

(2)  $i_{x2}$

$$-i_{x2} + 1 + \frac{-6i_{x2}}{3} + \frac{-6i_{x2} - 2i_{x2}}{2} = 0$$

$$\Rightarrow i_{x2} = \frac{1}{7}$$





(3)  $i_{x3}$

$$-i_{x3} + \frac{-6i_{x3}}{3} + \frac{-6i_{x3} - 10 - 2i_{x3}}{2} = 0$$

$$\Rightarrow i_{x3} = \frac{-5}{7}$$


Hence,
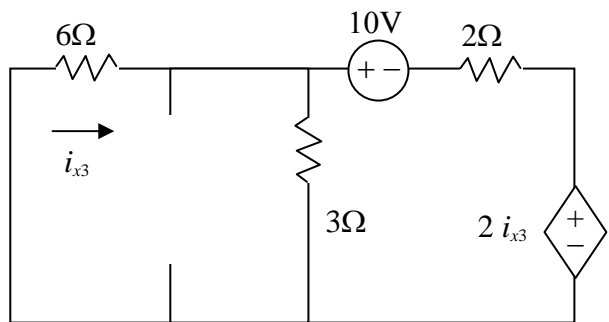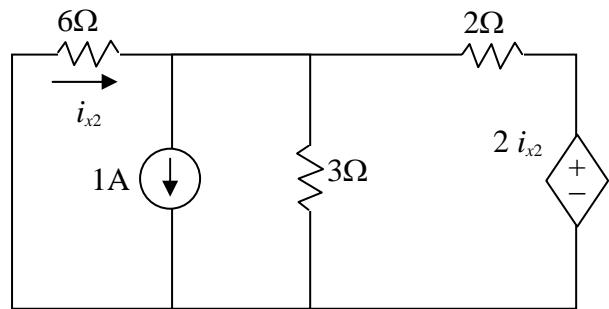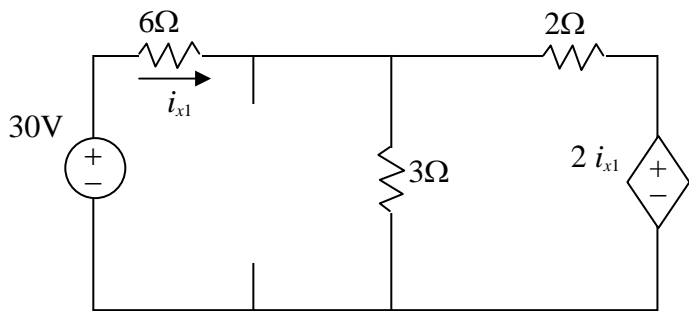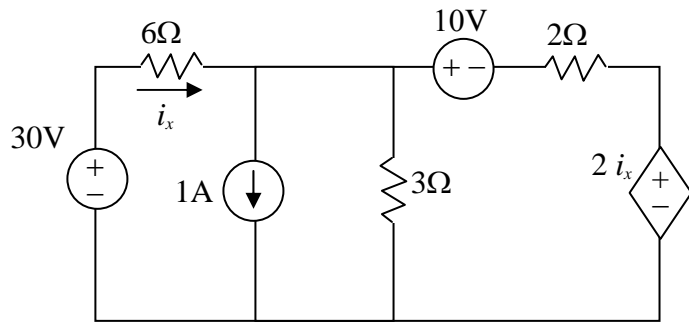
$$i_x = i_{x1} + i_{x2} + i_{x3} = \frac{25}{7} + \frac{1}{7} - \frac{5}{7} = 3 \text{ A}$$




4. (a) Determine the Norton equivalent circuit to the left of terminals  $a$  and  $b$ .

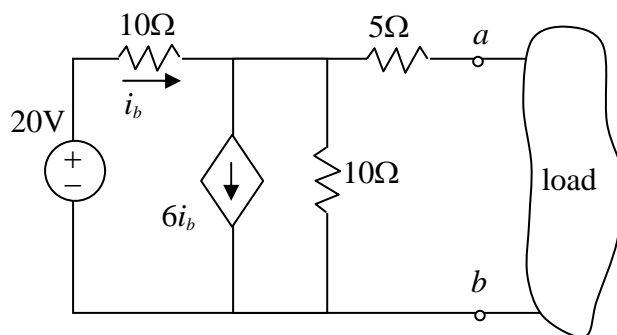- (b) If the load can absorb maximum power from the source, what is the equivalent resistance to the right of terminals  $a$  and  $b$ ? What is the maximum power?



**Solution:**

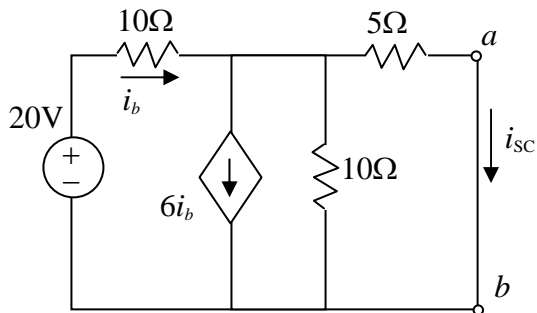(a) Norton equivalent circuit is derived as below:



<i>  $i_{sc}$ :

$$i_b = \frac{20 - 5i_{sc}}{10},$$


$$-i_b + 6i_b + \frac{5i_{sc}}{10} + i_{sc} = 0 \Rightarrow i_b = -\frac{3}{10}i_{sc} = \frac{20 - 5i_{sc}}{10} \Rightarrow i_{sc} = 10 \text{ A}$$

<ii>  $R_N$  (idle source)

$$i_b = -\frac{v_t - 5i_t}{10}$$

$$-i_b + 6i_b + \frac{-10i_b}{10} - i_t = 0$$

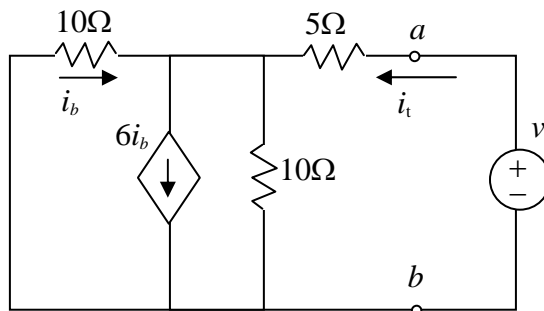
$$\Rightarrow i_t = 4i_b = -\frac{2v_t - 10i_t}{5} \Rightarrow i_t = 0.4v_t$$



Hence,  $R_N = \frac{v_t}{i_t} = 2.5 \Omega$ .

The Norton equivalent circuit is shown on the right.

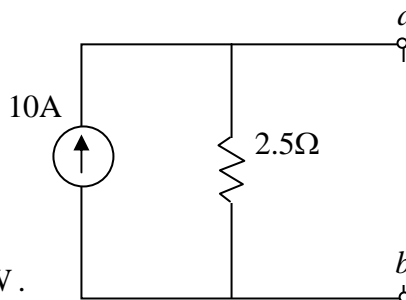(b) The equivalent resistance of the load that absorbs maximum power is  $R_L = R_N = 2.5 \Omega$ .




The maximum power is  $R_L \left( 10 \times \frac{2.5}{2.5 + R_L} \right)^2 = 62.5 \text{ W}$ .

5. (a) Find the output voltages  $v_o$  in terms of  $v_1$ ,  $v_2$  and  $v_3$ .

(b) Let  $v_1 = 2\cos(\omega t)$ ,  $v_2 = \sin(2\omega t)$  and

$$v_3 = \sin(\omega t - 0.25\pi) \text{ in volt.}$$

What is the effective value of  $v_o$ ?

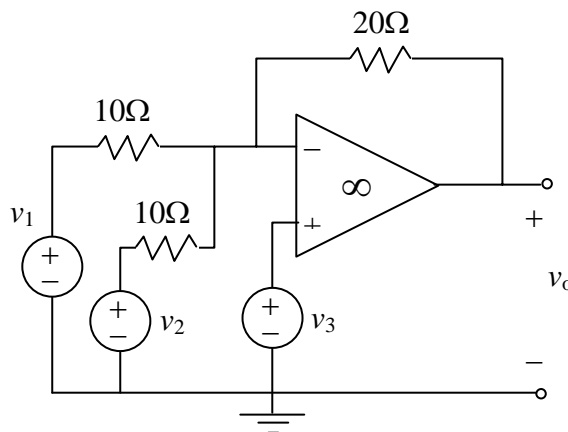

**Solution:**

$$(a) \quad i_1 = \frac{v_1 - v_3}{10}, \quad i_2 = \frac{v_2 - v_3}{10}, \quad i = \frac{v_3 - v_o}{20}$$

Since  $i = i_1 + i_2$ , we have


$$\begin{aligned} \frac{v_3 - v_o}{20} &= \frac{v_1 - v_3}{10} + \frac{v_2 - v_3}{10} \\ \Rightarrow v_o &= -2v_1 - 2v_2 + 5v_3 \end{aligned}$$

(b) The output voltage is

$$\begin{aligned} v_o &= -2v_1 - 2v_2 + 5v_3 \\ &= -4\cos(\omega t) - 2\sin(2\omega t) + 5\sin(\omega t - 0.25\pi) \\ &= -4\cos(\omega t) - 2\sin(2\omega t) + \frac{5}{\sqrt{2}}[\sin(\omega t) - \cos(\omega t)] \\ &= -\left(4 + \frac{5\sqrt{2}}{2}\right)\cos(\omega t) + \frac{5\sqrt{2}}{2}\sin(\omega t) - 2\sin(2\omega t) \end{aligned}$$


The effective value of  $v_o$  is
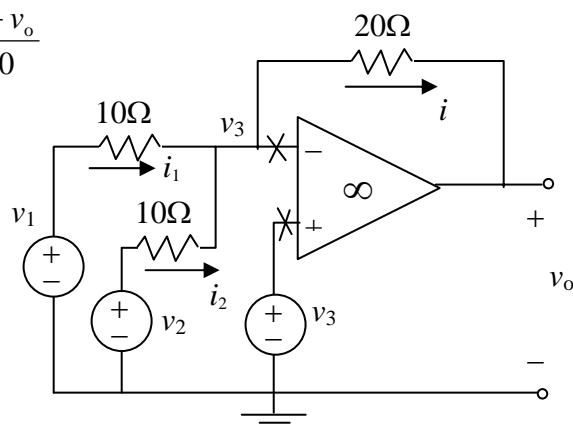
$$V_{eff} = \sqrt{\frac{\left(4 + \frac{5\sqrt{2}}{2}\right)^2 + \left(\frac{5\sqrt{2}}{2}\right)^2 + 2^2}{2}} = \sqrt{\frac{45 + 20\sqrt{2}}{2}} = 6.0533$$



6. Find the output voltages  $v_o$


if  $v_1 = 2$  V and  $v_2 = 1$  V.

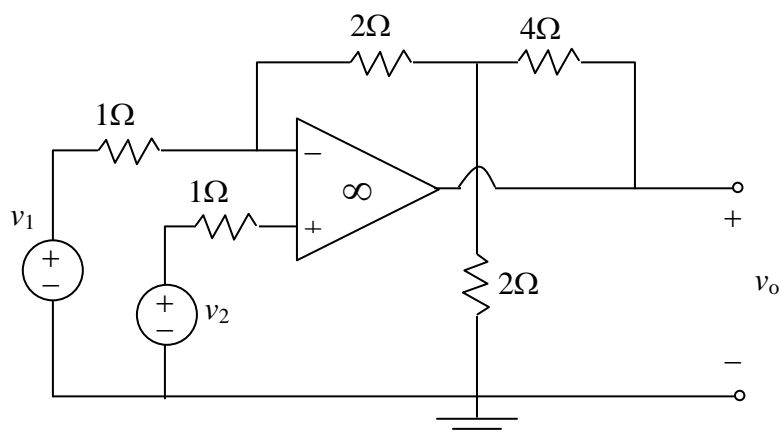
**Solution:**

$$i_1 = \frac{v_2 - v}{2} = \frac{v_1 - v_2}{1} = 1 \text{ A} \Rightarrow v = -1 \text{ V}$$

$$i = \frac{v}{2} = -0.5 \text{ A}, \quad i_o = \frac{v - v_o}{4} = i_1 - i = 1.5 \text{ A}$$

Hence,  $v_o = -7$  V

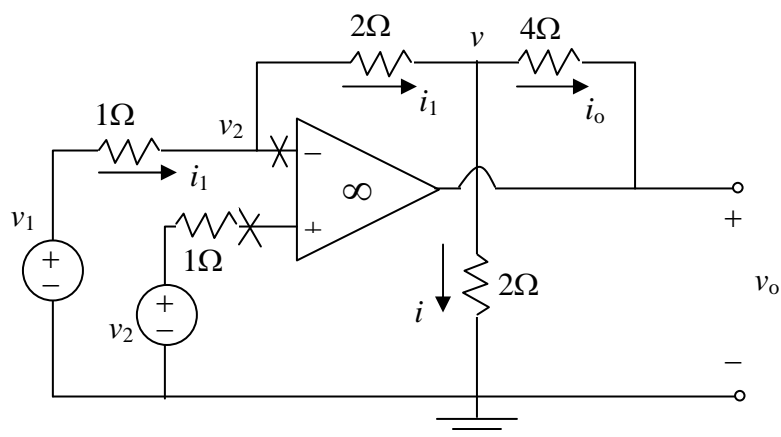

7. Consider the following first order differential equation:

$$\dot{y}(t) + 2y(t) = u(t), \quad y(0) = 1.$$

(a) If  $u(t) = t + 2e^{-3t}$ , determine  $y(t)$  for  $t > 0$ .

(b) If  $u(t) = 4\sin(2t)$ , determine  $y(t)$  for  $t \rightarrow \infty$ .

**Solution:**

(a) The total solution is  $y(t) = Ae^{-2t} + y_p(t)$ , where

$$\dot{y}_p(t) + 2y_p(t) = t + 2e^{-3t}$$

Let  $y_p(t) = \alpha t + \beta + \gamma e^{-3t}$ , then  $\dot{y}_p(t) = \alpha - 3\gamma e^{-3t}$  and

$$\alpha - 3\gamma e^{-3t} + 2\alpha t + 2\beta + 2\gamma e^{-3t} = t + 2e^{-3t}.$$

It results in  $\alpha = \frac{1}{2}$ ,  $\beta = -\frac{1}{4}$ ,  $\gamma = -2$ , i.e.,  $y_p(t) = \frac{1}{2}t - \frac{1}{4} - 2e^{-3t}$ .

Since  $y(0) = 1$ , we have  $y(0) = A + y_p(0) \Rightarrow 1 = A - \frac{9}{4} \Rightarrow A = \frac{13}{4}$ .

Hence,  $y(t) = \frac{13}{4}e^{-2t} + \frac{1}{2}t - \frac{1}{4} - 2e^{-3t}$ .

(b) For  $t \rightarrow \infty$ ,  $y(t) = 4 \left| \frac{1}{j2+2} \right| \sin\left(2t + \angle \frac{1}{j2+2}\right) = \sqrt{2} \sin\left(2t - \frac{\pi}{4}\right) = \sin(2t) - \cos(2t)$