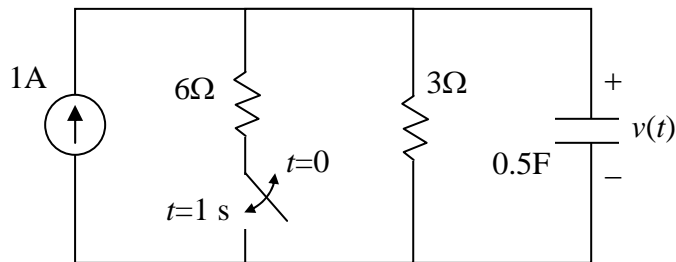


1. The switch has been closed for a long time. If the switch is opened at $t=0$ and is closed again at $t=1$ sec, determine $v(t)$ for $t>0$.



Sol:

Since the switch has been closed for a long time, we have $0.5 \frac{dv}{dt} + \frac{v}{3} + \frac{v}{6} = 1$, where $\frac{dv}{dt}(0^-) = 0$.

Hence, $v(0^-) = 2$ V.

For $t>0$, the switch is opened and then $0.5 \frac{dv}{dt} + \frac{v}{3} = 1 \Rightarrow \frac{dv}{dt} + \frac{2v}{3} = 2$.

This leads to $v(t) = Ae^{-\frac{2}{3}t} + 3$ and $v(0^+) = v(0^-) = 2 \Rightarrow A + 3 = 2 \Rightarrow A = -1$.

Hence, $v(t) = -e^{-\frac{2}{3}t} + 3$ for $t>0$.

For $t>1$, the switch is closed again and then $0.5 \frac{dv}{dt} + \frac{v}{3} + \frac{v}{6} = 1$, where $v(1^-) = -e^{-\frac{2}{3}} + 3$.


We have $0.5 \frac{dv}{dt} + \frac{v}{2} = 1$ and then $v(t) = Be^{-\frac{1}{2}t} + 2$.

Moreover, $v(1^+) = v(1^-) = -e^{-\frac{2}{3}} + 3 \Rightarrow Be^{-\frac{1}{2}} + 2 = -e^{-\frac{2}{3}} + 3 \Rightarrow B = -e^{-\frac{1}{6}} + e^{\frac{1}{2}} = 0.8022$.

This results in $v(t) = 0.8022e^{-\frac{1}{2}t} + 2$ V.

The total solution for $t>0$ is
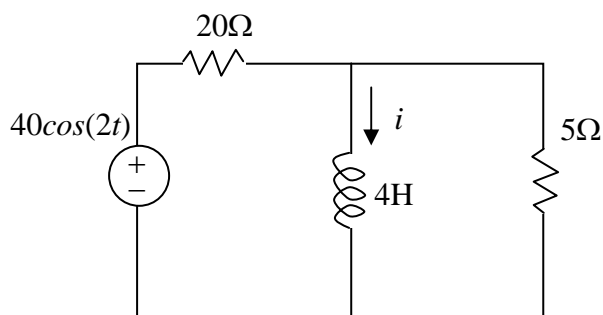
$$v(t) = \begin{cases} -e^{-\frac{2}{3}t} + 3, & 0 < t < 1 \\ 0.8022e^{-\frac{1}{2}t} + 2, & t > 1 \end{cases}$$



2. If $i(0^-) = 1$, determine $i(t)$ for $t>0$.

Sol:

The equation is $i + \left(4 \frac{di}{dt}\right) \frac{1}{5} + \left(4 \frac{di}{dt} - 40 \cos(2t)\right) \frac{1}{20} = 0 \Rightarrow \frac{di}{dt} + i = 2 \cos(2t)$.


First, calculate $\left. \frac{1}{D+1} \right|_{D=j2} = \left. \frac{1}{1+j2} \right| = \frac{1}{\sqrt{5}} \angle \theta$, where $\cos \theta = \frac{1}{\sqrt{5}}$ and $\sin \theta = -\frac{2}{\sqrt{5}}$.

Hence,

$$\begin{aligned} i(t) &= Ae^{-t} + \frac{2}{\sqrt{5}} \cos(2t + \theta) \\ &= Ae^{-t} + \frac{2}{\sqrt{5}} (\cos(2t)\cos\theta - \sin(2t)\sin\theta). \\ &= Ae^{-t} + \frac{2}{5} \cos(2t) + \frac{4}{5} \sin(2t) \end{aligned}$$

Furthermore, $i(0^+) = i(0^-) = 1 \Rightarrow A + \frac{2}{5} = 1 \Rightarrow A = \frac{3}{5}$.

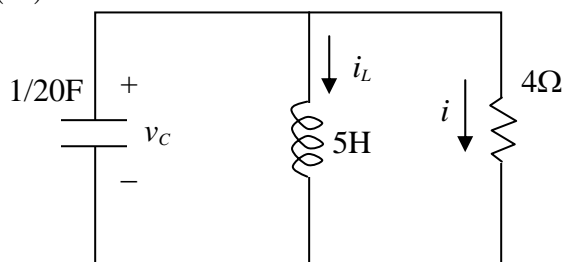The total solution is $i(t) = \frac{3}{5}e^{-t} + \frac{2}{5}\cos(2t) + \frac{4}{5}\sin(2t)$.



3. If $i_L(0^-) = 3$, $v_C(0^-) = 0$, determine $i(t)$ for $t > 0$.

Sol:

The component equations are

$$C \dot{v}_C = i_C = -i_L - \frac{v_C}{R} \Rightarrow \dot{v}_C(0^+) = -\frac{i_L(0^+)}{C} - \frac{v_C(0^+)}{RC} = -\frac{i_L(0^-)}{C} - \frac{v_C(0^-)}{RC} = -60$$

$$L \frac{di_L}{dt} = v_L = v_C$$

The system equation is derived as $\ddot{v}_C = \frac{1}{C} \frac{di_C}{dt} = -\frac{1}{C} \frac{di_L}{dt} - \frac{1}{RC} \dot{v}_C = -\frac{1}{RC} \dot{v}_C - \frac{1}{LC} v_C$,

i.e., $\ddot{v}_C + \frac{1}{LC} v_C + \frac{1}{RC} \dot{v}_C = 0$, $v_C(0^+) = v_C(0^-) = 0$ and $\dot{v}_C(0^+) = -60$.

We have

$$\ddot{v}_C + 5\dot{v}_C + 4v_C = 0, \quad v_C(0^+) = v_C(0^-) = 0 \quad \text{and} \quad \dot{v}_C(0^+) = -60$$


which results in eigenfunction $s^2 + 5s + 4 = 0 \Rightarrow s = -1, -4$, and then

$$v_C(t) = Ae^{-t} + Be^{-4t}, \quad v_C(0^+) = A + B = 0$$

$$\dot{v}_C(t) = -Ae^{-t} - 4Be^{-4t}, \quad \dot{v}_C(0^+) = -A - 4B = -60.$$

Hence, $A = -20$ and $B = 20$, i.e., $v_C(t) = -20e^{-t} + 20e^{-4t}$, $t > 0$.

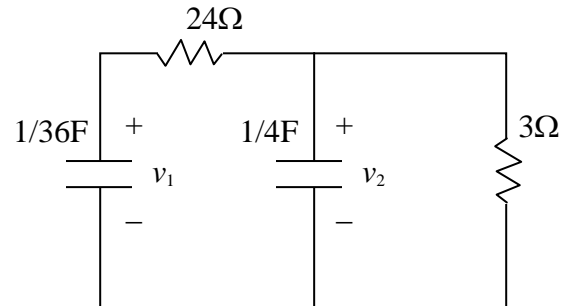The current $i(t) = \frac{v_C(t)}{4} = -5e^{-t} + 5e^{-4t}$, $t > 0$.



4. If $v_1(0^-)=1$, $v_2(0^-)=1$, determine $v_1(t)$ for $t>0$.

Sol:

The component equations are

$$\frac{1}{36} \dot{v}_1 = i_{C1} = \frac{v_2 - v_1}{24} \Rightarrow \dot{v}_1(0^+) = 3 \cdot \frac{v_2(0^+) - v_1(0^+)}{2} = 0$$

$$\frac{1}{4} \dot{v}_2 = i_{C2} = -i_{C1} - i = \frac{v_1 - v_2}{24} - \frac{v_2}{3} = \frac{v_1}{24} - \frac{3v_2}{8} \Rightarrow \dot{v}_2 = \frac{v_1}{6} - \frac{3v_2}{2}$$

The system equation is derived as

$$\dot{v}_1 = \frac{3}{2}(v_2 - v_1)$$

$$\Rightarrow \ddot{v}_1 = \frac{3}{2}(\dot{v}_2 - \dot{v}_1) = \frac{3}{2} \left(\left(\frac{v_1}{6} - \frac{3v_2}{2} \right) - \dot{v}_1 \right) = \left(\frac{v_1}{4} - \frac{9v_2}{4} \right) - \frac{3}{2} \dot{v}_1$$

$$\Rightarrow \ddot{v}_1 + \frac{3}{2} \dot{v}_1 - \frac{v_1}{4} = -\frac{9}{4} v_2 = -\frac{9}{4} \left(\frac{2}{3} \dot{v}_1 + v_1 \right) = -\frac{3}{2} \dot{v}_1 - \frac{9}{4} v_1$$

$$\Rightarrow \ddot{v}_1 + 3\dot{v}_1 + 2v_1 = 0$$

We have

$$\ddot{v}_1 + 3\dot{v}_1 + 2v_1 = 0, \quad v_1(0^+) = v_1(0^-) = 1 \quad \text{and} \quad \dot{v}_1(0^+) = 0.$$

which results in eigenfunction $s^2 + 3s + 2 = 0 \Rightarrow s = -1, -2$, and then

$$v_1(t) = Ae^{-t} + Be^{-2t}, \quad v_1(0^+) = A + B = 1$$

$$\dot{v}_1(t) = -Ae^{-t} - 2Be^{-2t}, \quad \dot{v}_1(0^+) = -A - 2B = 0.$$

Hence, $A = 2$ and $B = -1$. The total solution is $v_1(t) = 2e^{-t} - e^{-2t}$, $t > 0$.