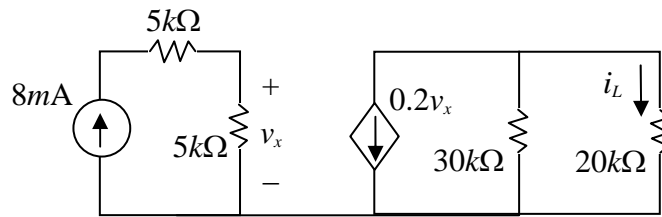


1. Find the load current i_L .




Solution:

The voltage $v_x = 8 \times 10^{-3} \times 5 \times 10^3 = 40 \text{ V}$



The load current

$$i_L = -0.2 v_x \times \frac{30 \times 10^3}{30 \times 10^3 + R_L} = -0.2 \times 40 \times \frac{30 \times 10^3}{30 \times 10^3 + 20 \times 10^3} = -4.8 \text{ A}$$

2. Transform the circuit from Y to Δ .

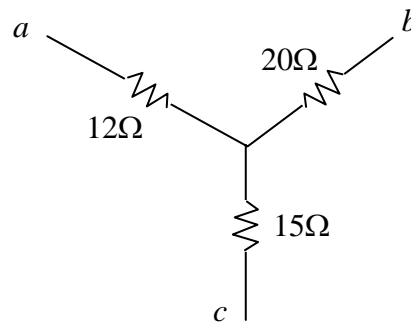

Solution:

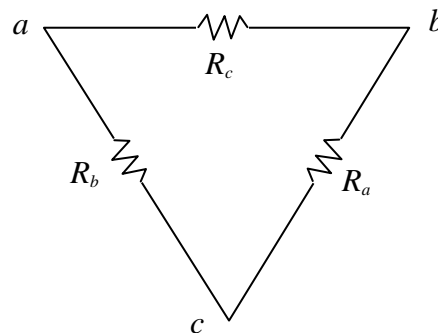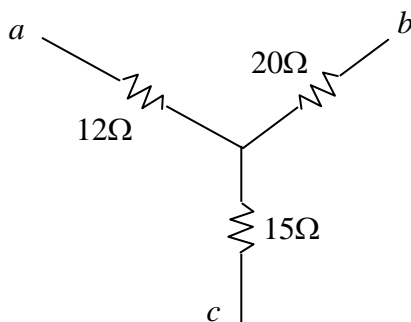


According to the transformation formula, we have

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{12 \times 20 + 20 \times 15 + 15 \times 12}{12} = \frac{720}{12} = 60 \text{ } \Omega$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{12 \times 20 + 20 \times 15 + 15 \times 12}{20} = \frac{720}{20} = 36 \text{ } \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{12 \times 20 + 20 \times 15 + 15 \times 12}{15} = \frac{720}{15} = 48 \text{ } \Omega$$

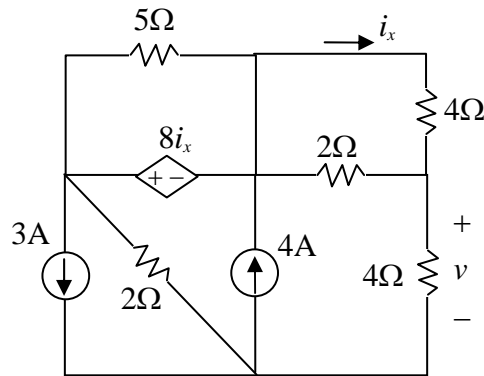3. Based on the mesh-current method, write a set of mesh current equations and determine the voltage v in the circuit.



Solution:

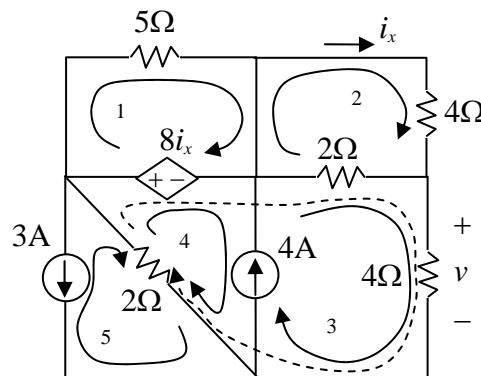

First, number the mesh current i_1, i_2, i_3, i_4 and i_5 .

There is a supermesh containing 3 and 4. The mesh current equations are

$$\text{KVL } 1: 5i_1 - 8i_x = 5i_1 - 8i_2 = 0 \quad (1)$$

$$\text{KVL } 2: 4i_2 + 2(i_2 - i_3) = 6i_2 - 2i_3 = 0 \quad (2)$$

$$\text{Supermesh } 3 \ 4: \text{KCL: } i_3 - i_4 = 4 \quad (3)$$


$$\text{KVL: } 2(i_4 - i_5) + 8i_2 + 2(i_3 - i_2) + 4i_3 = 6i_2 + 6i_3 + 2i_4 - 2i_5 = 0 \quad (4)$$

$$\text{KCL } 5: i_5 = -3 \quad (5)$$

$$\text{From (3)+(4)/2+(5), we have } 3i_2 + 4i_3 = 1 \quad (6)$$


From (6)-(2)/2, we have $5i_3 = 1$, i.e., $i_3 = 0.2$. Therefore, $v = 0.8$ V.

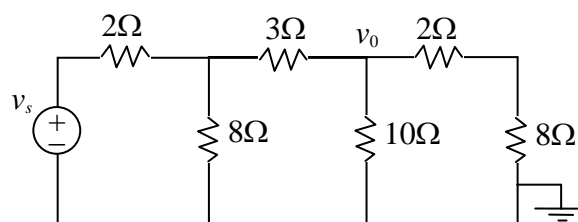4. (A) For the circuit below, if $v_0 = 1$ V, then find the source voltage v_s .
 (B) Based on linearity, if $v_s = 10$ V, determine v_0 .




Solution:

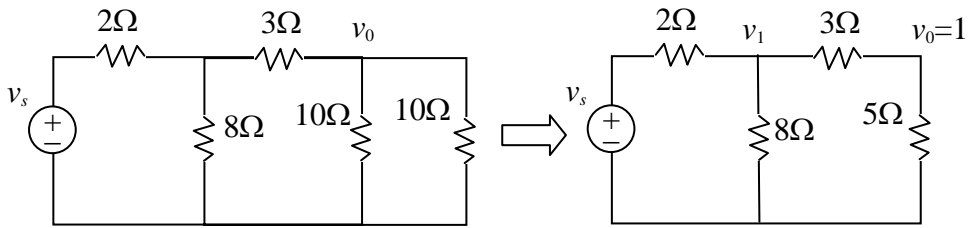(A) The circuit can be simplified as below:



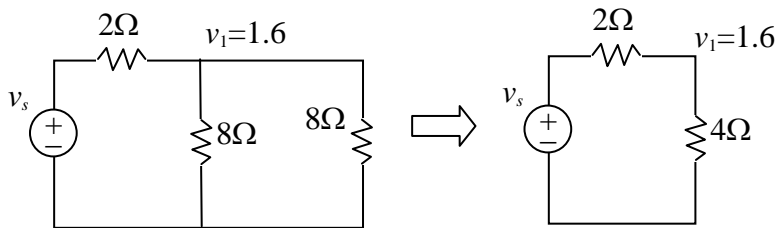
where $v_1 = \frac{8}{5}v_0 = 1.6 \text{ V}$. The circuit can be further simplified as below:



where $v_s = \frac{2+4}{4}v_1 = 2.4 \text{ V}$.


(B) From the linearity, if $v_s = 10 \text{ V}$, increased by a ratio $10/2.4$ to the value of v_s in (A), then the voltage v_0 will be also increased by the same ratio, i.e., $v_0 = 1 \times 10 / 2.4 = 25 / 6 \text{ V}$.

5. Use superposition to find v .

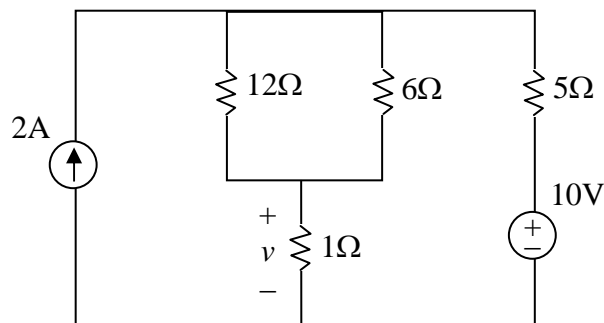


Solution:

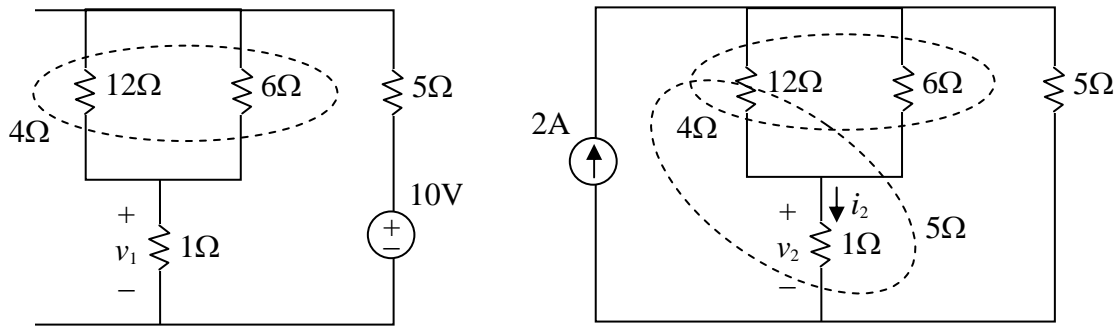The circuit can be solved by two cases. One takes away the current source and the other deletes the voltage source, shown as below:





The parallel resistances are equivalent to $\left(\frac{1}{12} + \frac{1}{6}\right)^{-1} = \frac{12}{1+2} = 4\Omega$. Then, the series resistances 4Ω and 1Ω are equivalent to 5Ω , as shown in the above circuits. Hence, from voltage division, we have $v_1 = 10 \times \frac{1}{5+4+1} = 1$. From current division, we have $i_2 = 2 \times \frac{5}{5+5} = 1$ and $v_2 = 1 \times i_2 = 1$. Based on superposition, the voltage $v = v_1 + v_2 = 1 + 1 = 2\text{V}$. then choose the reference point and number the node voltages v_1 , v_2 and v_3 .

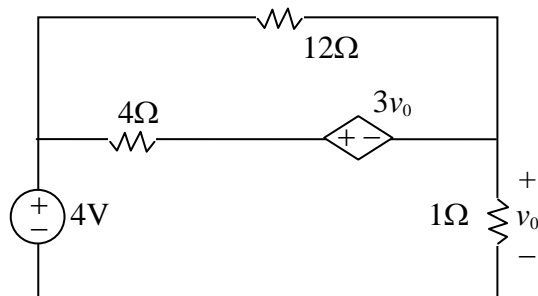6. Use source transformation to find v_0 .



Solution:

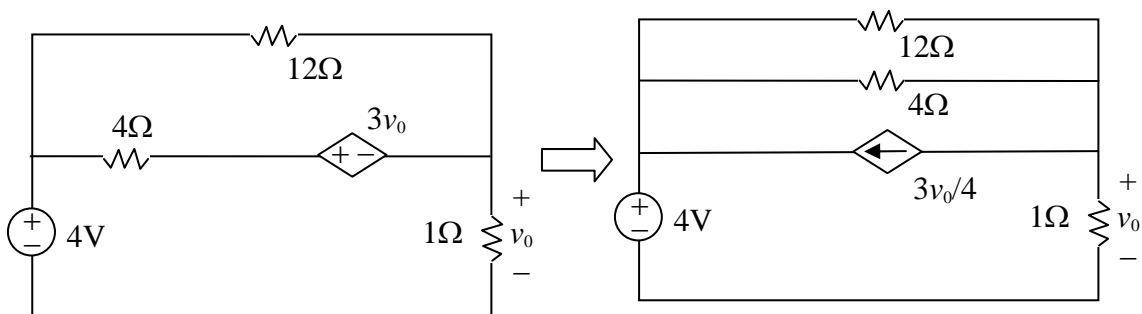


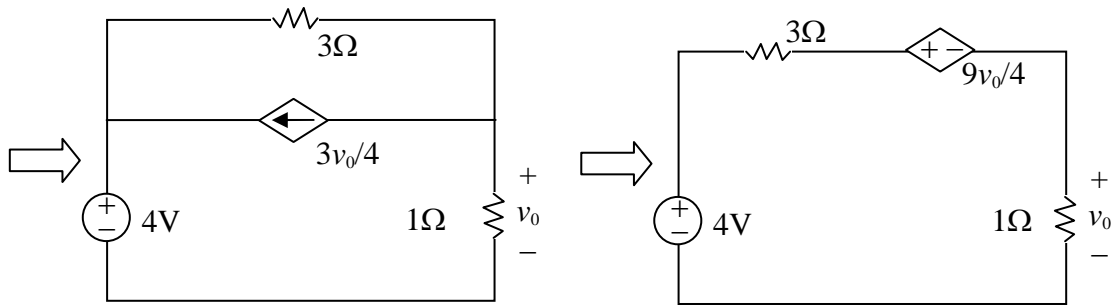

Since the voltage across 1Ω is v_0 , we know the voltage across 3Ω is $3v_0$. Hence, we have


$$3v_0 + 9v_0/4 + v_0 = 4 \Rightarrow v_0 = 0.64 \text{ V}$$

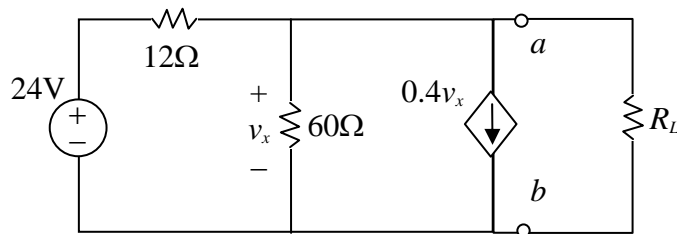7. Find the Norton equivalent circuits with respect to terminals a and b . What is the maximum power transferred to the load R_L .




Solution:

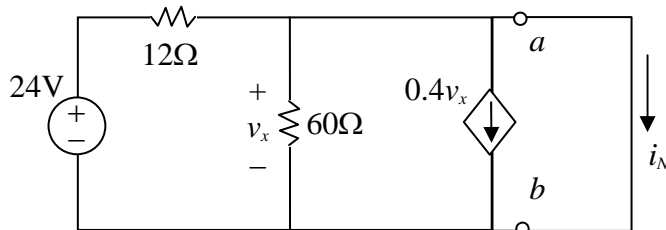First, find the Norton equivalent current i_N from the following circuit:



Clearly, $v_x=0$ and thus i_N is the same as the current through 12Ω , i.e., $i_N = \frac{24}{12} = 2 \text{ A}$.

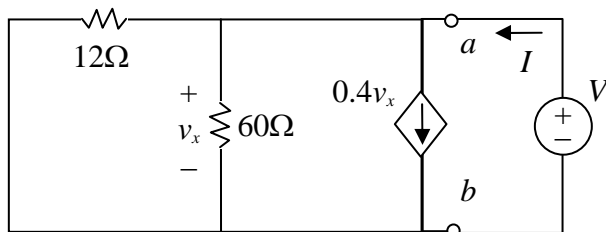The Norton resistance R_N can be determined by adding an extra voltage V as below:




It is easy to find that $I = \frac{V}{12} + \frac{V}{60} + 0.4v_x = \frac{V}{12} + \frac{V}{60} + 0.4V = 0.5V$

which leads to $R_N = \frac{V}{I} = 2 \Omega$

Therefore, when $R_L = R_N = 2\Omega$, the power transferred to the load is maximal and the maximum power is


$$P_{max} = R_N \left(\frac{1}{2} i_N \right)^2 = 2 \left(\frac{1}{2} \times 2 \right)^2 = 2 \text{ W}$$

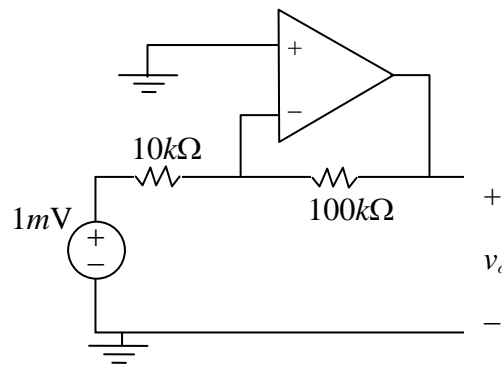8. The following op amp has $R_i = 100k\Omega$, $R_o = 100\Omega$, $A = 1000$. Find the output voltage v_o .



Solution:

The equivalent circuit is

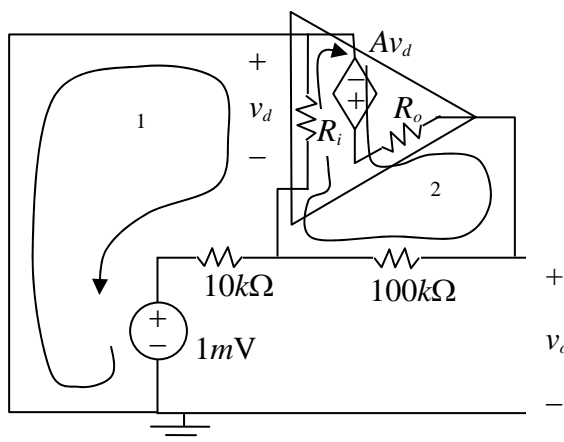

Hence, based on mesh current method, we have

$$10^5(i_1 - i_2) + 10^4 i_1 + 10^{-3} = 0$$

$$10^5(i_2 - i_1) - 10^3 \times 10^5(i_1 - i_2) + 100i_2 + 10^5 i_2 = 0$$


which can be rewritten as

$$11i_1 - 10i_2 + 10^{-7} = 0 \quad \text{and} \quad i_1 = 1.001i_2$$


Hence, $i_1 \approx -0.9901 \times 10^{-7}$ and $i_2 \approx -0.9891 \times 10^{-7}$.

We have $v_o = 10^5 i_2 + 10^4 i_1 + 10^{-3} \approx -0.0099 \text{ V}$.

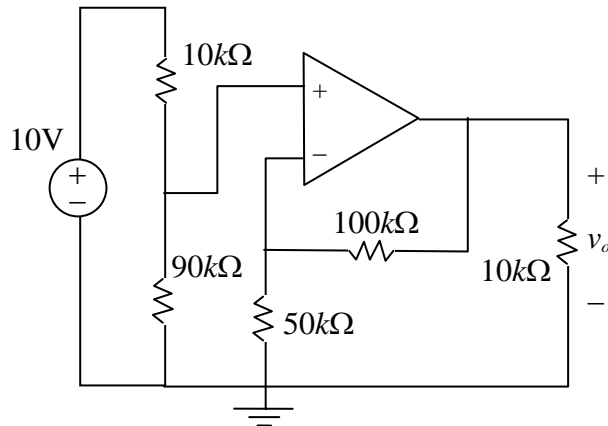9. The following circuit contains an ideal op amp, find the output voltage v_o .



Solution:

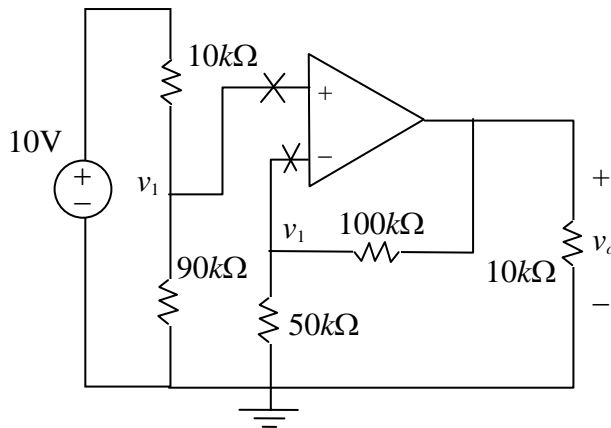

Since the input currents to the op amp is negligible, we have $v_1 = 10 \times \frac{90}{90+10} = 9$.

Hence, the output voltage

$$v_o = v_1 \times \frac{50+100}{50} = 3v_1 = 27 \text{ V.}$$

10. Use two op amps, design a circuit such that $v_o = 2v_2 - v_1$, where v_1 and v_2 are inputs and v_o is output.

Solution:

