
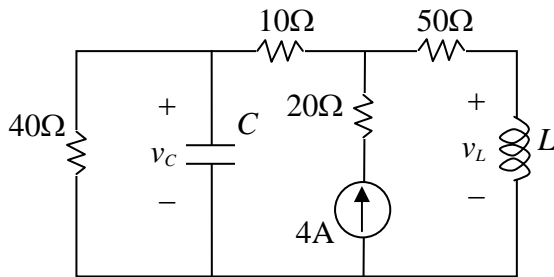


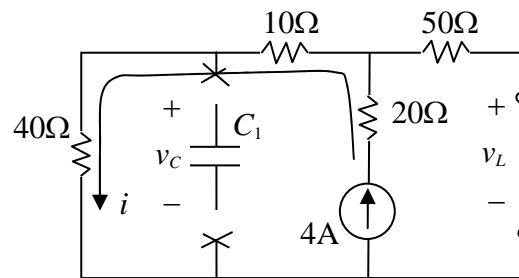1. Find v_C and v_L in the circuit under dc conditions.



Solution:

Under dc condition, C is open and L is short. Thus, the circuit is redrawn as



The current i is $i = \frac{50}{50 + (10 + 40)} \times 4 = 2 \text{ A}$. Hence, the voltage of C is $v_C = 40i = 80 \text{ V}$. Since the inductor L is short, its voltage $v_L = 0 \text{ V}$.

2. Express the following signal in terms of singularity functions.


$$x(t) = \begin{cases} 1 & -1 < t < 1 \\ 3 & 2 < t < 3 \\ 2 & 3 < t < 7 \\ 0 & \text{otherwise} \end{cases}$$

Solution:

The signal can be expressed as

$$x(t) = u(t+1) - u(t-1) + 3u(t-2) - u(t-3) - 2u(t-7)$$

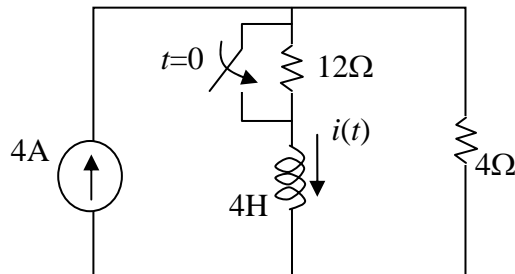
3. The switch has been operated for a long time and then it is closed at $t=0$. Determine $i(t)$ for $t > 0$.



Solution:

For $t=0^-$, the circuit is on the right and

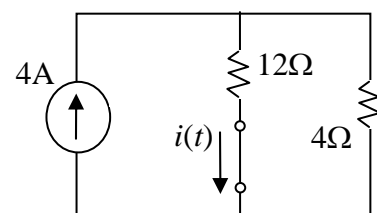
$i(0^-) = 4 \times \frac{4}{12+4} = 1 \text{ A}$. Since the inductor current can not abruptly change, at $t=0$ we have $i(0)=1 \text{ A}$.





Now for $t > 0$, the circuit is redrawn on the right, which is described by

$$\frac{di(t)}{dt} + i(t) = 4, \quad i(0) = 1 \text{ A}$$

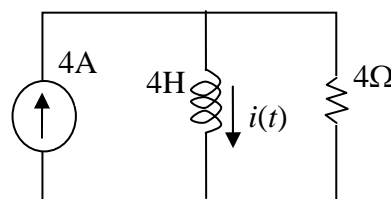where $L/R=1$. Hence, the solution is $i(t) = -3e^{-t} + 4 \text{ A}$ for $t > 0$.



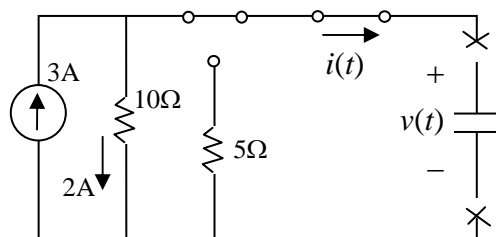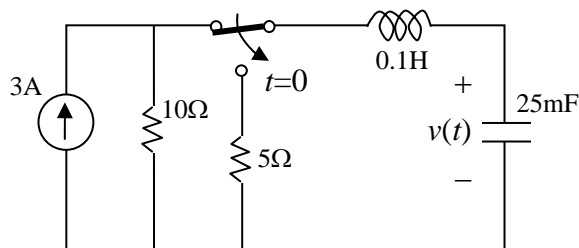4. The following circuit has been operated for a long time before $t=0$, find $v(t)$ for $t > 0$.



Solution:

For $t=0^-$, the circuit is redrawn on the right, where the inductor is short and the capacitor is open.

Hence, $v(0^-) = 3 \times 10 = 30 \text{ V}$ and $i(0^-) = 0$.

Then we have $\dot{v}(0^-) = \frac{1}{0.04} \times i(0^-) = 0$.

For $t > 0$, the circuit is redrawn on the right without source. and then $\ddot{v}(t) + 50\dot{v}(t) + 400v(t) = 0$, $v(0) = 30$, $\dot{v}(0) = 0$.

The characteristic equation is $\lambda^2 + 50\lambda + 400 = 0$


and the eigenvalues are $\lambda = -10$ or -40 . The solution only contains homogeneous part, which is written as

$$v(t) = A_1 e^{-10t} + A_2 e^{-40t}$$


Its derivative is $\dot{v}(t) = -10A_1 e^{-10t} - 40A_2 e^{-40t}$. Therefore, from initial conditions we have

$$v(0) = A_1 + A_2 = 30 \quad \text{and} \quad \dot{v}(0) = -10A_1 - 40A_2 = 0$$

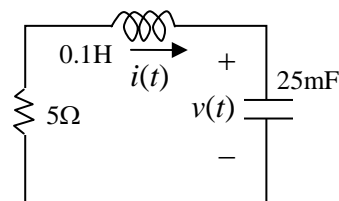which result in $A_1 = 40$ and $A_2 = -10$. Therefore, $v(t) = 40e^{-10t} - 10e^{-40t}$.



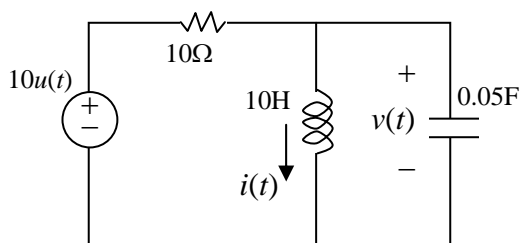5. In the following circuit, find $v(t)$ for $t > 0$. Assume $v(0) = 0 \text{ V}$ and $i(0) = 2 \text{ A}$.




Solution:

Since $v(t) = L \frac{di(t)}{dt}$,

we have $\frac{di(0^+)}{dt} = \frac{1}{L} v(0^+) = \frac{1}{L} v(0) = 0$.

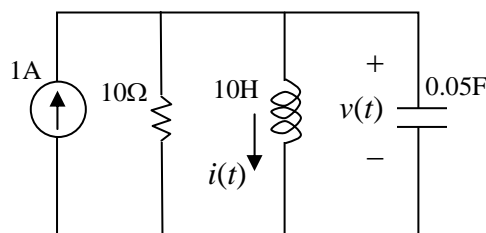For $t > 0$, the circuit is redrawn on the right,



which is described as

$$\frac{d^2i(t)}{dt^2} + \frac{1}{RC} \frac{di(t)}{dt} + \frac{i(t)}{LC} = \frac{1}{LC} \Rightarrow \frac{d^2i(t)}{dt^2} + 2 \frac{di(t)}{dt} + 2i(t) = 2$$

with initial conditions $\frac{di(0^+)}{dt} = 0$ and $i(0^+) = i(0) = 2$.

The characteristic equation is $\lambda^2 + 2\lambda + 2 = 0$

and the eigenvalues are $\lambda = -1 + j$ or $-1 - j$. The solution becomes

$$i(t) = e^{-t}(A_1 \cos(t) + A_2 \sin(t)) + 1$$

Its derivative is $\frac{di(t)}{dt} = -e^{-t}(A_1 \cos(t) + A_2 \sin(t)) + e^{-t}(-A_1 \sin(t) + A_2 \cos(t))$. Therefore, from initial conditions we have

$$i(0^+) = A_1 + 1 = 2 \quad \text{and} \quad \frac{di(0^+)}{dt} = -A_1 + A_2 = 0$$

which result in $A_1 = 1$ and $A_2 = 1$. Therefore, $i(t) = e^{-t}(\cos(t) + \sin(t)) + 1$, which leads to

$$v(t) = 10 \frac{di(t)}{dt} = -20e^{-t} \sin(t)$$

6. If $v_1(t) = 10 \cos(40t + \pi/4)$, $v_2(t) = 15 \cos(40t + 30^\circ)$ and $v(t) = v_1(t) + v_2(t)$, find the amplitude, phase and frequency f of $v(t)$.

Solution:

The phasors of $v_1(t)$ and $v_2(t)$ $V_1 = 10 \angle 45^\circ$ and $V_2 = 15 \angle 30^\circ$.


Then the phasor of $v(t)$ is

$$V = V_1 + V_2 = 10 \angle 45^\circ + 15 \angle 30^\circ$$

$$\begin{aligned} &= 10 \left(\frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \right) + 15 \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) \\ &= 10(0.707 + j0.707) + 15(0.866 + j0.5) \\ &= 7.07 + j7.07 + 12.99 + j7.5 \\ &= 20.06 + j14.57 = 24.7929 \angle 35.99^\circ \end{aligned}$$

The sum is $v(t) = 24.7929 \cos(40t + 35.99^\circ)$. Thus, its amplitude is 24.7929, its phase is 35.99° , and the frequency is $f = \frac{40}{2\pi} = 6.3662 \text{ s}^{-1}$.

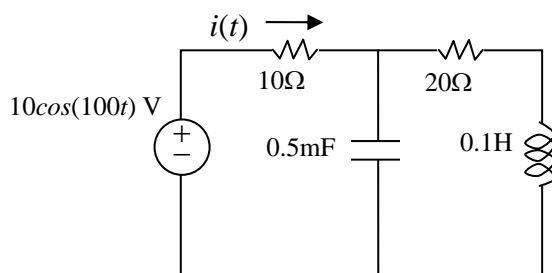7. In the following circuit, determine the steady-state current $i(t)$.



Solution:


Represent the circuit in the form of phasor on the right. The current phasor is obtained as

$$I = \frac{10\angle 0^\circ}{10 + \frac{-j20(20 + j10)}{(-j20) + (20 + j10)}}$$


$$= \frac{13 + j6}{41} = 0.3492\angle 24.7747^\circ$$

Hence,
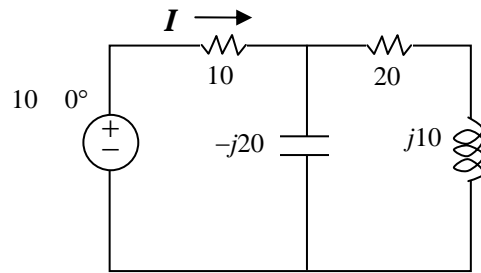
$$i(t) = 0.3492 \cos(100t + 24.7747^\circ)$$



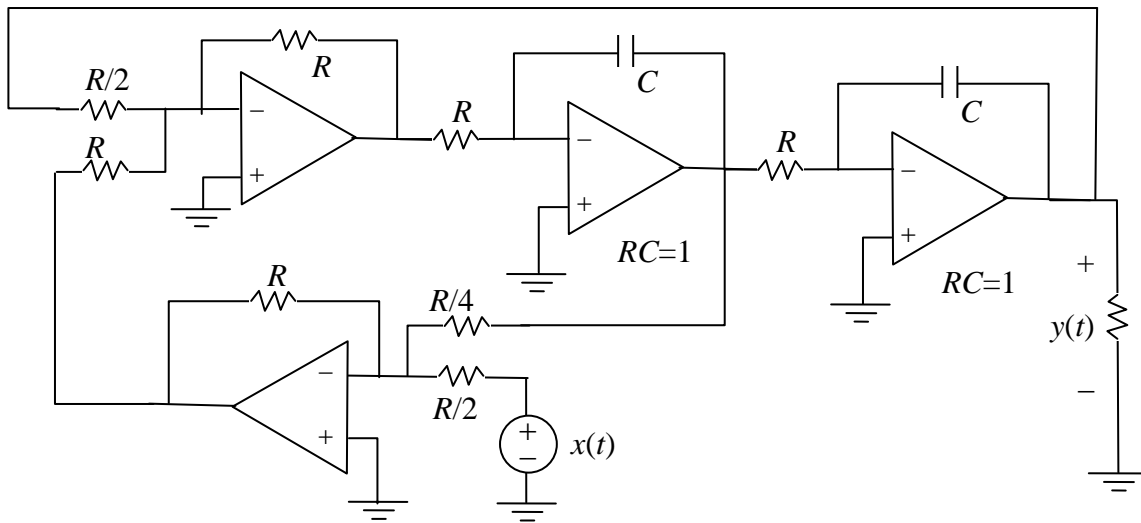8. The following analog computer circuit is used to solve an ordinary differential equation (ODE) with input $x(t)$ and output $y(t)$. If the initial conditions are neglected, what is the ODE?



Solution:

The ODE is $\frac{d^2 y(t)}{dt^2} = -4 \frac{dy(t)}{dt} - 2 y(t) + 2 x(t)$.