
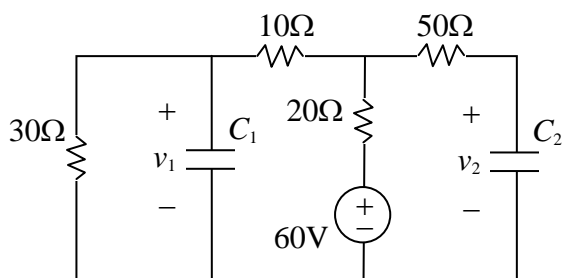


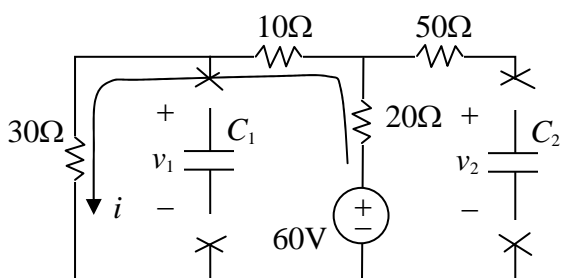1. Find v_1 and v_2 in the circuit under dc conditions.




Solution:

Under dc conditions, all the capacitors are treated as open and thus, the circuit is redrawn as



The current i is $i = \frac{60}{20+10+30} = 1 \text{ A}$. Hence, $v_1 = 30i = 30 \text{ V}$ and $v_2 = (10+30)i = 40 \text{ V}$.

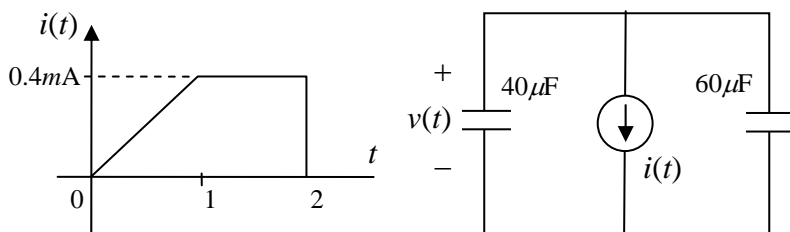2. Given the following circuit, sketch $v(t)$ for $t > 0$ if $v(0) = 1$.



Solution:

The circuit is equivalent to the circuit on the right.
Hence,

$$v(t) = v(t_0) - \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = v(t_0) - 10^4 \int_{t_0}^t i(\tau) d\tau$$

For $0 < t < 1$, $i(t) = 4 \times 10^{-4} t \text{ A}$

and then $v(t) = 1 - 10^4 \int_0^t (4 \times 10^{-4} \tau) d\tau = 1 - 2t^2 \text{ V}$.



At $t=1$, $v(1) = -1 \text{ V}$.

For $1 < t < 2$, $i(t) = 4 \times 10^{-4} \text{ A}$ and then


$v(t) = -1 - 10^4 \int_1^t (4 \times 10^{-4}) d\tau = -1 - 4(t-1) \text{ V}$.

At $t=2$, $v(2) = -5 \text{ V}$.

The curve is shown on the right.

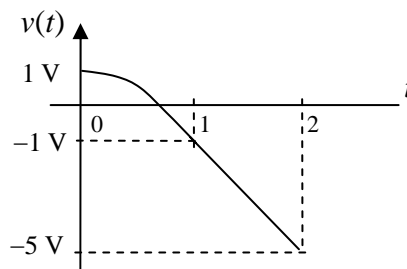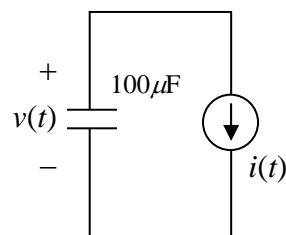

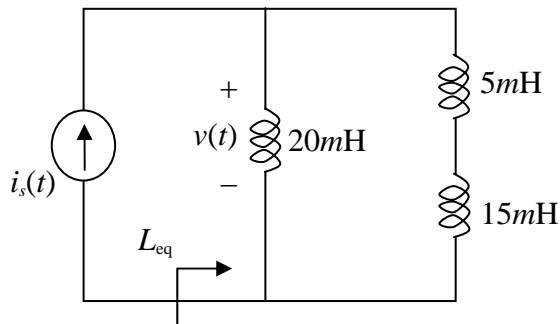3. In the following circuit, if $i_s(t) = 5e^{-2t}$ mA, find L_{eq} and $v(t)$.




Solution:

The equivalent inductance is $L_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{5+15}} = 10 \text{ mH}$.

The circuit is equivalent to the circuit on the right.

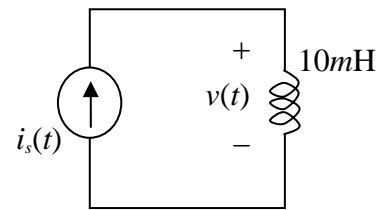Hence, $v(t) = L_{eq} \frac{di_s(t)}{dt} = 10^{-2} \times (-10e^{-2t}) = -0.1e^{-2t}$ mH.




4. Design an analog computer circuit to solve the following ordinary differential equation

$$\frac{dy(t)}{dt} + 3y(t) = 2f(t)$$

where $f(t)$ is the input and $y(t)$ is the output. Neglect the initial condition in this problem.

Solution:

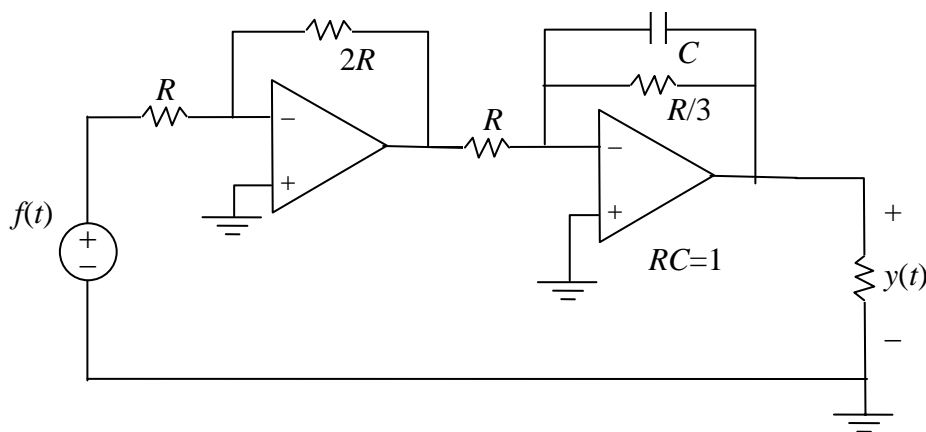The ODE is rewritten as $\frac{dy(t)}{dt} = -3y(t) + 2f(t)$ and the circuit is designed as below:



5. Express the following signal in terms of singularity functions.

$$x(t) = \begin{cases} t & 0 < t < 2 \\ 3 & 2 < t < 3 \\ 6-t & 3 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

Solution:

The signal can be expressed as

$$x(t) = r(t) - r(t-2) + u(t-2) - r(t-3) + r(t-8) + 2u(t-8)$$

6. Evaluate the following integrals:

$$(A) \int_{-\infty}^2 e^{(t-3)/2} \delta(t-1) dt$$

$$(B) \int_{-2}^2 (\cos(3t\pi)\delta(t+3) + \cos(2t\pi)\delta(t-1)) dt$$

$$(C) \int_{-\infty}^{\infty} 5(t-7)^7 \delta(6-t) dt$$


Solution:

$$(A) \int_{-\infty}^2 e^{(t-3)/2} \delta(t-1) dt = e^{-1} = 0.368$$

$$(B) \int_{-2}^2 (\cos(3t\pi)\delta(t+3) + \cos(2t\pi)\delta(t-1)) dt = \cos(2\pi) = 1$$

$$(C) \int_{-\infty}^{\infty} 5(t-7)^7 \delta(6-t) dt = -5$$

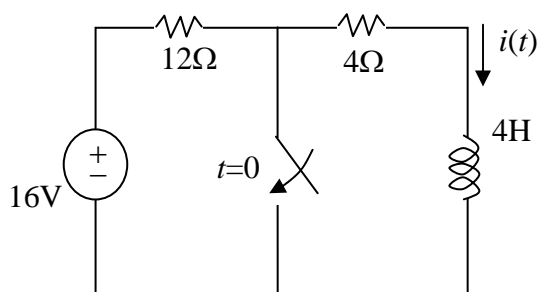7. The circuit has been operated for a long time and the switch is closed at $t=0$. Determine $i(t)$ for $t>0$.



Solution:

For $t=0^-$, we have the circuit on the right(up).


$$\text{The current } i(0^-) = \frac{16}{12+4} = 1 \text{ A.}$$

Since the inductor current can not abruptly change, at $t=0$ we have $i(0)=1$ A. Now for $t>0$, the circuit is shown on the right(down) and it is described by


$$\frac{di(t)}{dt} + i(t) = 0, \quad i(0) = 1 \text{ A}$$

where $R/L=1$. Hence, the solution is


$$i(t) = e^{-t} \text{ A for } t>0.$$

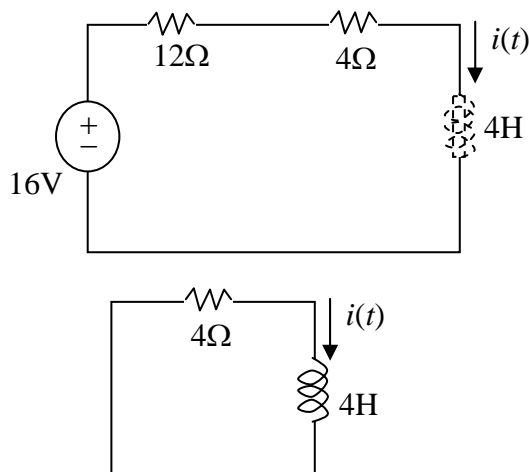

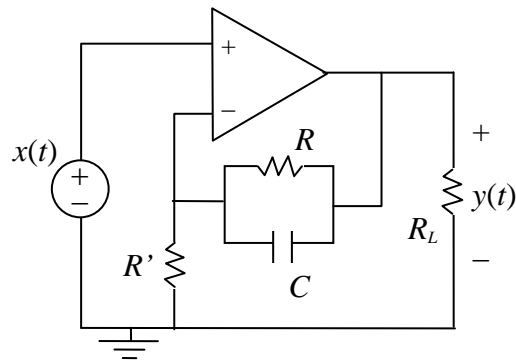8. Write the ordinary differential equation to describe the relationship between the output $y(t)$ and the input $x(t)$ of the following circuit which contains an ideal op amp. Note that R, R', R_L and C are given and the initial condition $y(0)$ is set to be 0.



Solution:

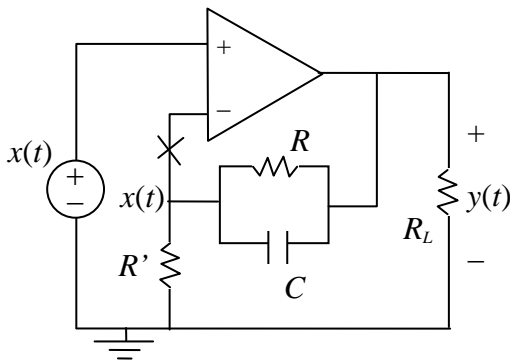

Since the use of an ideal op amp, we have the voltage $x(t)$ at the ‘-’ terminal, which is open. Hence, according to KCL, the circuit satisfies

$$\frac{x(t)}{R'} = \frac{y(t) - x(t)}{R} + C \frac{d(y(t) - x(t))}{dt}, \quad y(0) = 0 \text{ V}$$

$$\Rightarrow \dot{y}(t) + \frac{1}{RC} y(t) = \dot{x}(t) + \left(\frac{1}{RC} + \frac{1}{R'C} \right) x(t), \quad y(0) = 0 \text{ V}$$