
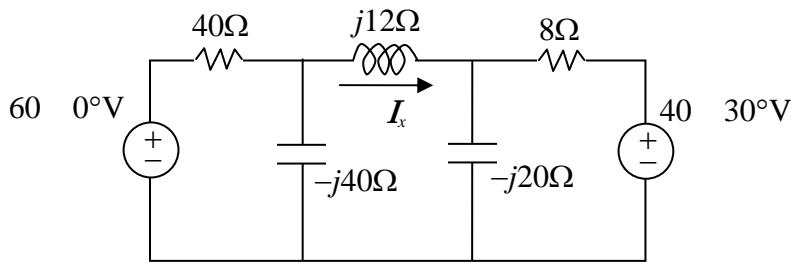


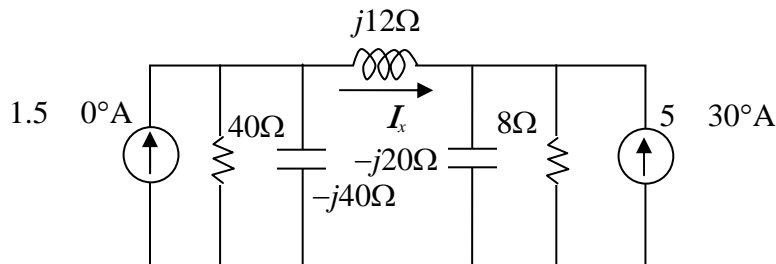1. Determine current  $I_x$  in the following circuit. (20%)




**Solution:**


Use source transformation, the circuit is redrawn as below:




Further, it is changed as below:

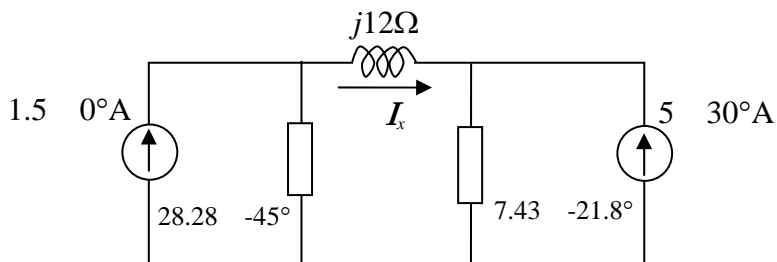

Then, we have

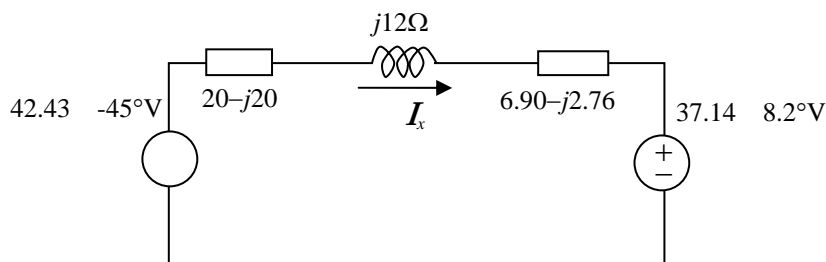


i.e.,

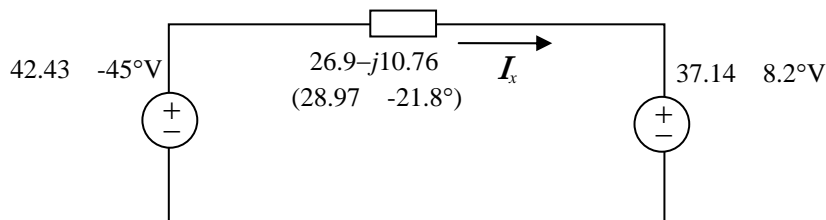

Hence,

$$I_x = \frac{42.43 \angle -45^\circ - 37.14 \angle 8.2^\circ}{28.97 \angle -21.8^\circ} = 0.24 - j1.22 \text{ A} = 1.24 \angle -79^\circ \text{ A}$$

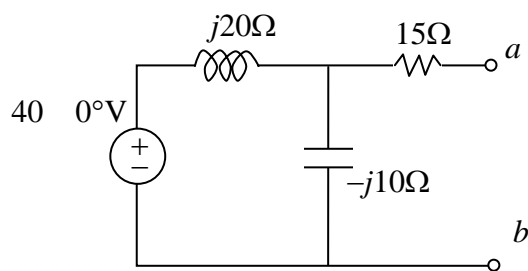2. Find the Norton equivalent circuit at terminals  $a-b$ . (20%)




**Solution:**

The Norton current  $I_N$  is the current passing the short path from  $a$  to  $b$  on the right:

Hence,

$$I_N = \frac{-j10}{15 - j10} \times \frac{40}{j20 + \frac{1}{\frac{1}{15} + \frac{1}{-j10}}}$$
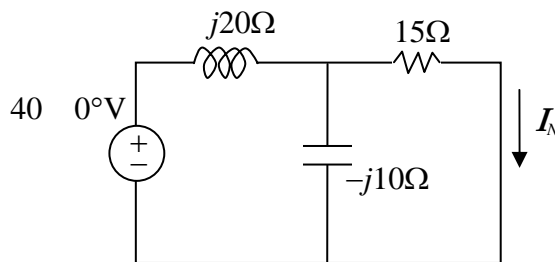
$$= -0.96 - j1.28 = 1.6 \angle -126.9^\circ$$




The Norton impedance is obtained by eliminating the voltage source on the right:


Hence,

$$Z_N = 15 + \frac{1}{\frac{1}{j20} + \frac{1}{-j10}}$$


$$= 15 - j20 = 25 \angle -53.1^\circ$$

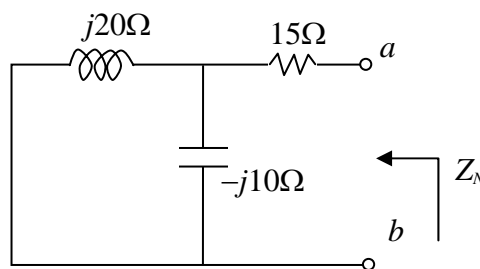

The equivalent circuit is

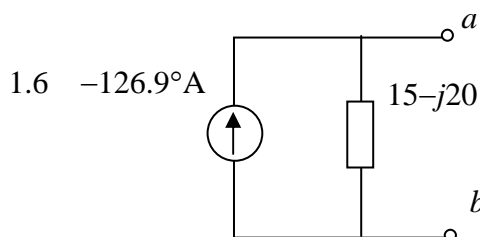


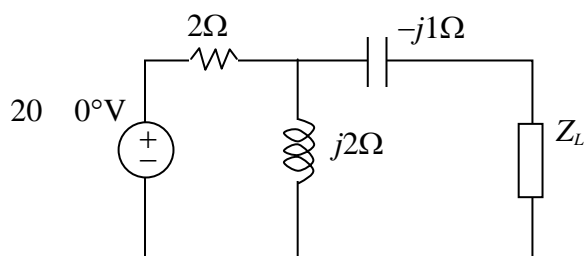3. Find  $Z_L$  that will absorb the maximum power and determine the maximum power. (20%)



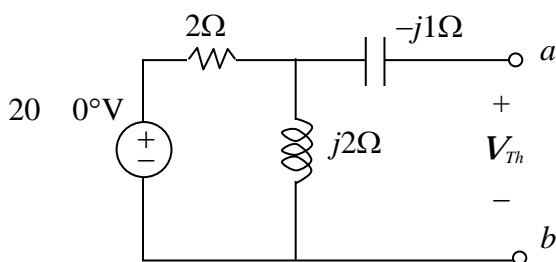
**Solution:**

First, find the Thevenin circuit. The Thevenin voltage  $V_{Th}$  is the voltage across the open terminals  $a$  to  $b$  as below:



It can be found that  $V_{Th} = 20 \times \frac{j2}{2+j2} = 10 + j10 = 14.14 \angle 45^\circ$

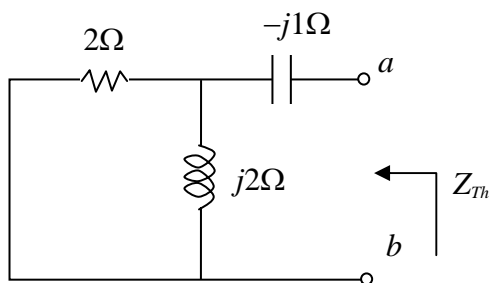The Thevenin impedance is obtained by eliminating the voltage source as below:




Hence,

$$Z_{Th} = -j + \frac{1}{\frac{1}{2} + \frac{1}{j2}} = 1$$

Clearly,  $Z_L = Z_{Th}^* = 1\Omega$  will absorb the maximum power and the maximum power is

$$P_L = \frac{V_{Th}^2}{8R_L} = \frac{14.14^2}{8} = 25 \text{ W}$$

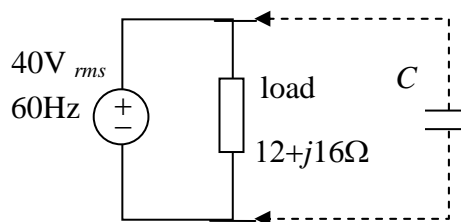4. In the circuit on the right, find (20%)  
 (A) the average power dissipated in the load,  
 (B) the reactive power delivered by the source,  
 (C) the power factor,



- (D) the capacitance  $C$  that will give a unity power factor when connected to the load.

**Solution:**

The effective current through the load is

$$I_L = \frac{40}{12 + j16} = 1.2 - j1.6$$

The complex power is  $S_L = V_L I_L^* = 40(1.2 + j1.6) = 48 + j64 \text{ VA}$ .

(A) The average power is 48 W.

(B) The reactive power is 64 VAR

(C) The power factor is  $pf = \frac{48}{\sqrt{48^2 + 64^2}} = 0.6$

(D) The admittance of the load is  $\frac{1}{12 + j16} = \frac{12 - j16}{400}$ .


To get a unity power factor, the capacitance must satisfy  $j\omega C = j\frac{16}{400}$ , i.e.,

$$C = \frac{16}{400\omega} = \frac{16}{400 \times 2\pi \times 60} = 106\mu\text{F}$$

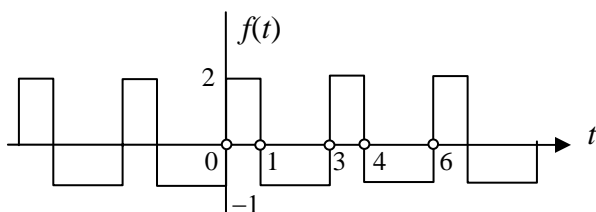5. The periodic function  $f(t)$  can be expressed as the following Fourier series: (20%)

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$

Find  $a_k$ ,  $k=0,1,2,3,4$ , and  $b_k$ ,  $k=1,2,3,4,5$ .



**Solution:**

The Fourier series expansion is

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$

where  $\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{3}$  and  $a_0 = \frac{1}{3} \left[ \int_0^1 2 dt + \int_1^3 (-1) dt \right] = 0$

$$\begin{aligned} a_n &= \frac{2}{3} \left[ \int_0^1 2 \cos(n\omega_0 t) dt - \int_1^3 \cos(n\omega_0 t) dt \right] \\ &= \frac{2}{3} \left[ \frac{2 \sin(n\omega_0 t)}{n\omega_0} \Big|_0^1 - \frac{\sin(n\omega_0 t)}{n\omega_0} \Big|_1^3 \right] = \frac{3}{n\pi} \sin\left(\frac{2n\pi}{3}\right) \end{aligned}$$

$$\begin{aligned} b_n &= \frac{2}{3} \left[ \int_0^1 2 \sin(n\omega_0 t) dt - \int_1^3 \sin(n\omega_0 t) dt \right] \\ &= \frac{2}{3} \left[ -\frac{2 \cos(n\omega_0 t)}{n\omega_0} \Big|_0^1 + \frac{\cos(n\omega_0 t)}{n\omega_0} \Big|_1^3 \right] = \frac{3}{n\pi} \left( 1 - \cos\left(\frac{2n\pi}{3}\right) \right) \end{aligned}$$

Hence,  $a_0 = 0$ ,  $a_1 = \frac{3\sqrt{3}}{2\pi}$ ,  $a_2 = -\frac{3\sqrt{3}}{4\pi}$ ,  $a_3 = 0$ ,  $a_4 = \frac{3\sqrt{3}}{8\pi}$

$$b_1 = \frac{9}{2\pi}, b_2 = \frac{9}{4\pi}, b_3 = 0, b_4 = \frac{9}{8\pi}, b_5 = \frac{9}{10\pi}$$