
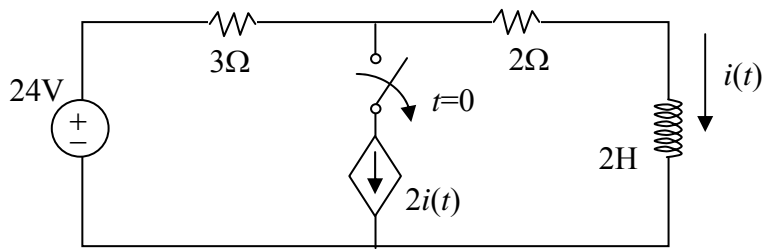


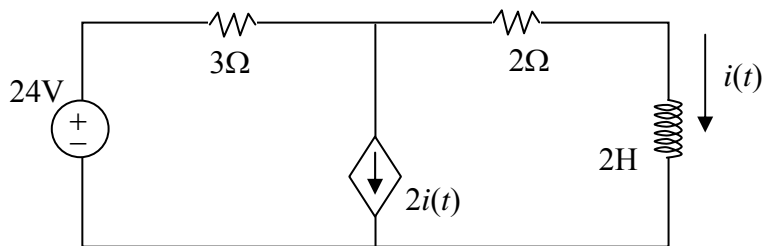1. Suppose that the switch has been closed for a long time and is opened at  $t=0$ . Determine the inductor current  $i(t)$  for  $t>0$ .




(12%)

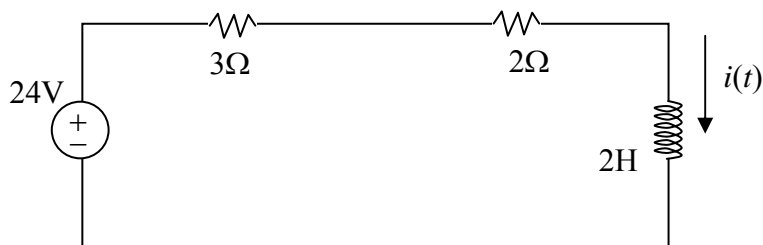**Sol:**



For  $t<0$ , we have

$$24 = 3(2i(0^-) + i(0^-)) + 2i(0^-) = 11i(0^-) \Rightarrow i(0^-) = \frac{24}{11}$$



For  $t>0$ , we have


$$24 = (3 + 2)i(t) + 2 \frac{di(t)}{dt} \Rightarrow \frac{di(t)}{dt} + \frac{5}{2}i(t) = 12$$

Hence,  $i(t) = Ae^{-\frac{5}{2}t} + \frac{24}{5}$ . Since  $i(0) = i(0^-) = \frac{24}{11}$ , we have


$$A + \frac{24}{5} = \frac{24}{11} \Rightarrow A = \frac{24}{11} - \frac{24}{5} = \frac{24 \times (-6)}{55} = -\frac{144}{55}$$

Therefore,  $i(t) = -\frac{144}{55}e^{-\frac{5}{2}t} + \frac{24}{5}$  A.

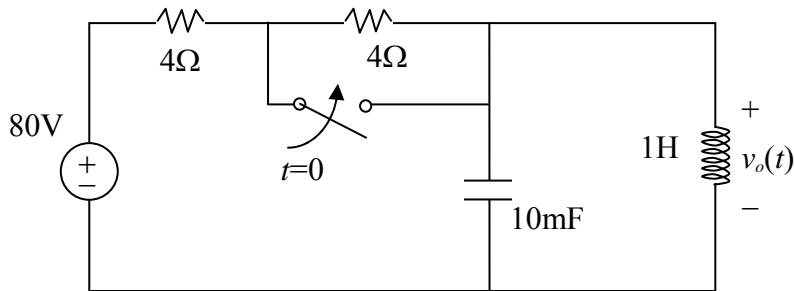
2. Suppose that the switch has been opened for a long time and is closed at  $t=0$ . Find the output voltage  $v_o(t)$  for  $t>0$ .



**Sol:**

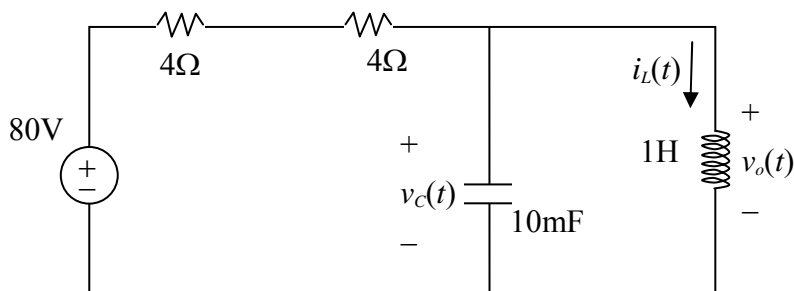

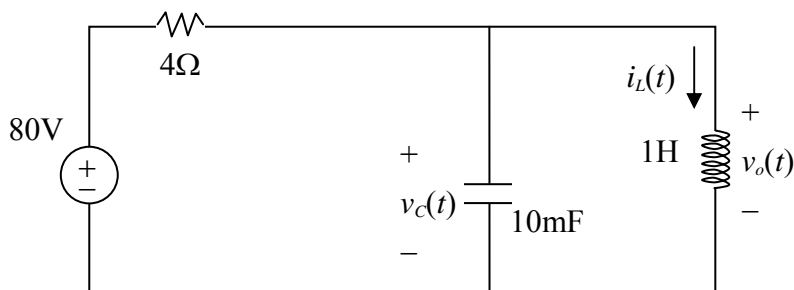For  $t<0$ , we have  $i_L(0^-) = \frac{80}{4+4} = 10$  and  $v_C(0^-) = 0$  (1)



For  $t>0$ , we have  $\frac{di_L(t)}{dt} = v_C(t)$  and  $\frac{dv_C(t)}{dt} = 100\left(\frac{80 - v_C(t)}{4} - i_L(t)\right)$

Therefore, from (1) we obtain  $v_C(0^-) = 0$  and  $\dot{v}_C(0^-) = 25 \times 80 - 100 \times 10 = 1000$ . Besides,


$$\ddot{v}_C(t) = -25\dot{v}_C(t) - 100\frac{di_L(t)}{dt} = -25\dot{v}_C(t) - 100v_C(t)$$

i.e.,  $\ddot{v}_C(t) + 25\dot{v}_C(t) + 100v_C(t) = 0$ . The eigenvalues satisfy  $\lambda^2 + 25\lambda + 100 = 0$  or  $\lambda = -5, -20$ , which results in  $v_C(t) = Ae^{-5t} + Be^{-20t}$  and  $\dot{v}_C(t) = -5Ae^{-5t} - 20Be^{-20t}$ . Thus,  $A+B=0$  and

$$-5A - 20B = 1000. \text{ Then we have } A = \frac{200}{3} \text{ and } B = -\frac{200}{3}.$$


Hence,  $v_o(t) = v_C(t) = \frac{200}{3}e^{-5t} - \frac{200}{3}e^{-20t}$ .

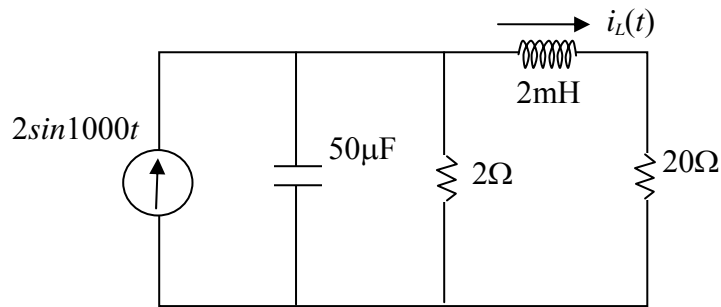3. Based on phasor method, determine the inductor current  $i_L(t)$ .



(15%)

**Sol:**

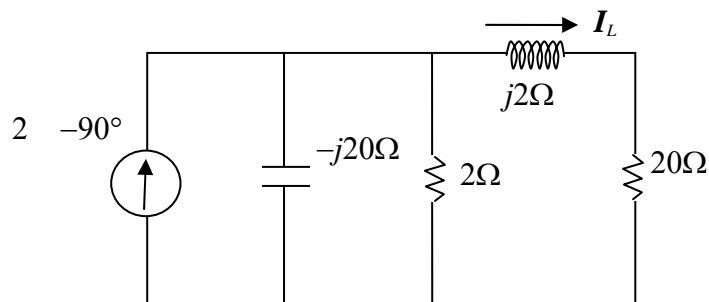


Based on phasor method, we have

$$\begin{aligned}
 I_L &= 2\angle -90^\circ \times \left( \frac{\frac{1}{20 + j2}}{\frac{j}{20} + \frac{1}{2} + \frac{1}{20 + j2}} \right) = \frac{-j2}{(20 + j2)\left(\frac{j}{20} + \frac{1}{2}\right) + 1} \\
 &= \frac{-j40}{(20 + j2)(j + 10) + 20} = -0.0326 - j0.1775 = 0.1805\angle -100.4^\circ
 \end{aligned}$$

Hence, we obtain


$$i_L(t) = 0.1805 \cos(1000t - 100.4^\circ)$$

4. Solve the phasor current  $I$ .

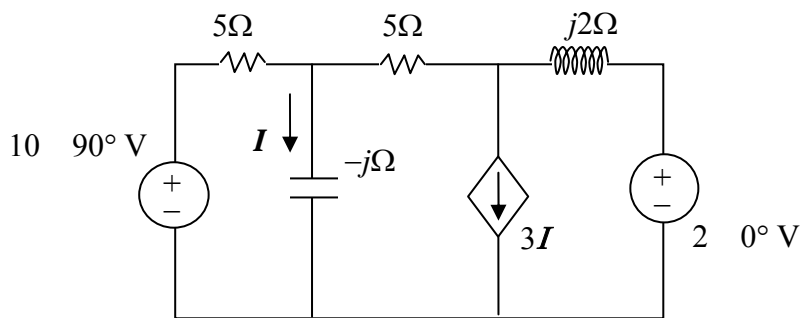

(15%)

Sol:

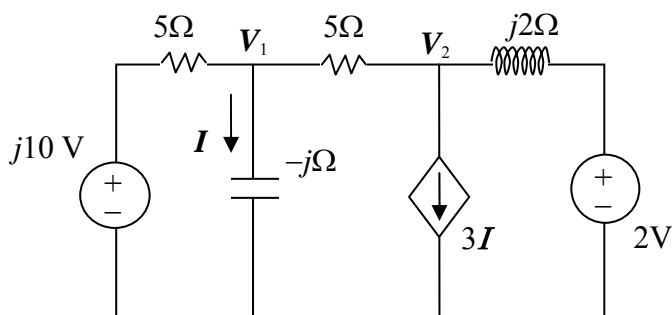

From nodal analysis, we have


$$\frac{V_1 - j10}{5} + \frac{V_1}{-j} + \frac{V_1 - V_2}{5} = 0 \Rightarrow (2 + j5)V_1 - V_2 = j10$$

$$\frac{V_2 - 2}{j2} + 3\frac{V_1}{-j} + \frac{V_2 - V_1}{5} = 0 \Rightarrow (-2 + j30)V_1 + (2 - j5)V_2 = -j10$$

Hence,  $V_1 = 1.0129 - j0.7551$  and  $V_2 = 5.8011 - j6.4457$ . Therefore, we have


$$I = \frac{V_1}{-j} = \frac{1.0129 - j0.7551}{-j} = 0.7551 + 1.0129j = 1.2634 \angle 53.3^\circ$$

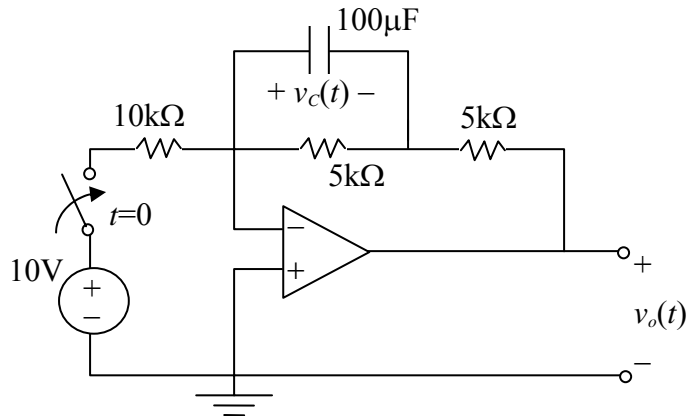5. For the circuit with an ideal OP-amp, if the capacitor voltage is initially charged to be  $v_c(0)=1\text{V}$ , determine the output voltage  $v_o(t)$  for  $t>0$ .



(12%)

**Sol:**

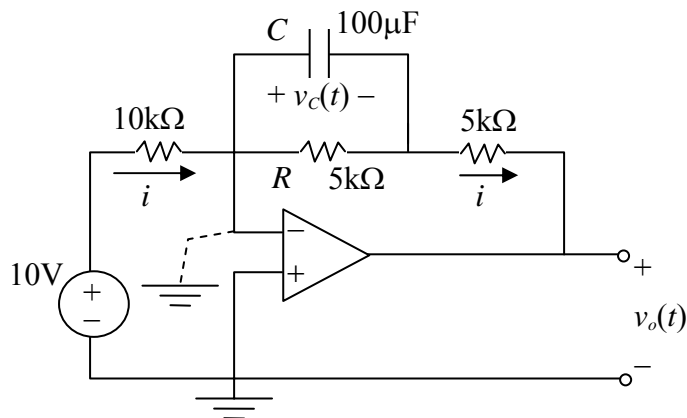

For  $t>0$ , we have

$$i(t) = \frac{10}{10\text{k}} = 1 \text{ mA}$$

and from the KCL, we obtain

$$\begin{aligned} i(t) &= C \frac{dv_c(t)}{dt} + \frac{v_c(t)}{R} \\ \Rightarrow \frac{dv_c(t)}{dt} + \frac{v_c(t)}{RC} &= \frac{i(t)}{C} \\ \Rightarrow \dot{v}_c(t) + 2v_c(t) &= 10 \\ \Rightarrow v_c(t) &= 5 + Ae^{-2t} \end{aligned}$$

Since  $v_c(0)=1$ , we have  $A=-4$ .

Furthermore,  $v_o(t) = -v_c(t) - 5000 \times 10^{-3} = -5 + 4e^{-2t} - 5 = 4e^{-2t} - 10 \text{ V}$ .


6. Consider the following third-order circuit with input voltage  $v(t)$ .

(a) Write the state equation  $\dot{\mathbf{x}}(t) = \mathbf{A}\mathbf{x}(t) + \mathbf{b}v(t)$ , where  $\mathbf{x}(t) = [x_1(t) \ x_2(t) \ x_3(t)]^T$  contains three state variables  $x_1(t)$ ,  $x_2(t)$  and  $x_3(t)$  shown in the circuit. (10%)

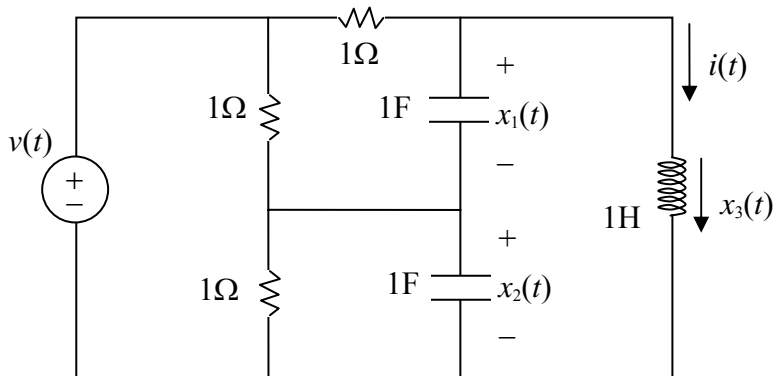
(b) Let the inductor current be the output, i.e.,  $y(t)=i(t)=x_3(t)$ . Then, the circuit can be described by a third-order differential equation given as (6%)

$$\ddot{y}(t) + a_2\dot{y}(t) + a_1y(t) = b_2\ddot{v}(t) + b_1\dot{v}(t) + b_0v(t)$$

Find the coefficients  $a_i$  and  $b_i$ ,  $i=0,1,2$ .



**Sol:**

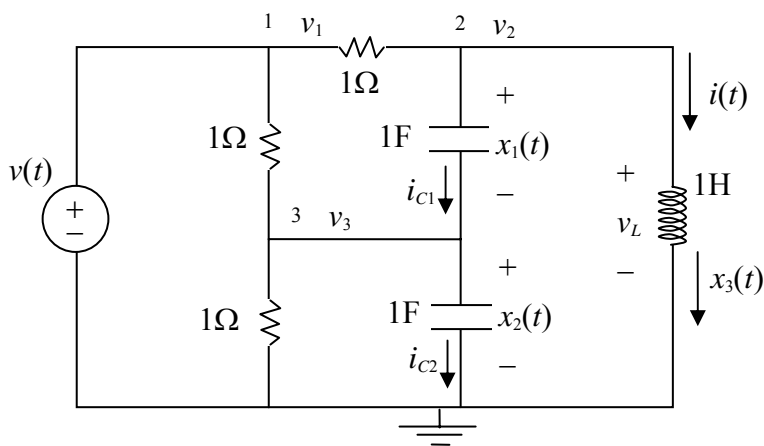

(a)

From nodal analysis and by treating state variables as sources, we have node equations

$$\begin{aligned} v_1 &= v(t) \\ v_2 &= x_1(t) + x_2(t) \\ v_3 &= x_2(t) \end{aligned}$$

Based on the component equations, we have

**NCTU 2008 Course: *Electric Circuit(I)***  
Midterm-2 (Cap7 to Chap10)

$$\begin{aligned}\dot{x}_1(t) &= i_{C1} = \frac{v_1 - v_2}{1} - i(t) = v(t) - (x_1(t) + x_2(t)) - x_3(t) \\ &= -x_1(t) - x_2(t) - x_3(t) + v(t) \\ \dot{x}_2(t) &= i_{C2} = i_1 + \frac{v_1 - v_3}{1} - \frac{v_3}{1} \\ &= -x_1(t) - x_2(t) - x_3(t) + v(t) + v(t) - x_2(t) - x_2(t) \\ &= -x_1(t) - 3x_2(t) - x_3(t) + 2v(t) \\ \dot{x}_3(t) &= v_L = v_2 = x_1(t) + x_2(t)\end{aligned}$$

Rearranging the above equations yields

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \\ \dot{x}_3(t) \end{bmatrix} = \begin{bmatrix} -1 & -1 & -1 \\ -1 & -3 & -1 \\ 1 & 1 & 0 \end{bmatrix} \cdot \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} + \begin{bmatrix} 1 \\ 2 \\ 0 \end{bmatrix} v(t)$$

(b)

Since  $y(t)=i(t)=x_3(t)$ , we have

$$\begin{aligned}y(t) &= x_3(t) \\ \dot{y}(t) &= \dot{x}_3(t) = x_1(t) + x_2(t) \\ \ddot{y}(t) &= \dot{x}_1(t) + \dot{x}_2(t) \\ &= -x_1(t) - x_2(t) - x_3(t) + v(t) - x_1(t) - 3x_2(t) - x_3(t) + 2v(t) \\ &= -2x_1(t) - 4x_2(t) - 2x_3(t) + 3v(t) \\ \ddot{\ddot{y}}(t) &= -2\dot{x}_1(t) - 4\dot{x}_2(t) - 2\dot{x}_3(t) + 3\dot{v}(t) \\ &= 2x_1(t) + 2x_2(t) + 2x_3(t) - 2v(t) \\ &\quad + 4x_1(t) + 12x_2(t) + 4x_3(t) - 8v(t) - 2x_1(t) - 2x_2(t) + 3\dot{v}(t) \\ &= 4x_1(t) + 12x_2(t) + 6x_3(t) - 10v(t) + 3\dot{v}(t)\end{aligned}$$

According to the characteristic equation

$$|\lambda \mathbf{I} - \mathbf{A}| = \begin{vmatrix} \lambda + 1 & 1 & 1 \\ 1 & \lambda + 3 & 1 \\ -1 & -1 & \lambda \end{vmatrix} = \lambda^3 + 4\lambda^2 + 4\lambda + 2$$


the third-order differential equation can be derived as

$$\ddot{\ddot{y}}(t) + 4\ddot{y}(t) + 4\dot{y}(t) + 2y(t) = 3\dot{v}(t) + 2v(t)$$

Hence, we obtain  $a_2=4$ ,  $a_1=4$ ,  $a_0=2$ ,  $b_2=0$ ,  $b_1=3$ ,  $b_0=2$ .

7. Complete the design of  $R$  in the following oscillator and calculate its oscillation frequency.

(15%)

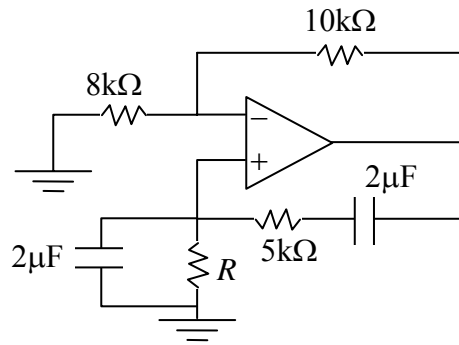


**Sol:**

It is true that  $v_1$  and  $v_o$  must be in phase.

Therefore, their phasors must satisfy the following condition:
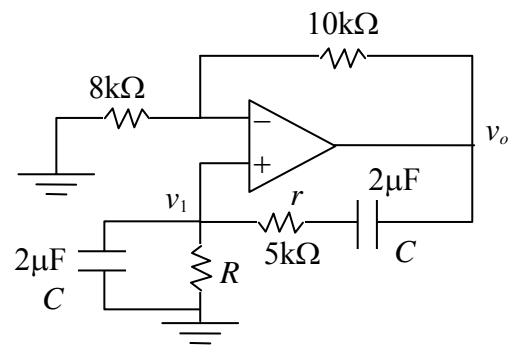
$$\frac{V_1}{V_o} = \frac{8}{10+8} = \frac{\frac{1}{R^{-1} + j\omega C}}{\frac{1}{R^{-1} + j\omega C} + r + \frac{1}{j\omega C}}$$



Hence,

$$\frac{4}{9} = \frac{\frac{R}{1 + j\omega RC}}{\frac{R}{1 + j\omega RC} + r + \frac{1}{j\omega C}} = \frac{R}{R + \left(r + \frac{1}{j\omega C}\right)(1 + j\omega RC)}$$

$$\Rightarrow \frac{4}{9} = \frac{R}{2R + r + j\left(\omega r RC - \frac{1}{\omega C}\right)}$$

$$\Rightarrow \begin{cases} \frac{4}{9} = \frac{R}{2R + r} \\ \omega r RC - \frac{1}{\omega C} = 0 \end{cases}$$

$$\Rightarrow R = 4r = 20\text{k}\Omega \quad \text{and} \quad \omega = \sqrt{\frac{1}{rRC^2}} = \frac{1}{2rC} = 50$$

$$\Rightarrow R = 20\text{k}\Omega \quad \text{and} \quad f = \frac{50}{2\pi} \text{ Hz}$$