

1. For the following signal

10% $x(t) = e^{-2t} [u(t) - u(t-1)]$

find the Laplace transform $X(s)$ and sketch the pole/zero plot.


2. Given the following Laplace transform

12% $X(s) = \frac{5}{s^3 + s^2 - 2}$

(a) find all the possible $x(t)$ corresponding to different ROCs.

(b) determine the causality and stability of $x(t)$ found in (a).

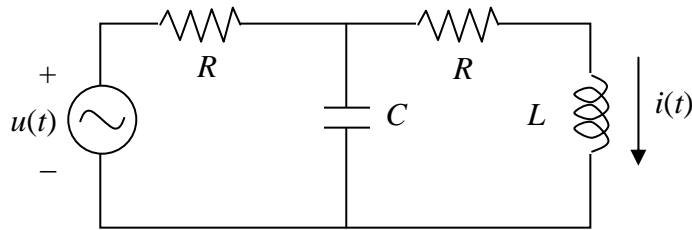3. Consider the following circuit with $R=1\Omega$, $C=1F$, $L=1H$:



10%

(a) Find the transfer function $H(s)$, which is equal to $I(s)/U(s)$ with $I(s)$ and $U(s)$ being the Laplace transform of $i(t)$ and $u(t)$, respectively.

3%

(b) As $t \rightarrow \infty$, determine $i(t)$ if $u(t) = \sin(2t)$ (volt).

3%

(c) As $t \rightarrow \infty$, determine $i(t)$ if $u(t) = 1$ (volt).

6% (d) The circuit can be expressed as $\dot{\mathbf{x}} = \mathbf{A}\mathbf{x} + \mathbf{b}u(t)$, where

$$\mathbf{x} = [x_1 \ x_2]^T, \quad x_1 = i(t), \text{ and } x_2 = v(t). \text{ Please find } \mathbf{A} \text{ and } \mathbf{b}.$$

12%

(e) Calculate $e^{\mathbf{A}t}$.

4. Design the third order Butterworth filter $H(s)$ with half-power frequency set at $\omega = 2 \text{ rad/sec}$.

16%

(a) What is the transfer function $H(s)$.

3%

(b) Express the filter in ODE with input $x(t)$ and output $y(t)$.

5. Use OPAMps to implement the following system:

15% $H(s) = \frac{s^2 + 1}{s^3 + 3s^2 + 5s + 3}$

6. Determine the following system function $H(s)$:

10%

